



Daffodil
International
University

Microwave Engineering



ETE 415

LECTURE 2
TRANSMISSION-LINE THEORY-I

T-Line Theory


T-Lines are used in countless ways in modern society

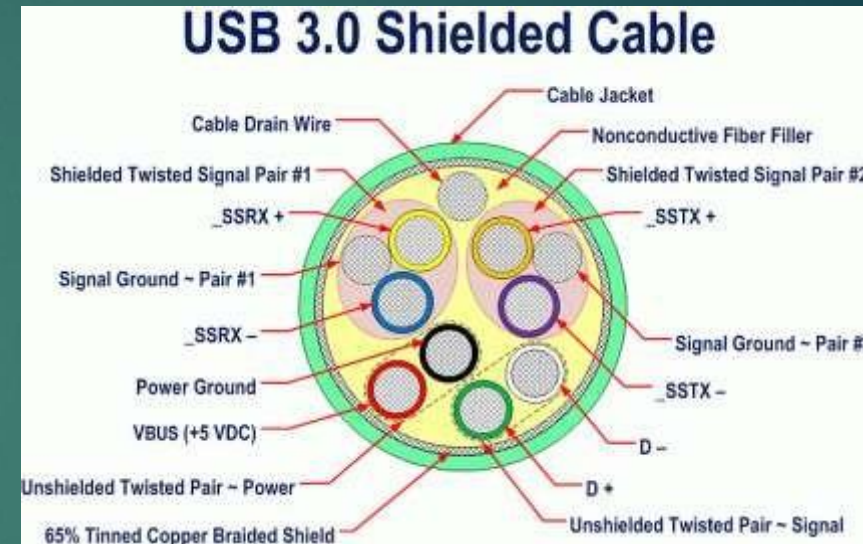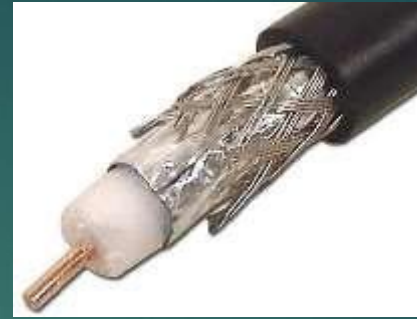- Communications
- Electronics circuits/ Computers
- Power distribution
- Photonics



Why T-Lines?-I

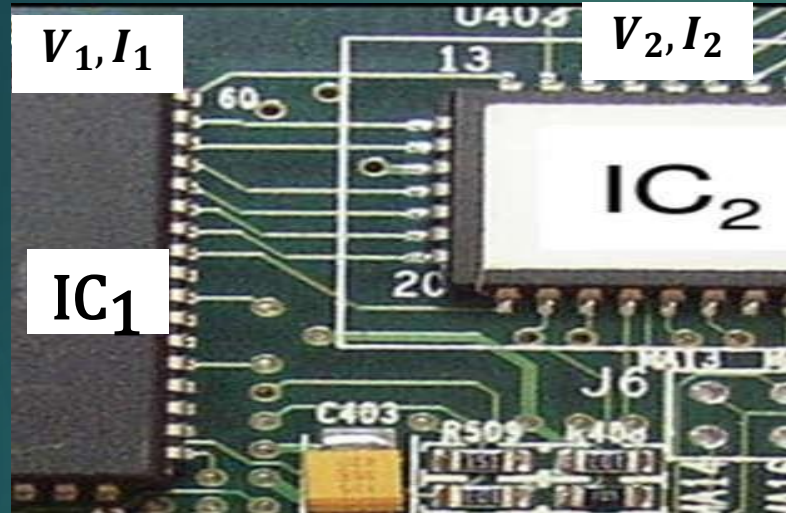Consider two ICs being connected by conducting traces on PCB.



When the voltage at **1** changes state, does that new voltage appear at **2** Instantaneously ?



If these two points are separated by a large electrical distance, there will be a **propagation delay** as the change in state (electrical signal) travels to 2. \Rightarrow Not an instantaneous effect!!

This propagation of voltage signals is modeled as a **“T-line”**.

We will see that **voltage and current can propagate along a T-Line as waves!**
Fantastic.


T-Line Theory

- Lumped circuits: resistors, capacitors, inductors

Neglects time delays (phase change)

- Distributed circuit elements: T-lines

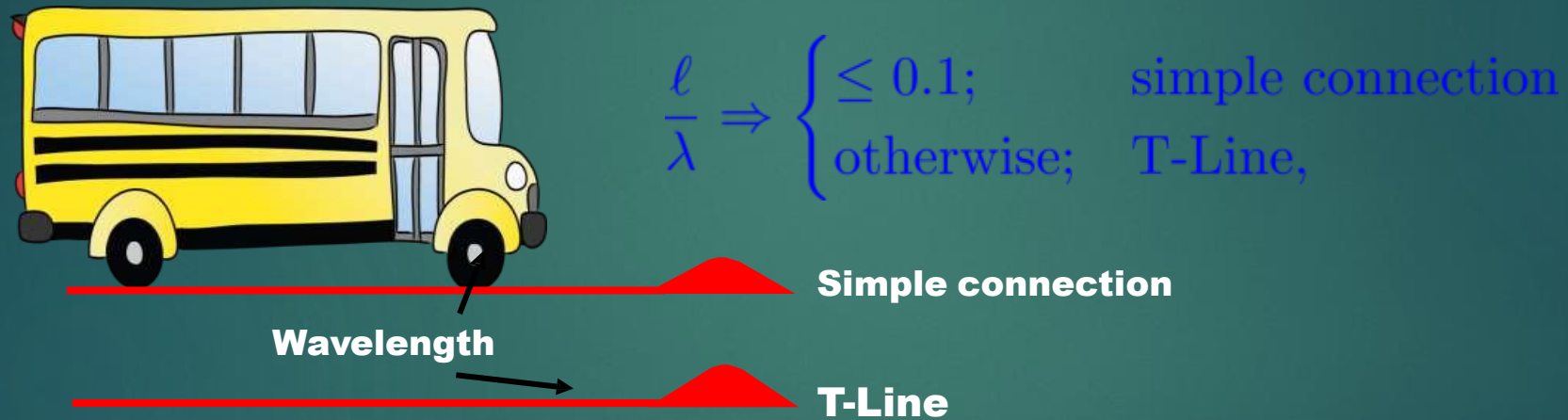
Account for propagation and time delays (phase change)



We need T-line theory whenever the length of a line is significant compared to a wavelength.

TEM T-Lines


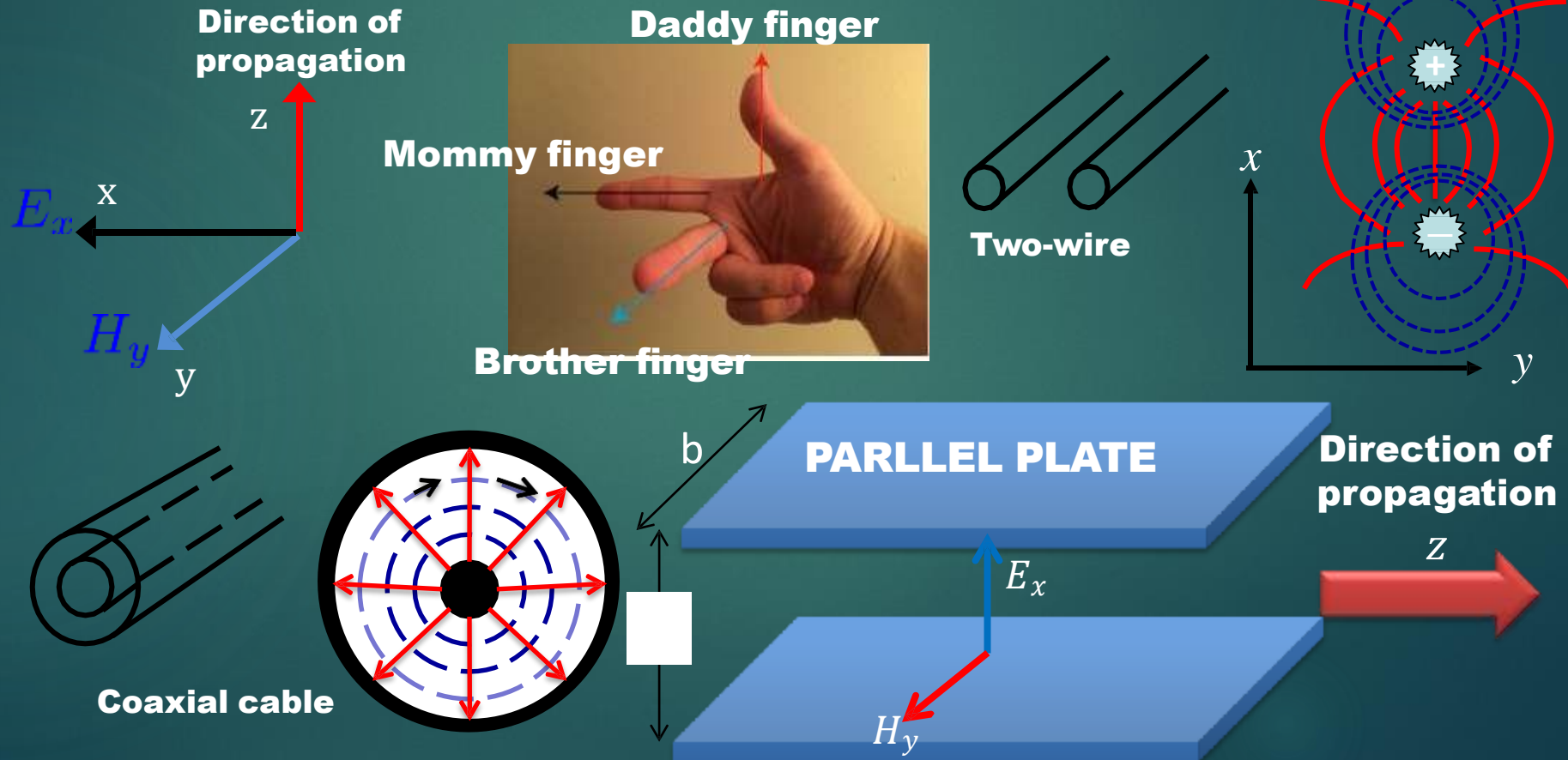
- All true TLs share one common characteristic: the E and H fields are all \perp the direction of propagation.
- These are called **TEM fields** for **t**ransverse **e**lectric and **m**agnetic fields.




T-Line Model (*RLGC* Model)

- There is **conduction current** in the two conductors and a **displacement current** between these two conductors where the electric field E is varying with time.
- Conduction current impedance effects:
 - R' [Ω/m], series resistance due to losses in the conductors,
 - L' [H/m], series inductance due to the current flow in the conductors and the magnetic flux linking the current path.
- Displacement current impedance effects:
 - G' [S/m], shunt conductance due to losses in the dielectric between the conductors,
 - C' [F/m], shunt capacitance due to the time varying electric field between the two conductors.




Note: R' and G' , represent loss.

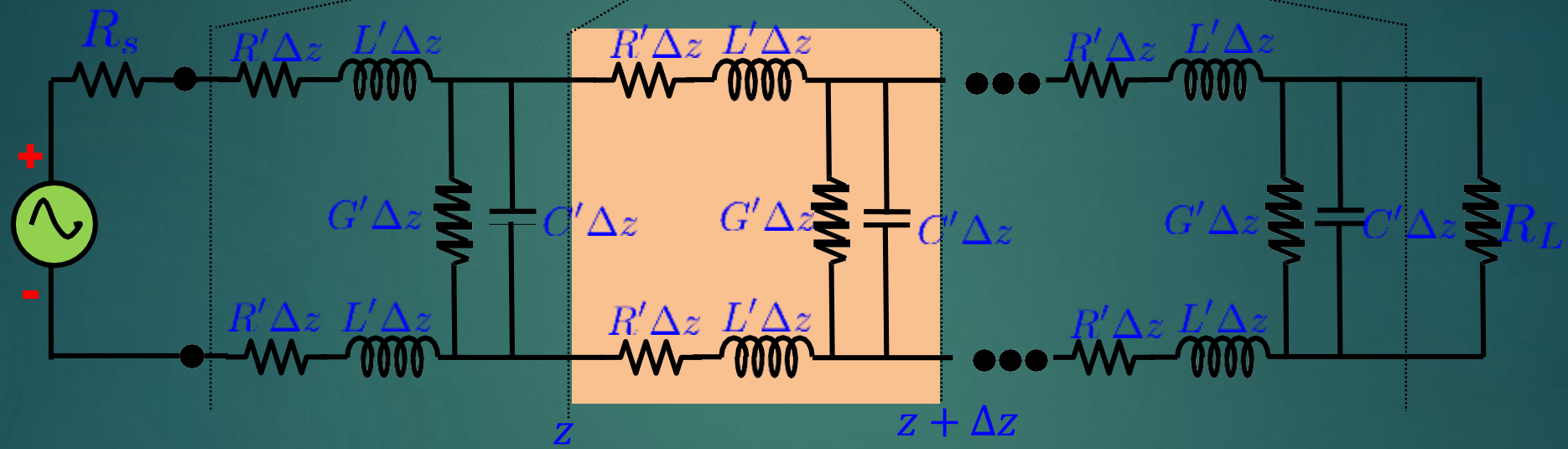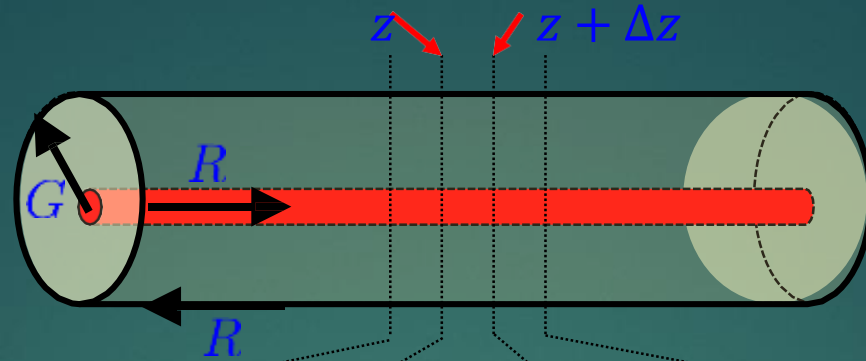

Generic equivalent circuit model

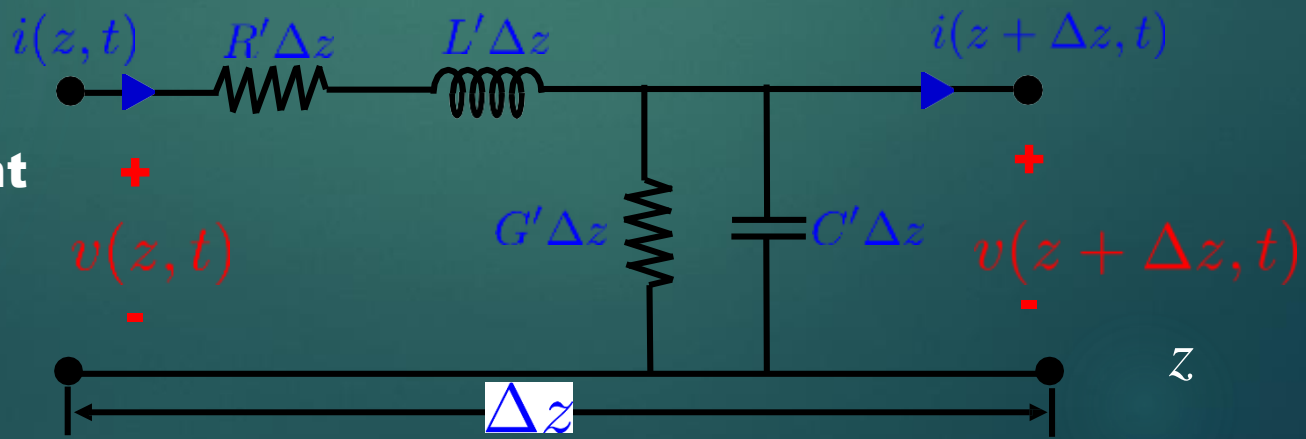


A 4 nsec, 80 Ω , lumped element T-Line

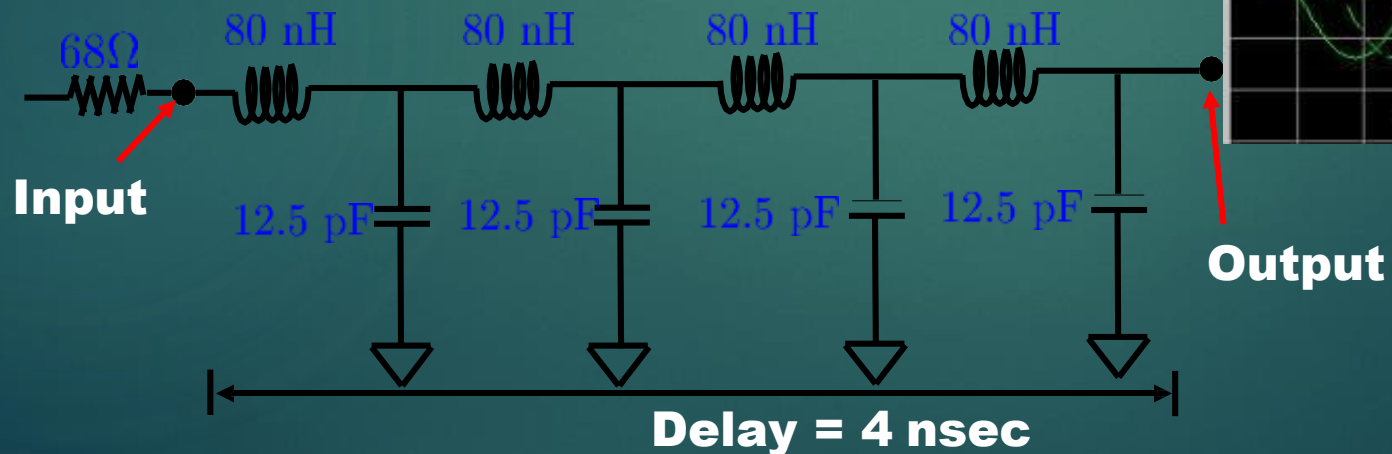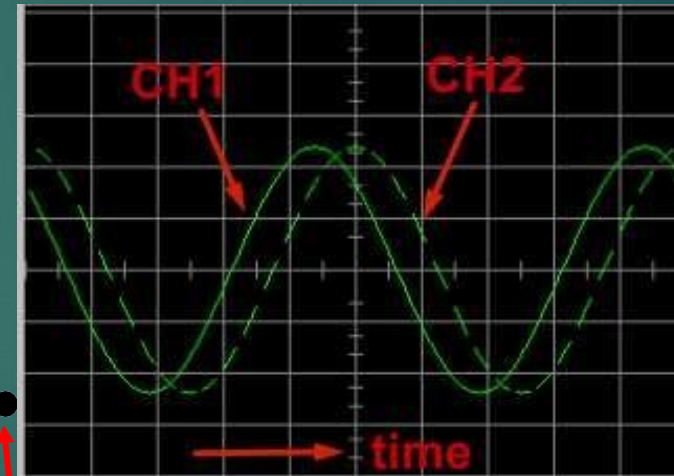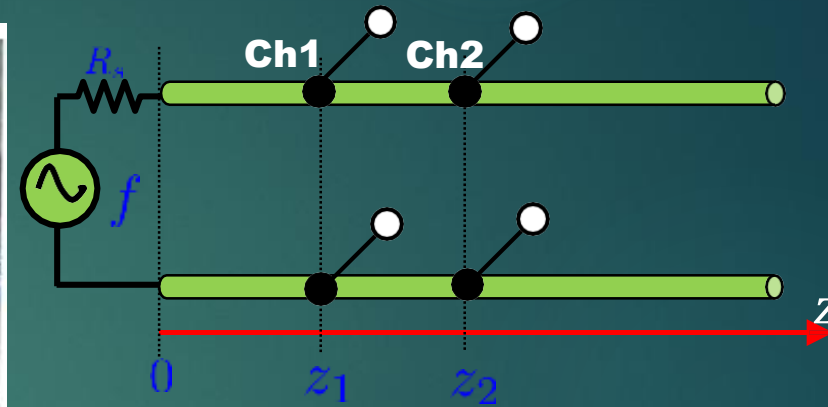

Analysis of T-Lines

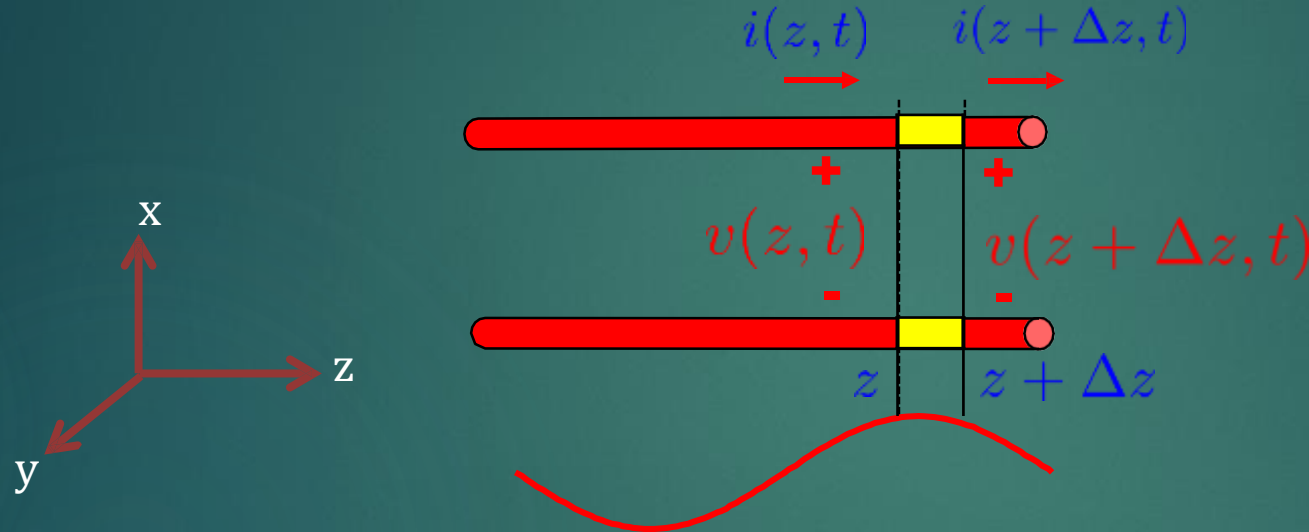On a T-Line, the **voltage and current vary along the structure in time t and spatially in the z direction** \Rightarrow they are expressed as $i(z, t)$, and $v(z, t)$, respectively




How do we solve for $v(z, t)$ and $i(z, t)$?

- We first need to develop the **governing equations** for the voltage and current, and then solve these equations.



T-Line Equations-I

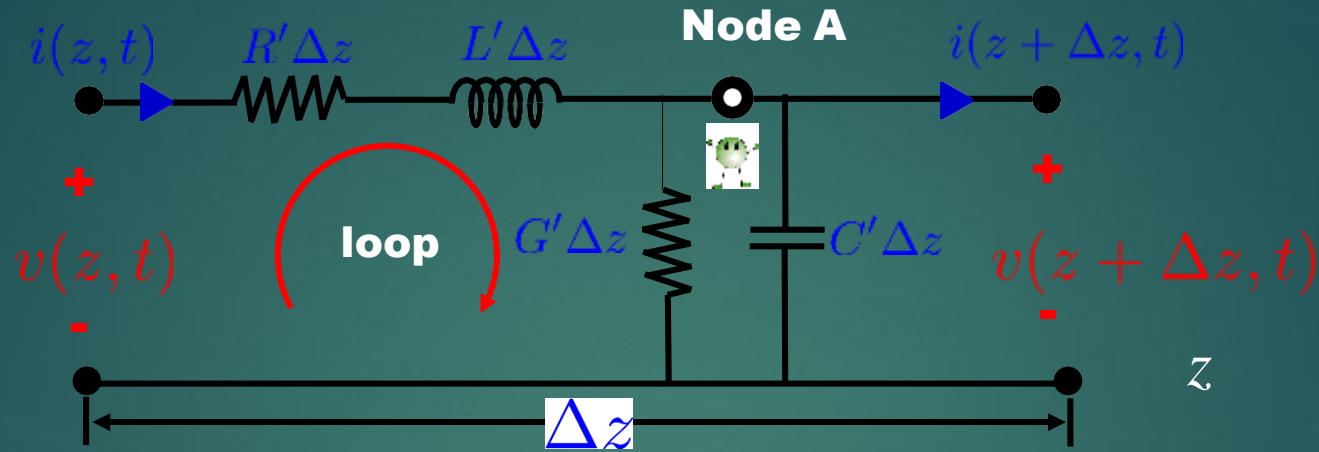

■ To develop the governing equation for $v(z, t)$, apply **KVL**:

$$v(z, t) = v(z + \Delta z, t) + i(z, t)R' \Delta z + L' \Delta z \frac{\partial i(z, t)}{\partial t} \quad (1a)$$

$$\Delta v = v(z + \Delta z, t) - v(z, t) = -i(z, t)R' \Delta z - L' \Delta z \frac{\partial i(z, t)}{\partial t}$$

■ Similarly, for the current $i(z, t)$ apply **KCL** at the node A:

$$i(z, t) = i(z + \Delta z, t) + v(z + \Delta z, t)G' \Delta z + C' \Delta z \frac{\partial v(z + \Delta z, t)}{\partial t} \quad (1b)$$

$$\Delta i = i(z + \Delta z, t) - i(z, t) = -v(z + \Delta z, t)G' \Delta z - C' \Delta z \frac{\partial v(z + \Delta z, t)}{\partial t}$$

T-Line Equations-II

Divide (1a) and (1b) by Δz :

$$\frac{v(z + \Delta z, t) - v(z, t)}{\Delta z} = -R' i(z, t) - L' \frac{\partial i(z, t)}{\partial t} \quad (2)$$

$$\frac{i(z + \Delta z, t) - i(z, t)}{\Delta z} = -G' v(z + \Delta z, t) - C' \frac{\partial v(z + \Delta z, t)}{\partial t} \quad (3)$$

➔ In the limit as $\Delta z \rightarrow 0$, the term on the LHS in (2) and (3) is the **forward difference definition of derivative**. Hence,

$$\frac{\partial v(z, t)}{\partial z} = -R' i(z, t) - L' \frac{\partial i(z, t)}{\partial t} \quad (4)$$

$$\frac{\partial i(z, t)}{\partial z} = -G' v(z, t) - C' \frac{\partial v(z, t)}{\partial t} \quad (5)$$

coupled partial differential equations

Eqs. (4) and (5) are called the **telegrapher equations** or the **T-Line equations**.

T-Line Wave Equations-I

- Now combine (4) and (5) to form two equations, each a **function of v or i only**.

- To do this, take $\frac{\partial}{\partial z}$ of Eq. (4) $\left(\frac{\partial v}{\partial z} = -R'i - L'\frac{\partial i}{\partial t}\right)$: **Switch the order of the derivatives.**

$$\frac{\partial^2 v}{\partial z^2} = -R'\frac{\partial i}{\partial z} - L'\frac{\partial}{\partial z}\left(\frac{\partial i}{\partial t}\right) = -R'\frac{\partial i}{\partial z} - L'\frac{\partial}{\partial t}\left(\frac{\partial i}{\partial z}\right)$$

- Substituting from Eq. (5) $\left(\frac{\partial i}{\partial z} = -G'v - C'\frac{\partial v}{\partial t}\right)$:

$$\frac{\partial^2 v}{\partial z^2} = -R'\left[-G'v - C'\frac{\partial v}{\partial t}\right] - L'\left[-G'\frac{\partial v}{\partial t} - C'\frac{\partial^2 v}{\partial t^2}\right]$$

$$\frac{\partial^2 v}{\partial z^2} - (R'G')v - (R'C' + L'G')\frac{\partial v}{\partial t} - L'C'\frac{\partial^2 v}{\partial t^2} = 0$$

- The same equation also holds for i .

$$\frac{\partial^2 i}{\partial z^2} - (R'G')i - (R'C' + L'G')\frac{\partial i}{\partial t} - L'C'\frac{\partial^2 i}{\partial t^2} = 0$$

T-Line Wave Equations-II

Time-Harmonic Waves:

$$\frac{\partial}{\partial t} \rightarrow j\omega$$

$$\frac{d^2 V}{dz^2} - \underline{(R'G')}V - \underline{(R'C' + L'G')}j\omega V - \underline{L'C'(-\omega^2)}V = 0$$

Convention: small letter for time-domain form, capital letter for phasor.

Note that

$$R'G' + j\omega(R'C' + L'G') - \omega^2 L'C' = (R' + j\omega L')(G' + j\omega C')$$

Then we can write

$$\frac{d^2 V}{dz^2} - \gamma^2 V = 0 \quad \text{and} \quad \frac{d^2 I}{dz^2} - \gamma^2 I = 0$$

➔ Where

$$\gamma = \alpha + j\beta = \sqrt{(R' + j\omega L')(G' + j\omega C')}$$

➔ is the complex propagation constant, which is a function of frequency.

➔ $\alpha \geq 0$ is the attenuation constant and $\beta \geq 0$ is the phase constant.



Voltage Wave Equation Solutions

- The voltage wave equation has solution in the form

$$V(z) = \underbrace{V_o^+ e^{-\gamma z}}_{V^+(z)} + \underbrace{V_o^- e^{\gamma z}}_{V^-(z)}$$

+z wave **-z wave**

Note: $V_o^\mp = |V_o^\mp| e^{j\phi^\mp}$

Complex

- where ϕ^\mp is the phase angle of the complex voltage V_o^\mp

- Forward** travelling wave (a wave traveling in the +z direction):

$$V^+(z) = V_o^+ e^{-\gamma z} = V_o^+ e^{-\alpha z} e^{-j\beta z}$$

$\gamma = \alpha + j\beta$

- Converting back to the time domain

$$\begin{aligned} v^+(z, t) &= \Re \left\{ (V_o^+ e^{-\alpha z} e^{-j\beta z}) e^{j\omega t} \right\} \\ &= \Re \left\{ \left(|V_o^+| e^{j\phi^+} e^{-\alpha z} e^{-j\beta z} \right) e^{j\omega t} \right\} \\ &= |V_o^+| e^{-\alpha z} \cos(\omega t - \beta z + \phi^+) \end{aligned}$$

Voltage Wave Equation Solutions

■ **Backward** travelling wave (a wave traveling in the $-z$ direction):

$$V^-(z) = V_o^- e^{+\gamma z} = V_o^- e^{+\alpha z} e^{+j\beta z}$$

■ Converting back to the time domain

$$\begin{aligned} v^-(z, t) &= \Re \left\{ (V_o^- e^{\alpha z} e^{j\beta z}) e^{j\omega t} \right\} \\ &= \Re \left\{ \left(|V_o^-| e^{j\phi^-} e^{\alpha z} e^{j\beta z} \right) e^{j\omega t} \right\} \\ &= |V_o^-| e^{+\alpha z} \cos(\omega t + \beta z + \phi^-) \end{aligned}$$

➡ where ϕ^- is the phase angle of the complex voltage V_o^-

■ Complete time domain solution:

$$\begin{aligned} v(z, t) &= \Re \{ V(z) e^{j\omega t} \} \\ &= |V_o^+| e^{-\alpha z} \cos(\omega t - \beta z + \phi^+) + |V_o^-| e^{+\alpha z} \cos(\omega t + \beta z + \phi^-) \\ i(z, t) &= |I_o^+| e^{-\alpha z} \cos(\omega t - \beta z + \phi^+) + |I_o^-| e^{+\alpha z} \cos(\omega t + \beta z + \phi^-) \end{aligned}$$


Attenuation Constant (α)

■ **The attenuation constant α [Np/m]:** decreases the amplitude of the voltage and current wave along the T-Line.

■ For +ve traveling wave:


$$1 \text{ Np} = 10 \log e^2 = 8.686 \text{ dB}$$

$$v^+(z, t) = |V_o^+| e^{-\alpha z} \cos(\omega t - \beta z + \phi^+)$$

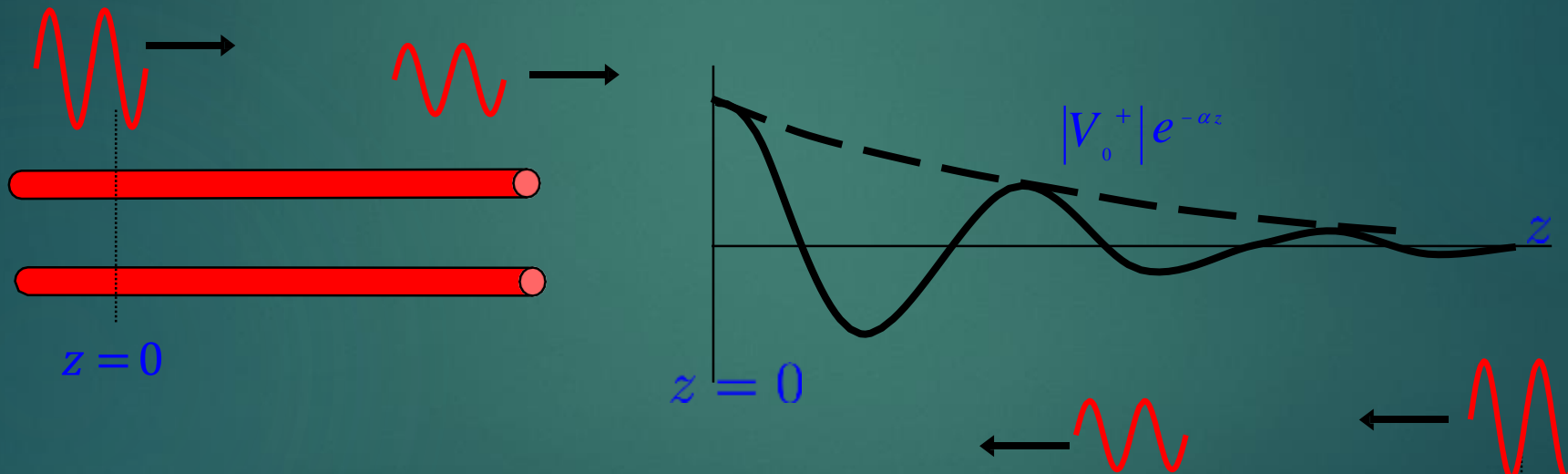



■ For -ve traveling wave:

$$v^-(z, t) = |V_o^-| e^{+\alpha z} \cos(\omega t + \beta z + \phi^-)$$

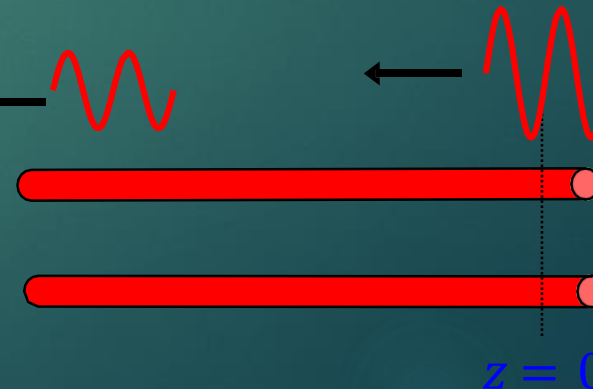

Wavelength (λ_g)

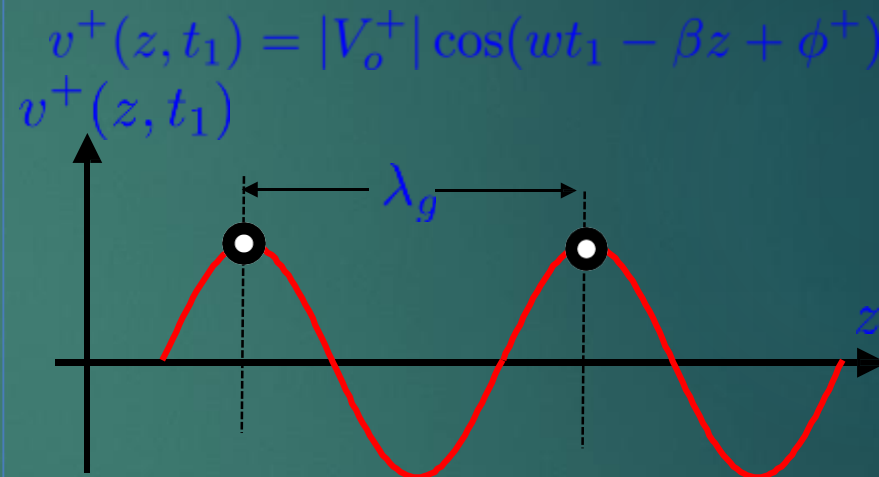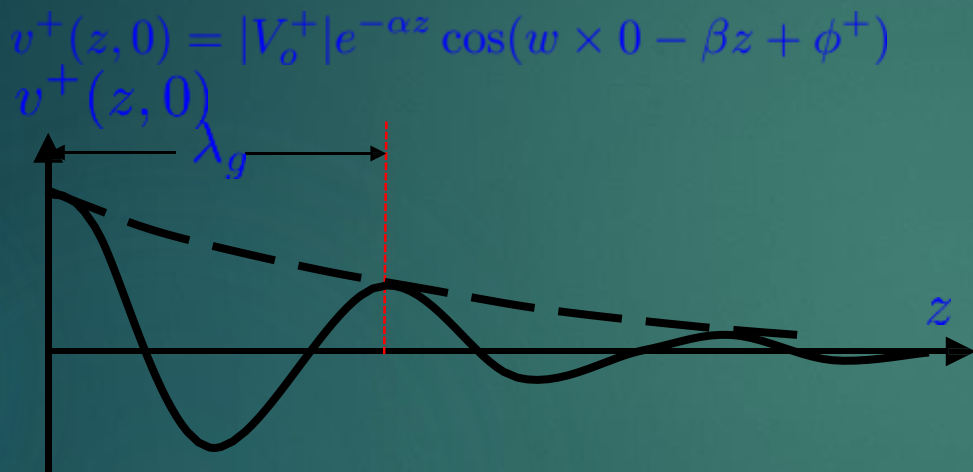- **The wavelength, λ_g** :- the distance between two successive maxima (or minima, or any other reference points) on the wave at a fixed instant of time.



■ Thus,

$$(\cancel{\omega t_1} - \cancel{\beta z} + \cancel{\phi^+}) - [\cancel{\omega t_1} - \beta(z + \lambda_g) + \cancel{\phi^+}] = 2\pi$$

■ The wave “repeats” when: $\beta \lambda_g = 2\pi$


■ Hence:

$$\lambda_g = \frac{2\pi}{\beta}$$

Phase Velocity (v_p)

- Phase velocity v_p : velocity at which a fixed phase point on the wave travels.

$$v^+(z, 0) = |V_o^+|e^{-\alpha z} \cos(\omega t - \beta z + \phi^+)$$

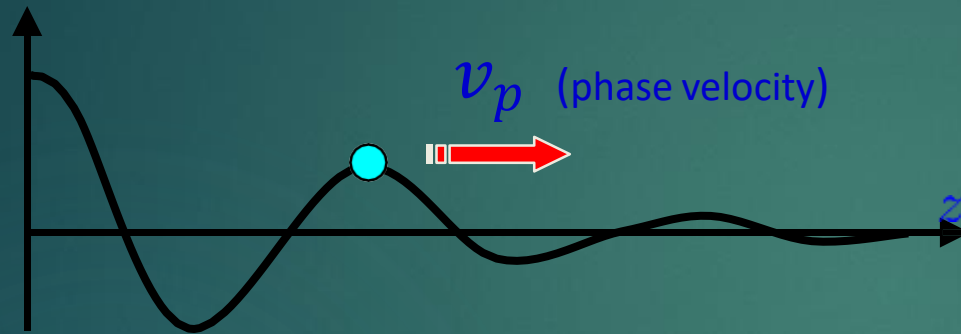

- Consider **“riding”** one part of the wave

$$\omega t - \beta z = \text{constant (choose 0)} \quad \Rightarrow \quad z = \frac{\omega t}{\beta}$$

- Phase velocity** calculation

$$\frac{dz}{dt} = \frac{d}{dt} \left(\frac{\omega t}{\beta} \right) = \frac{\omega}{\beta}$$

In expanded form:

$$v_p = \frac{\omega}{\text{Im}\{\sqrt{(R' + j\omega L')(G' + j\omega C')}\}}$$


- Hence $v_p = \frac{\omega}{\beta}$

Wave Motion

$$v^+(z, t) = |V_o^+| \cos(\omega t - \beta z + \phi^+) = |V_o^+| \cos \left(\omega \left(t - \frac{\beta}{\omega} z \right) + \phi^+ \right) \quad v_p = \frac{\omega}{\beta}$$

$$v^+(z, t) = f \left(t - \frac{z}{v_p} \right)$$

Let $v_p = 1$ m/s

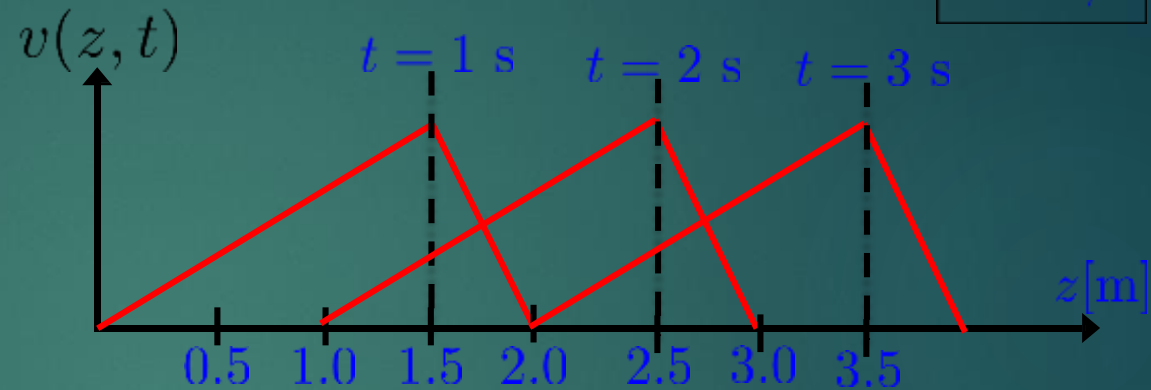

At $t = 1$ s, focus on the peak located at $z = 1.5$ m

$$\Rightarrow S_+ = t - \frac{z}{v_p} = 1 - \frac{1.5}{1} = -0.5$$

The argument S_+ stays constant for varying t & $z \Rightarrow$ **at $t = 2$ s**, for example:

$$S_+ = -0.5 = t - \frac{z}{v_p} = 2 - \frac{z}{1} \Rightarrow z = 2.5 \text{ m.}$$


So, the peak has now moved to position $z = 2.5$ m at $t = 2$ s.

Likewise, every point on this function moves the same distance (1 m) in this time (1 s). \Rightarrow This is called **wave motion**.

The speed of this movement is: $\frac{\Delta z}{\Delta t} = \frac{1}{1} = 1 \text{ m s} = v_p$



Characteristic Impedance (Z_0)

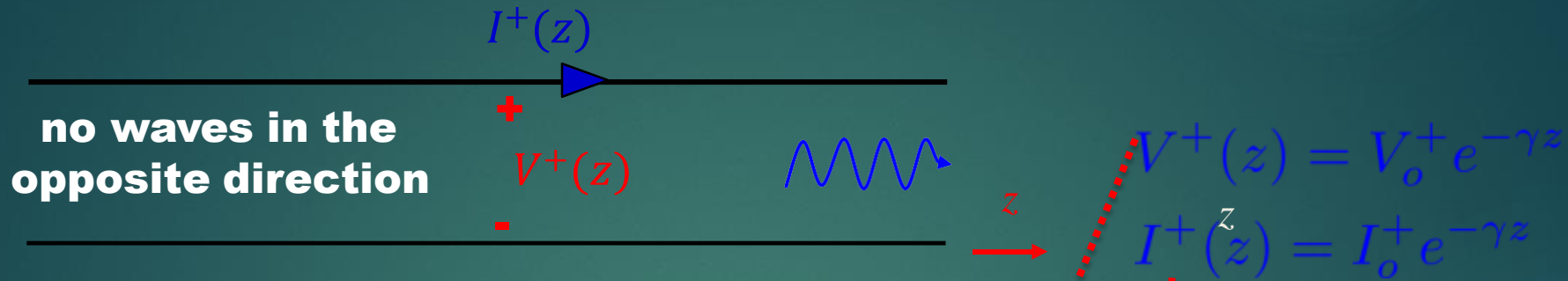

A wave is traveling in the **+Z** direction.

$$Z_0 \equiv \frac{V^+(z)}{I^+(z)} = \frac{V_0^+ e^{-\gamma z}}{I_0^+ e^{-\gamma z}} = \frac{V_0^+}{I_0^+}$$

(Note: Z_0 is a number, not a function of z)

Use Telegrapher's Equation:

$$\frac{\partial v}{\partial z} = -R' i - L' \frac{\partial i}{\partial t} \Rightarrow \frac{dV}{dz} = -R' I - j\omega L' I$$


Hence:

$$-\gamma V_0^+ e^{-\gamma z} = -(R' + j\omega L') I_0^+ e^{-\gamma z}$$

From this we have:

$$Z_0 = \frac{V_0^+}{I_0^+} = \frac{R' + j\omega L'}{\gamma} = \sqrt{\frac{R' + j\omega L'}{G' + j\omega C'}}$$

Z_0 for Backward-Traveling Wave

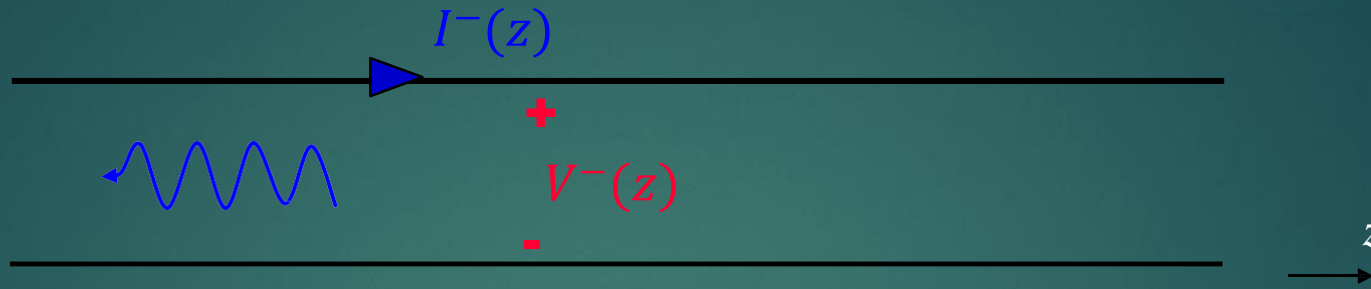


A wave is traveling in the **$-z$ direction**.

$$Z_0 = \frac{V^-(z)}{-I^-(z)} \quad \text{so} \quad \frac{V^-(z)}{I^-(z)} = -Z_0$$

Note: The reference directions for voltage and current are the same as for the forward wave.



General Case

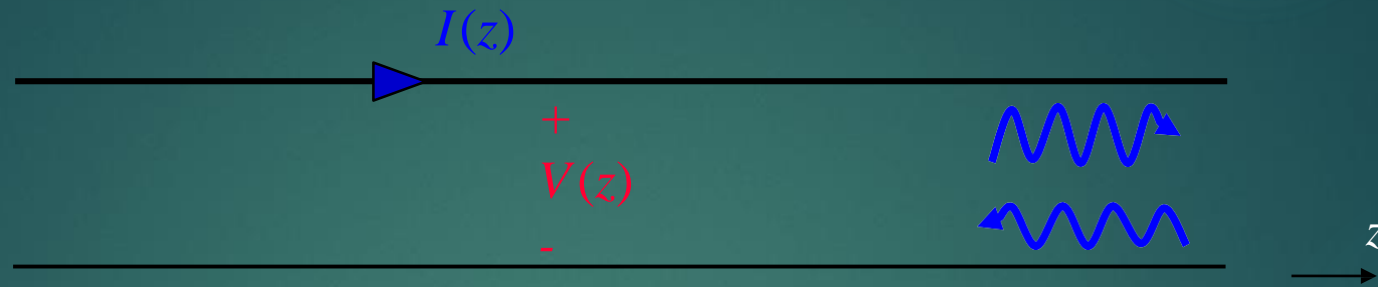


Most general case: A general superposition of forward and backward traveling waves:

$$V(z) = V_o^+ e^{-\gamma z} + V_o^- e^{+\gamma z}$$

$$I(z) = \frac{1}{Z_0} [V_o^+ e^{-\gamma z} - V_o^- e^{+\gamma z}]$$

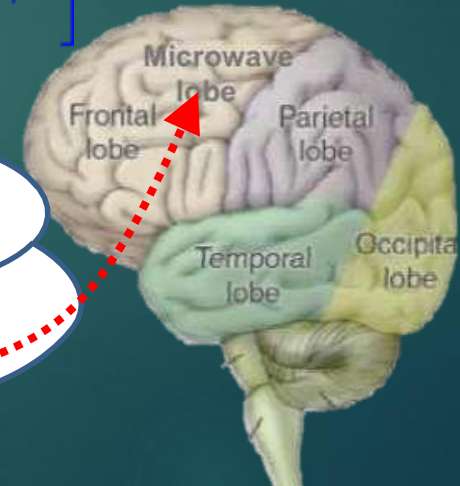Both of these equations should be committed to memory. They are the general form of **phasor voltages** and **currents** on TLs



50 Ohm T-Lines!!

In most RF systems,

$$Z_0 = 50 \Omega$$

WHY???



The Lossless T-Line

- Set $R' = G' = 0$

$$\begin{aligned}\gamma = \alpha + j\beta &= \sqrt{\cancel{(R' + j\omega L')}\cancel{(G' + j\omega C')}} \\ &= j\omega\sqrt{L'C'} = j\beta\end{aligned}$$

- So $\alpha = 0$ and $\beta = \omega\sqrt{L'C'}$

$$Z_0 = \sqrt{\frac{\cancel{R' + j\omega L'}}{\cancel{G' + j\omega C'}}$$



$$Z_0 = \sqrt{\frac{L'}{C'}}$$

real and independent of frequency

$$v_p = \frac{\omega}{\beta}$$



$$v_p = \frac{1}{\sqrt{L'C'}}$$

Independent of f

- If the medium between the two conductors is homogeneous (uniform) and is characterized by (μ, ϵ) , then we have that:

$$L'C' = \mu\epsilon \Rightarrow v_p = \frac{1}{\sqrt{\mu\epsilon}}$$

it is always the speed of light (in the material).




Generality of T-Line Theory

$$R_s = \sqrt{\pi f \mu_c / \sigma_c}$$

$$\epsilon = \epsilon' - j\epsilon''$$

$$= \epsilon_o \epsilon_r (1 - j \tan \delta)$$
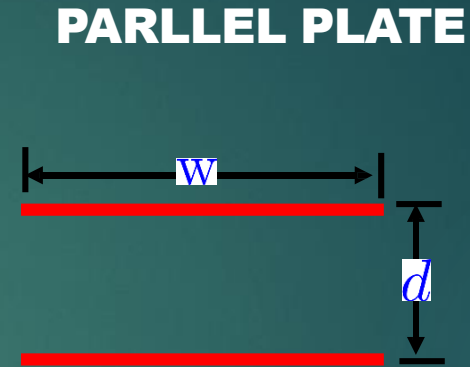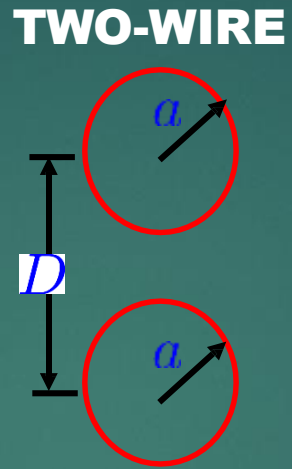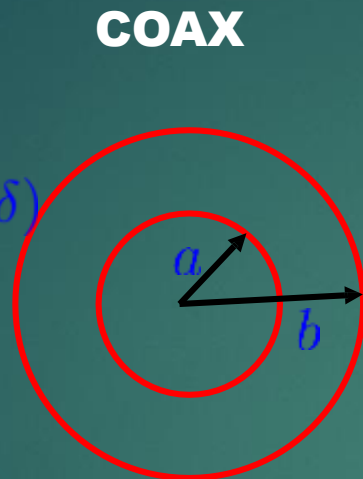
$$\delta = \sqrt{\frac{2}{\omega \mu \sigma}}$$




L'	$\frac{\mu}{2\pi} \ln \frac{b}{a}$	$\frac{\mu}{\pi} \cosh^{-1} \left(\frac{D}{2a} \right)$	$\frac{\mu d}{w}$	H/m
C'	$\frac{2\pi\epsilon'}{\ln(b/a)}$	$\frac{\pi\epsilon'}{\cosh^{-1}(D/2a)}$	$\frac{\epsilon' w}{d}$	F/m
R'	$\frac{R_s}{2\pi} \left(\frac{1}{a} + \frac{1}{b} \right)$	$\frac{R_s}{\pi a}$	$\frac{2R_s}{w}$	Ω/m
G'	$\frac{2\pi\omega\epsilon''}{\ln(b/a)}$	$\frac{\pi\omega\epsilon''}{\cosh^{-1}(D/2a)}$	$\frac{\omega\epsilon'' w}{d}$	S/m

Terminated T-Line-I


$$V(z) = V_o^+ e^{-\gamma z} + V_o^- e^{+\gamma z}$$
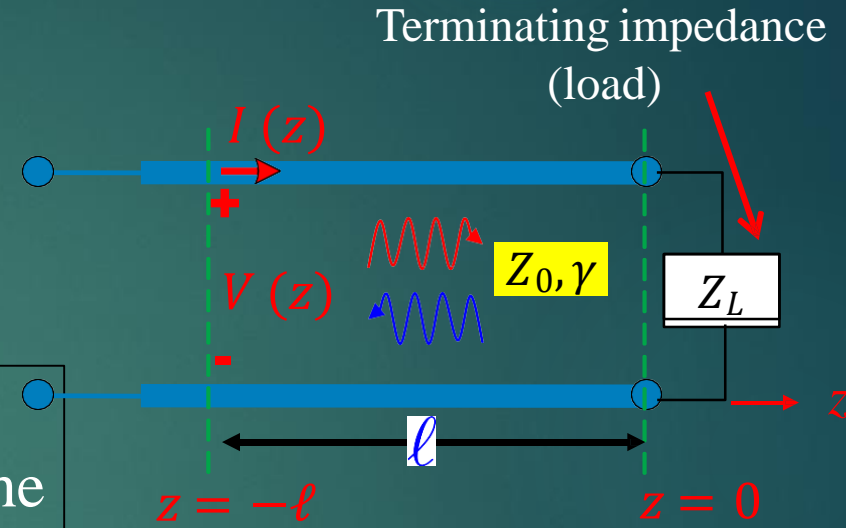
$$I(z) = \frac{1}{Z_0} [V_o^+ e^{-\gamma z} - V_o^- e^{+\gamma z}]$$




Where do we assign $z = 0$?

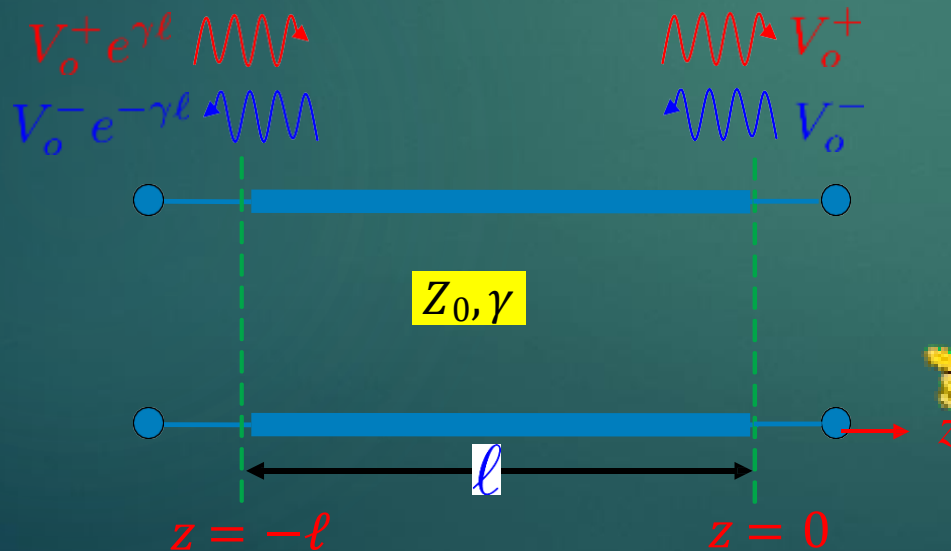For mathematical convenience, the usual choice is at the load, i.e., $z = 0$.



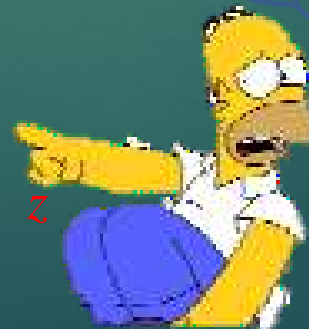Note: The length ℓ measures distance from the load: $\ell = -z$



Terminated T-Line-II

- The “lumped load” Z_L that terminates the TL is considered a **boundary condition** for the voltage and current:

$$V(z = 0) = I(z = 0)Z_L \quad \Rightarrow \quad Z_L = \frac{V(0)}{I(0)}$$


- Apply this boundary condition as:

$$V(z = 0) = V_o^+ + V_o^-$$

$$I(z = 0) = \frac{1}{Z_0} (V_o^+ - V_o^-)$$


- Hence
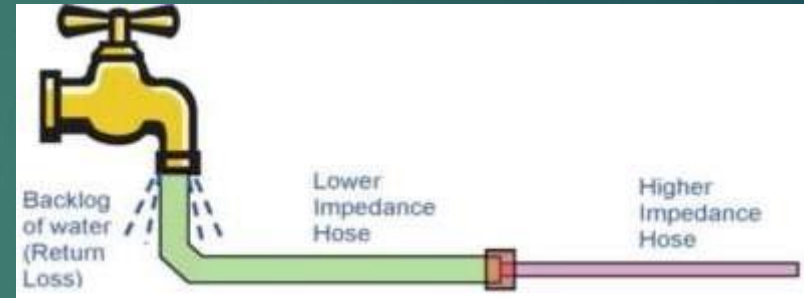
$$\frac{V(0)}{I(0)} = \frac{V_o^+ + V_o^-}{V_o^+ - V_o^-} Z_0 = Z_L$$



- Solving for V_o^-/V_o^+ , and defining this ratio as the **voltage reflection coefficient at the load** ($z = 0$), we find

complex number

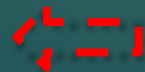

$$\Gamma_L \equiv \left. \frac{V_o^-}{V_o^+} \right|_{z=0} = \frac{Z_L - Z_0}{Z_L + Z_0}$$



Z_{in} of a T-Line-I


$$\therefore V(z) = V_o^+ e^{-\gamma z} + V_o^- e^{+\gamma z}$$

$\ell \equiv$ distance away from load

$$\begin{aligned} V(-\ell) &= V_o^+ e^{+\gamma \ell} + V_o^- e^{-\gamma \ell} \\ &= V_o^+ e^{+\gamma \ell} \left(1 + \frac{V_o^-}{V_o^+} e^{-2\gamma \ell} \right) \\ &= V_o^+ e^{+\gamma \ell} (1 + \Gamma_L e^{-2\gamma \ell}) \end{aligned}$$

Similarly, the current at $z = -\ell$
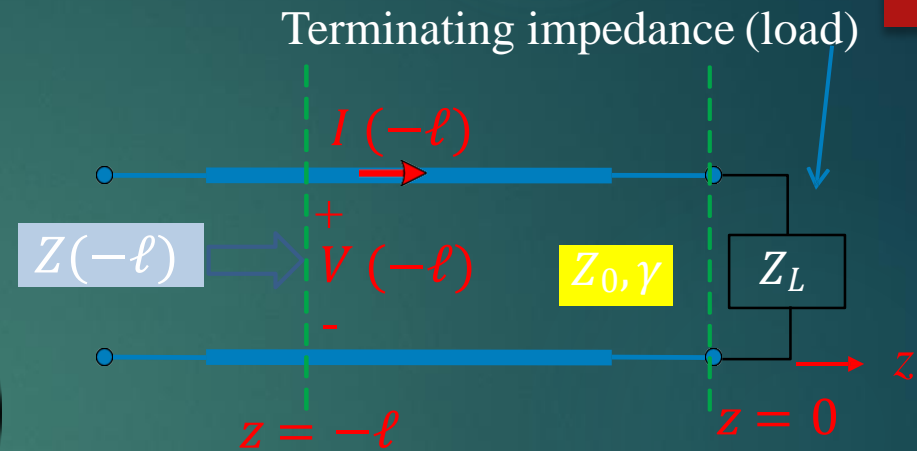
$$\begin{aligned} I(-\ell) &= \frac{1}{Z_0} [V_o^+ e^{+\gamma \ell} - V_o^- e^{-\gamma \ell}] \\ &= \frac{V_o^+}{Z_0} e^{+\gamma \ell} \left(1 - \frac{V_o^-}{V_o^+} e^{-2\gamma \ell} \right) \\ &= \frac{V_o^+}{Z_0} e^{+\gamma \ell} (1 - \Gamma_L e^{-2\gamma \ell}) \end{aligned}$$



Input impedance seen “looking” towards load at $z = -\ell$.

$$\begin{aligned} Z_{in} = Z(-\ell) &\equiv \frac{V(-\ell)}{I(-\ell)} \\ &= Z_0 \frac{1 + \Gamma_L e^{-2\gamma \ell}}{1 - \Gamma_L e^{-2\gamma \ell}} \end{aligned}$$

$Z(0) = ?$

Z_{in} of a T-Line-II

■ Substituting for $\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0}$:

■ Thus,
$$Z(-\ell) = Z_0 \frac{1 + \left(\frac{Z_L - Z_0}{Z_L + Z_0}\right) e^{-2\gamma\ell}}{1 - \left(\frac{Z_L - Z_0}{Z_L + Z_0}\right) e^{-2\gamma\ell}} \times \frac{Z_L + Z_0}{Z_L + Z_0}$$

$$Z(-\ell) = Z_0 \frac{(Z_L + Z_0) + (Z_L - Z_0)e^{-2\gamma\ell}}{(Z_L + Z_0) - (Z_L - Z_0)e^{-2\gamma\ell}} \times \frac{e^{+\gamma\ell}}{e^{+\gamma\ell}}$$

$$= Z_0 \frac{(Z_L + Z_0)e^{+\gamma\ell} + (Z_L - Z_0)e^{-\gamma\ell}}{(Z_L + Z_0)e^{+\gamma\ell} - (Z_L - Z_0)e^{-\gamma\ell}}$$

$$= Z_0 \frac{Z_L(e^{+\gamma\ell} + e^{-\gamma\ell}) + Z_0(e^{+\gamma\ell} - e^{-\gamma\ell})}{Z_0(e^{+\gamma\ell} + e^{-\gamma\ell}) + Z_L(e^{+\gamma\ell} - e^{-\gamma\ell})}$$

Z_{in} of a T-Line-III

Using trigonometric identities:

$$\cosh x = \frac{1}{2} (e^x + e^{-x}) \quad \text{and} \quad \sinh x = \frac{1}{2} (e^x - e^{-x})$$

Hence, we have

$$Z(-\ell) = Z_0 \frac{Z_L \cosh(\gamma\ell) + Z_0 \sinh(\gamma\ell)}{Z_0 \cosh(\gamma\ell) + Z_L \sinh(\gamma\ell)}$$

Divide both the numerator and the denominator by $\cosh(\gamma\ell)$

$$Z_{in} = Z(-\ell) = Z_0 \frac{Z_L + Z_0 \tanh(\gamma\ell)}{Z_0 + Z_L \tanh(\gamma\ell)}$$



Input Impedance of a Lossless TL

$$\gamma = \cancel{\alpha} + j\beta = j\beta$$

$$V(-\ell) = V_0^+ e^{j\beta\ell} (1 + \Gamma_L e^{-2j\beta\ell})$$

$$I(-\ell) = \frac{V_0^+}{Z_0} e^{j\beta\ell} (1 - \Gamma_L e^{-2j\beta\ell})$$

$$Z(-\ell) = Z_0 \left(\frac{1 + \Gamma_L e^{-2j\beta\ell}}{1 - \Gamma_L e^{-2j\beta\ell}} \right)$$




$$Z_{\text{in}} = Z(-\ell) = Z_0 \frac{Z_L + jZ_0 \tan(\beta\ell)}{Z_0 + jZ_L \tan(\beta\ell)}$$



Note:
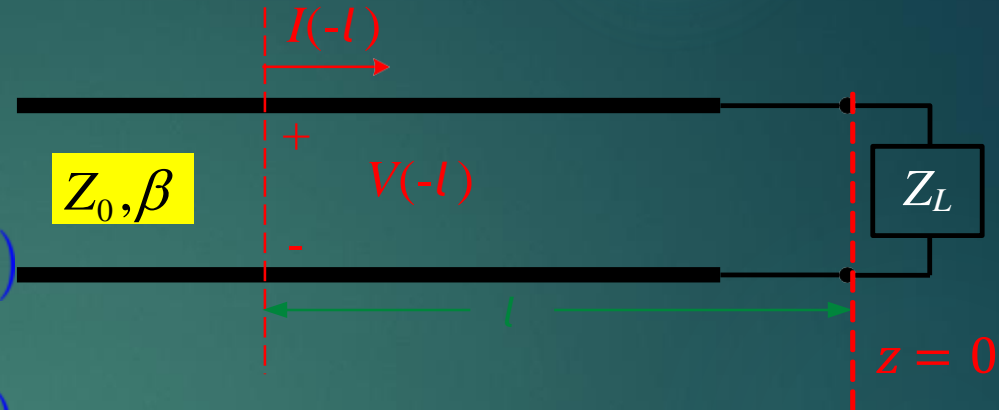
$$\tanh(\gamma\ell) = \tanh(j\beta\ell) = j \tan(\beta\ell)$$



tan repeats when


$$\beta\ell = \pi \Rightarrow \frac{2\pi}{\lambda_g} \ell = \pi$$

$$\Rightarrow \ell = \lambda_g/2$$

Impedance is periodic with period $\lambda_g/2$



Matched Load ($Z_L = Z_0$)

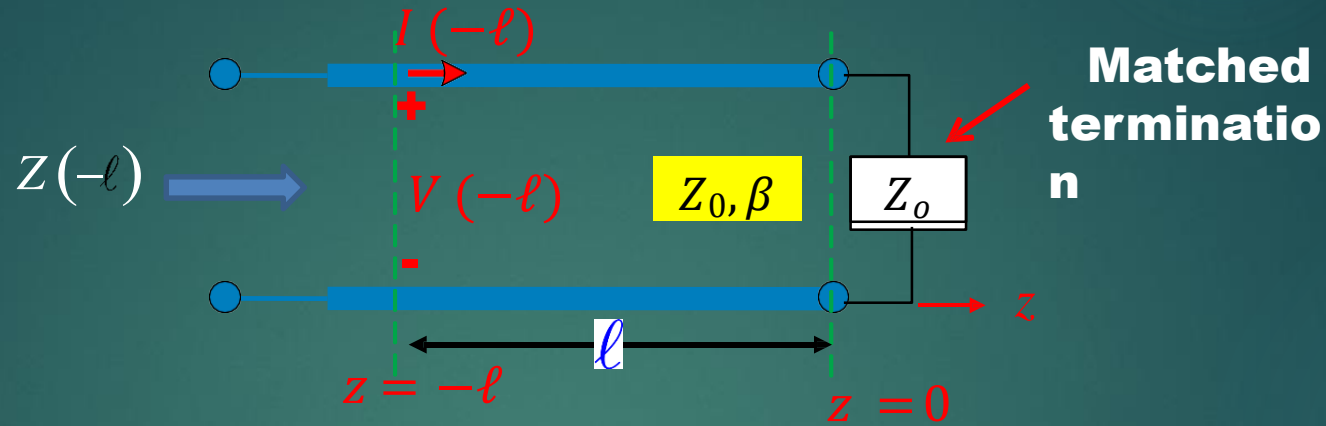

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} = 0 \quad \leftarrow \text{No reflection from the load}$$

$$\Rightarrow V(-l) = V_0^+ e^{j\beta l} (1 + \Gamma_L e^{-2j\beta l}) = V_0^+ e^{j\beta l}$$

$$I(-l) = \frac{V_0^+}{Z_0} e^{j\beta l} (1 - \Gamma_L e^{-2j\beta l}) = \frac{V_0^+}{Z_0} e^{j\beta l}$$

$$Z(-l) = \frac{V(-l)}{I(-l)} = Z_0$$

$$Z_{\text{in}} = Z_0 \quad [\Omega]$$

The input impedance is Z_0 regardless of the length of the TL.

Short-Circuit Load ($Z_L = 0$)

$$\Gamma_L = \frac{0 - Z_0}{0 + Z_0} = -1$$

$$\Rightarrow Z(-\ell) = Z_0 \frac{Z_L + jZ_0 \tan(\beta\ell)}{Z_0 + jZ_L \tan(\beta\ell)}$$

$$= jZ_0 \tan(\beta\ell)$$


Always imaginary!



$$\Rightarrow Z(-\ell) = jX_{SC}$$


$$\therefore X_{SC} = Z_0 \tan(\beta\ell)$$

$$Z_{in} \Big|_{Z_L=0} = jZ_0 \tan(\beta\ell) \quad [\Omega]$$

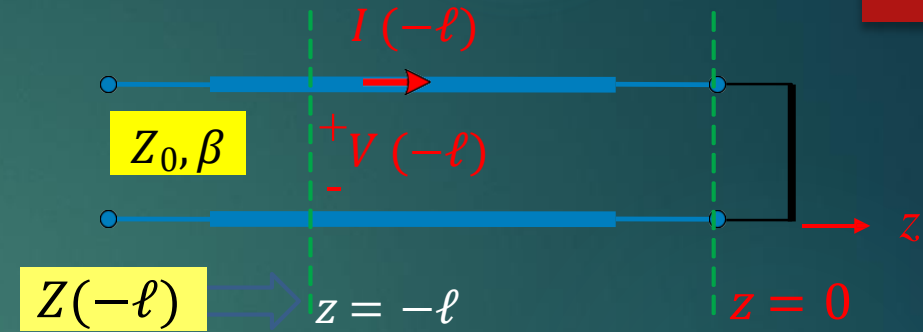

Note:
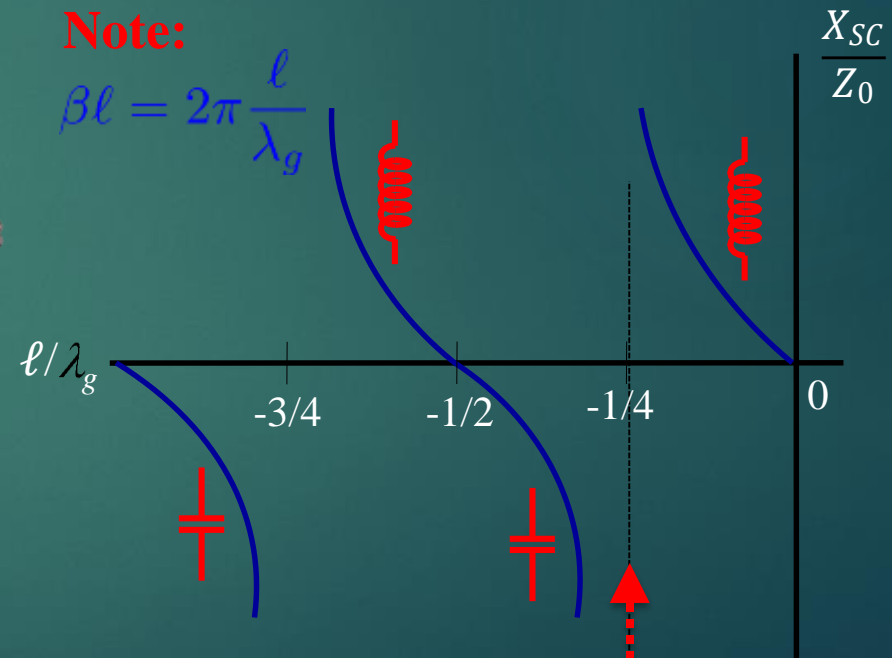
$$\beta\ell = 2\pi \frac{\ell}{\lambda_g}$$



S.C. can become an O.C. with a $\lambda_g/4$ TL

Open-Circuit Load ($Z_L = \infty$)

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{1 - \cancel{(Z_0/Z_L)}}{1 + \cancel{(Z_0/Z_L)}} = +1$$



$$\begin{aligned} Z(-\ell) &= Z_0 \frac{Z_L + jZ_0 \tan(\beta\ell)}{Z_0 + jZ_L \tan(\beta\ell)} \\ &= Z_0 \frac{1 + j\cancel{(Z_0/Z_L)} \tan(\beta\ell)}{\cancel{(Z_0/Z_L)} + j \tan(\beta\ell)} \\ &= -jZ_0 \cot(\beta\ell) \end{aligned}$$

Always imaginary!



Note: $Z(-\ell) = jX_{OC}$
 $\Rightarrow X_{OC} = -Z_0 \cot(\beta\ell)$

$$Z_{in} \Big|_{Z_L=\infty} = -jZ_0 \cot(\beta\ell) \quad [\Omega]$$

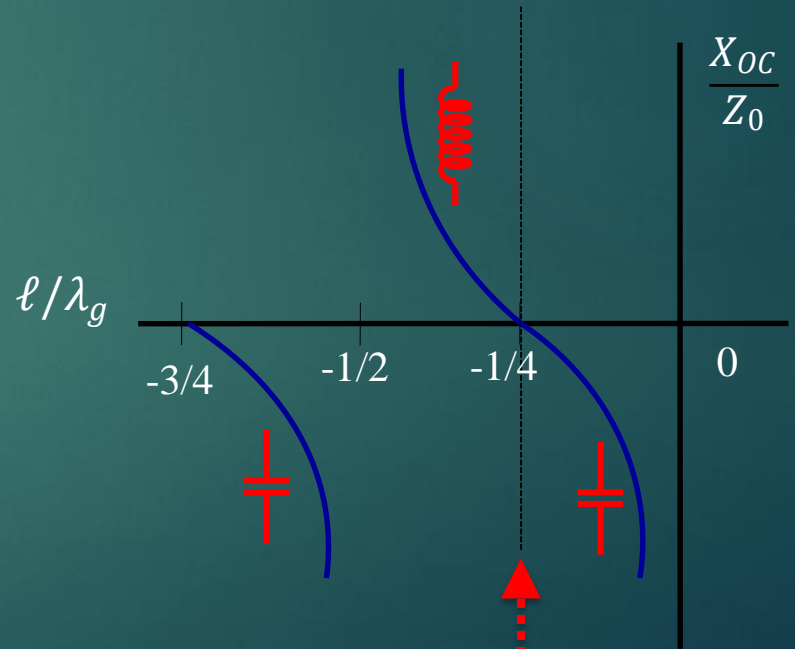
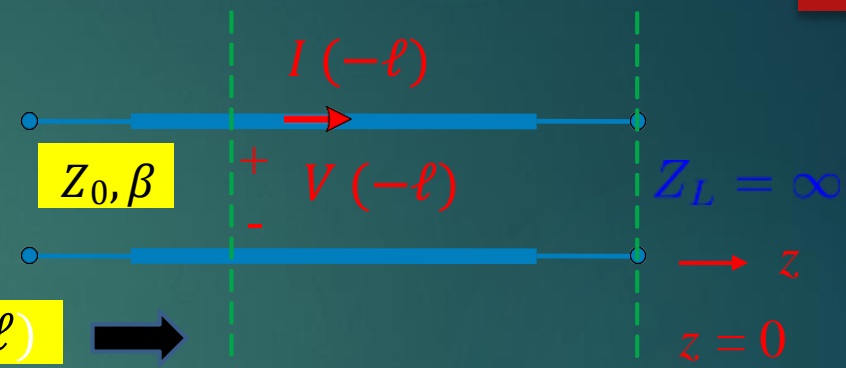


O.C. can become a S.C. with a $\lambda_g/4$ transmission line.



Using TLs to Synthesize Elements

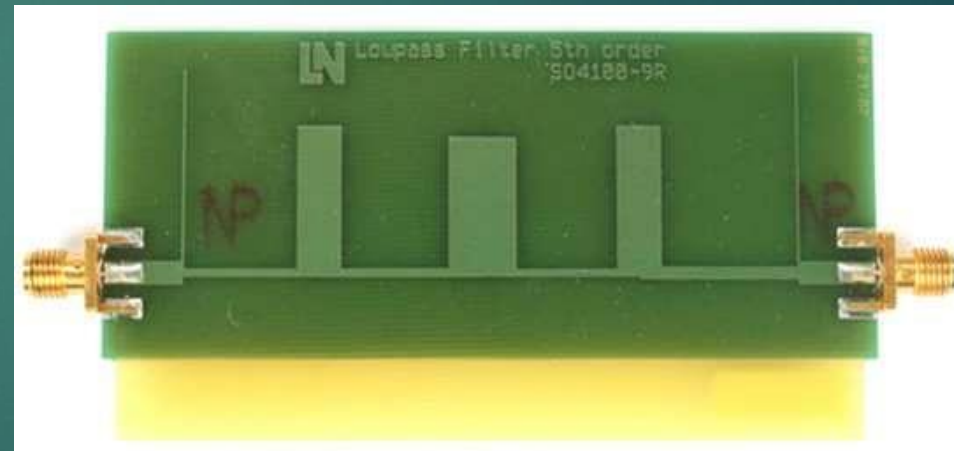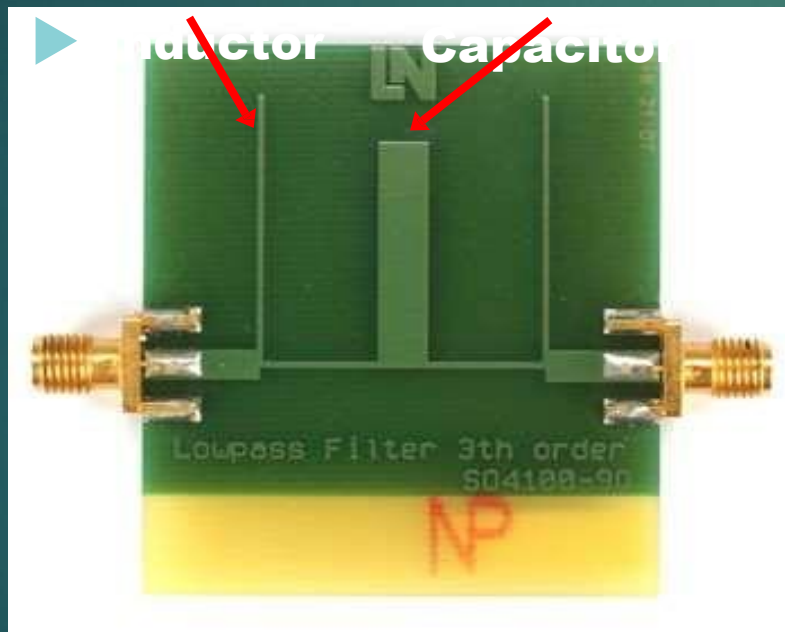- ▶ We can obtain any reactance that we want from a short or open TL.
- ▶ This is very useful in microwave engineering.



A microwave filter constructed from microstrip.

Thank you Very Much !!!