



Daffodil International University (DIU)
Department of Electrical and Electronic Engineering

EEE 422: Measurement and Instrumentation Lab

EXPERIMENT NO: 06

NAME OF THE EXPERIMENT: STUDY OF INSTRUMENTATION AMPLIFIER

Theory:

The instrumentation is one of the most useful, precise, versatile amplifiers available today. It is made from three Op-Amps and seven resistors. It is actually made by connecting buffer amplifier to differential amplifier. Op-Amp A3 and its four equal resistors R from a differential amplifier with gain 1. Only the A3 resistor have to be matched. The primed resistor R' can be made variable to balance out any common mode voltage as shown in figure. The resistor aR is used to set the gain according to the following equation where $a = aR/R$.

$$V_0 / (E_1 - E_2) = 1 + (2/a)$$

Circuit Diagram:

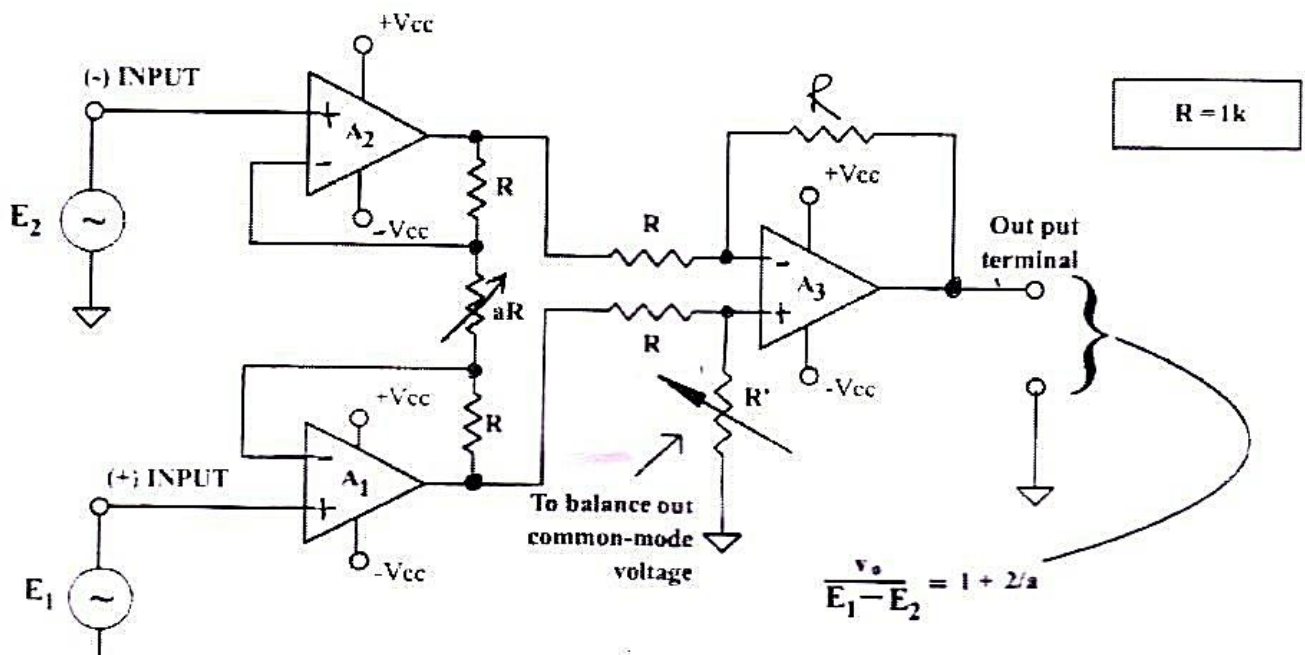


Fig.1: Instrumentation Amplifier

Apparatus:

1. IC 741 3 pcs
2. Resistors 1k-5 pcs
3. Pot 1k- 2 pcs
4. Trainer Board
5. Oscilloscope
6. Signal Generator

Procedure:

1. Connect the circuit as above. Use $R=1K$
2. Connect E2 to ground and provide a 5v P-P voltage at E1.
3. Calculate a for a gain of 2.
4. Operate the aR pot again to get a gain of 2.
5. Draw the voltage wave shape at the output of the three Op-amps.
6. Compare the two values of a .

Report:

1. Describe the operation of the circuit and theoretically prove the equation of the instrumentation amplifier as given in the instruction.
2. Why it is a kind of a differential amplifier and how could we use it as an amplifier?
3. What is the advantage of instrumentation amplifier?

