


18/02/2021
L3T2 - B(E)

Node/Bus elimination by Matrix Algebra.

Matrix partitioning

node/junction
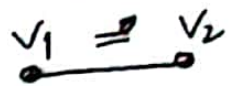
$$\text{Let, } A = \begin{bmatrix} a_{11} & a_{12} & a_{13} \\ a_{21} & a_{22} & a_{23} \\ a_{31} & a_{32} & a_{33} \end{bmatrix} = \begin{bmatrix} E & F \\ G & H \end{bmatrix}$$



$$\text{Where, } E = \begin{bmatrix} a_{11} & a_{12} \\ a_{21} & a_{22} \end{bmatrix}, \quad F = \begin{bmatrix} a_{13} \\ a_{23} \end{bmatrix}$$

$$G = \begin{bmatrix} a_{31} & a_{32} \end{bmatrix}, \quad H = \begin{bmatrix} a_{33} \end{bmatrix}$$

$$\text{and, } B = \begin{bmatrix} b_{11} \\ b_{21} \\ b_{31} \end{bmatrix} = \begin{bmatrix} Q \\ R \end{bmatrix}$$

$$\text{Then, } C = \underline{A \times B} = \begin{bmatrix} E & F \\ G & H \end{bmatrix} \times \begin{bmatrix} Q \\ R \end{bmatrix} = \begin{bmatrix} EQ + FR \\ GQ + HR \end{bmatrix}$$

Node/Bus current in matrix form.

$$\underline{I}_{BUS} = \underline{Y}_{BUS} \cdot \underline{V}_{BUS}$$

I_{BUS}, V_{BUS} - Column mat
 Y_{BUS} - Sym. Square mat

$$\begin{bmatrix} I_A \\ I_X \end{bmatrix} = \begin{bmatrix} K & L \\ L^T & M \end{bmatrix} \begin{bmatrix} V_A \\ V_X \end{bmatrix}$$

I_A, V_A - current/voltages need to retain ($I_A \neq 0$)
 I_X, V_X - current/voltages need to eliminate ($I_X = 0$)

After multiplication,

$$I_A = KV_A + LV_X \quad \text{--- (1)}$$

$$\text{and } I_X = L^T V_A + M V_X \quad \text{--- (2)}$$

From eqⁿ ②, we get, (since all elements of I_x are equal to zero)

$$I_x = 0 = L^T V_A + M V_x$$
$$\Rightarrow V_x = - \frac{L^T V_A}{M} = - L^T V_A \cdot M^{-1}$$

Substituting the value of V_x in eqⁿ ①

$$I_A = K V_A + L V_x$$
$$= K V_A + L \cdot (-L^T V_A \cdot M^{-1})$$
$$\Rightarrow \underline{I_A} = \underline{\frac{K - L \cdot M^{-1} \cdot L^T}{R}} V_A$$


After eliminating bus(es)/node(s), we have

$$\underline{Y_{Bus, new}} = \underline{K - L M^{-1} L^T}$$


$$Y_{Bus} = \begin{bmatrix} K \\ \hline L \end{bmatrix}$$

Stevenson Jr

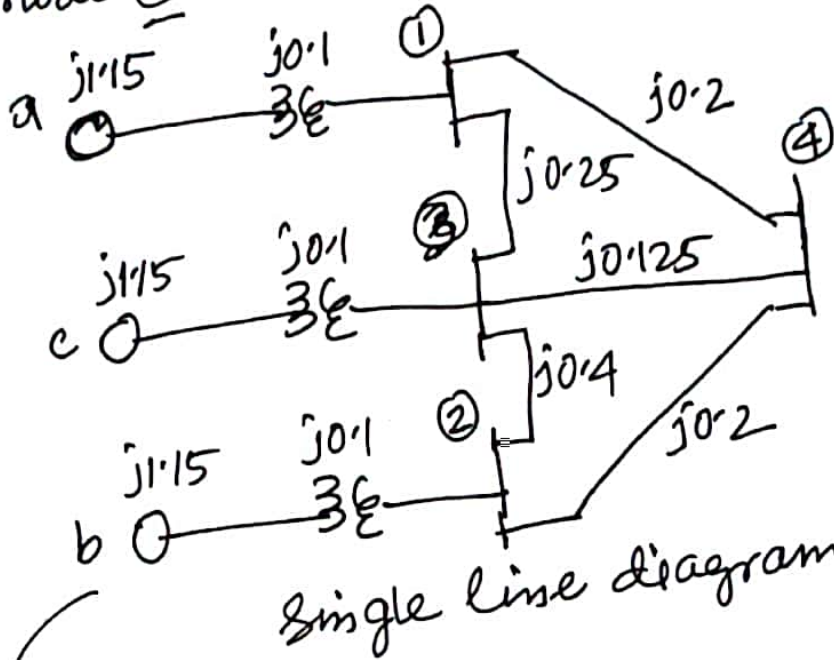
7.3 If the generator and transformer at bus ③ are removed from the circuit, eliminate node ③ and ④ by matrix algebra procedure.



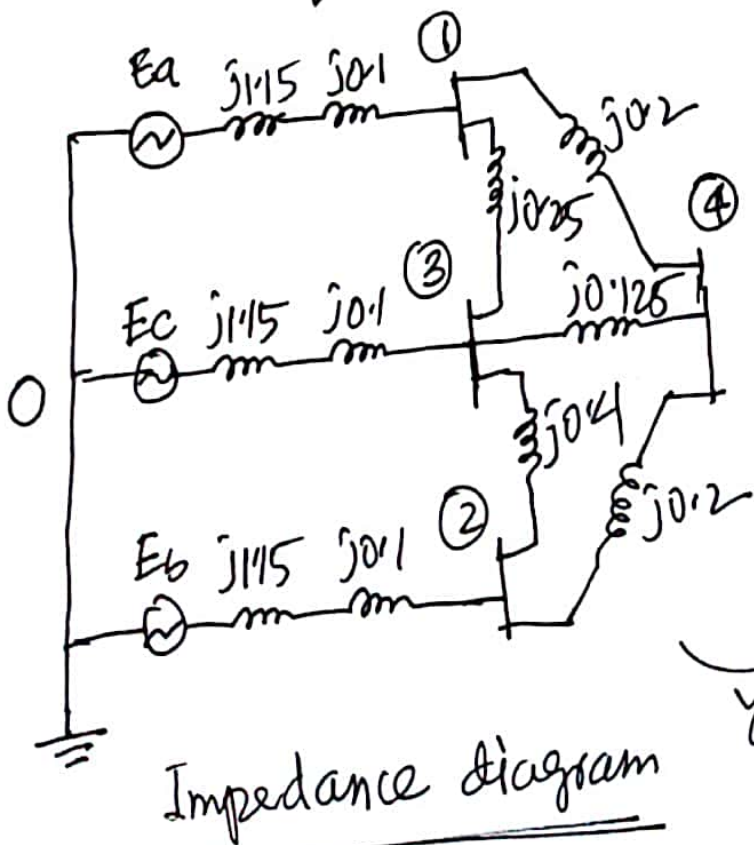$E_a = E_c = 1.5 \angle 0$
 $E_b = 1.5 \angle -36.87^\circ$



$Y = \frac{1}{Z}$

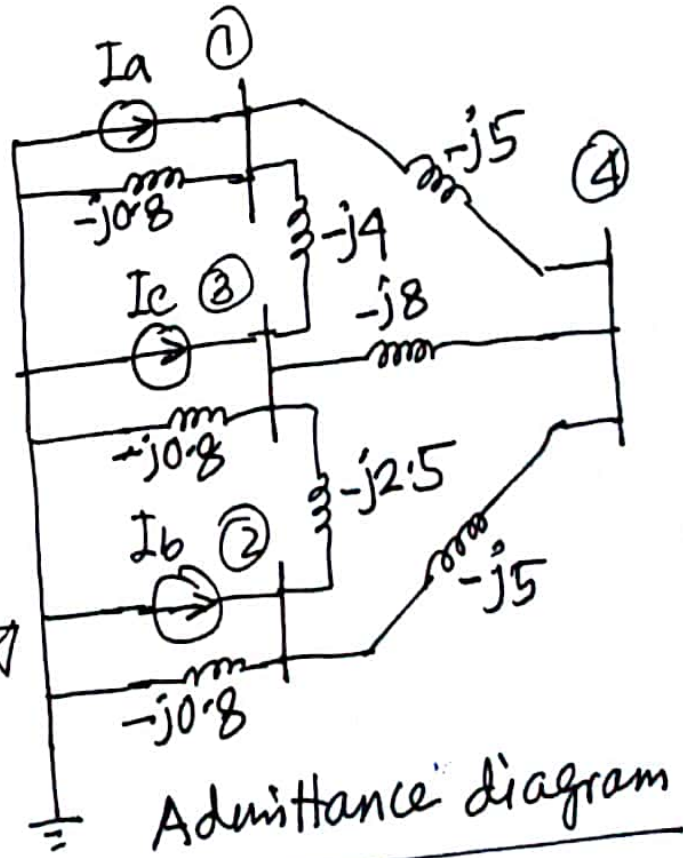

without
After removing generator and transformer from bus ③
we get,

$$Y_{BUS} = \begin{bmatrix} -j9.8 & 0 & j4 & j5 \\ 0 & -j8.3 & j2.5 & j5 \\ j4 & j2.5 & -j15.3 & j8 \\ j5 & j5 & j8 & -j18 \end{bmatrix}$$

After removing generator and transformer at bus ③

$$Y_{BUS} = \begin{bmatrix} -j9.8 & 0 & j4 & j5 \\ 0 & -j8.3 & j2.5 & j5 \\ r3 & j4 & j2.5 & -j14.5 & j8 \\ r4 & j5 & j5 & j8 & -j18 \end{bmatrix} = \begin{bmatrix} K & L \\ LT & M \end{bmatrix}$$

After eliminating node ③ and ④

$$Y_{BUS}(new) = K - LM^{-1}LT$$

Here, $M = \begin{bmatrix} -j14.5 & j8 \\ j8 & -j18 \end{bmatrix}$

Then, $M^{-1} = \frac{1}{|M|} \times \text{Adj}(M)$

$$= \frac{1}{(-j14.5 \times -j18) - j8 \times j8} \times \begin{bmatrix} -j18 & -j8 \\ -j8 & -j14.5 \end{bmatrix}$$

$$= \frac{1}{-261 - (-64)} \times \begin{bmatrix} -j18 & -j8 \\ -j8 & -j14.5 \end{bmatrix}$$

$$A = \begin{vmatrix} a & b \\ c & d \end{vmatrix}$$

$$A^{-1} = \frac{1}{|A|} \times \text{Adj}(A)$$

$$= \frac{1}{ad-bc} \times \begin{bmatrix} d & -b \\ -c & a \end{bmatrix}$$

$$\Rightarrow M^{-1} = \frac{1}{-197} \begin{bmatrix} -j18 & -j8 \\ -j8 & -j14.5 \end{bmatrix} = \begin{bmatrix} j0.0914 & j0.0406 \\ j0.0406 & j0.0736 \end{bmatrix}$$

Again,

$$LM^{-1}L^T$$

$$= \begin{bmatrix} j4 & j5 \\ j2.5 & j5 \end{bmatrix} \times \begin{bmatrix} j0.0914 & j0.0406 \\ j0.0406 & j0.0736 \end{bmatrix} \\ \times \begin{bmatrix} j4 & j2.5 \\ j5 & j5 \end{bmatrix}$$

$$M^{-1} = \frac{1}{M} \\ = \frac{1}{j} \begin{bmatrix} -14.5 & 8 \\ 8 & -18 \end{bmatrix} \\ = -j \begin{bmatrix} -0.091 & -0.04 \\ -0.04 & -0.073 \end{bmatrix}$$

Calculator

$$= (j \times j \times j) \times \begin{bmatrix} 4 & 5 \\ 2.5 & 5 \end{bmatrix} \begin{bmatrix} 0.0914 & 0.0406 \\ 0.0406 & 0.0736 \end{bmatrix} \begin{bmatrix} 4 & 2.5 \\ 5 & 5 \end{bmatrix}$$

MATA MATB MATC

$$= -j \times \begin{bmatrix} 4.9264 & 4.0735 \\ 4.0735 & 3.4262 \end{bmatrix}$$

$$= \begin{bmatrix} -j4.9264 & -j4.0735 \\ -j4.0735 & -j3.4262 \end{bmatrix}$$

After eliminating node ③ and ④, we get

$$Y_{bus}(new) = K - LM^{-1}L^T$$

$$= \begin{bmatrix} -j9.8 & 0 \\ 0 & -j8.3 \end{bmatrix} - \begin{bmatrix} -j4.9264 & -j4.0735 \\ -j4.0735 & -j3.4262 \end{bmatrix}$$

$$= \begin{bmatrix} -j4.8736 & j4.0735 \\ j4.0735 & -j4.8738 \end{bmatrix}$$

$$= \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix}$$

Admittance between bus ① and ② -

$$y_{12} = -Y_{12} = -Y_{21} = -j4.0735 \text{ pu}$$

$$\left(\begin{array}{l} Y_{12} = -Y_{21} \\ = Y_{21} \end{array} \right)$$

Admittance between bus ① and ground

$$y_{10} = Y_{11} - Y_{12} = -j4.8736 - (-j4.0735)$$

$$= -j0.8001 \text{ pu}$$

$$\left(Y_{11} = \underbrace{Y_{10}} + Y_{12} \right)$$


Admittance between bus ② and ground

$$y_{20} = Y_{22} - Y_{21} = -j4.8738 - (-j4.0735)$$

$$= -j0.8003 \text{ pu.}$$

$$\left(Y_{22} = Y_{20} + Y_{21} \right)$$

Admittance diagram

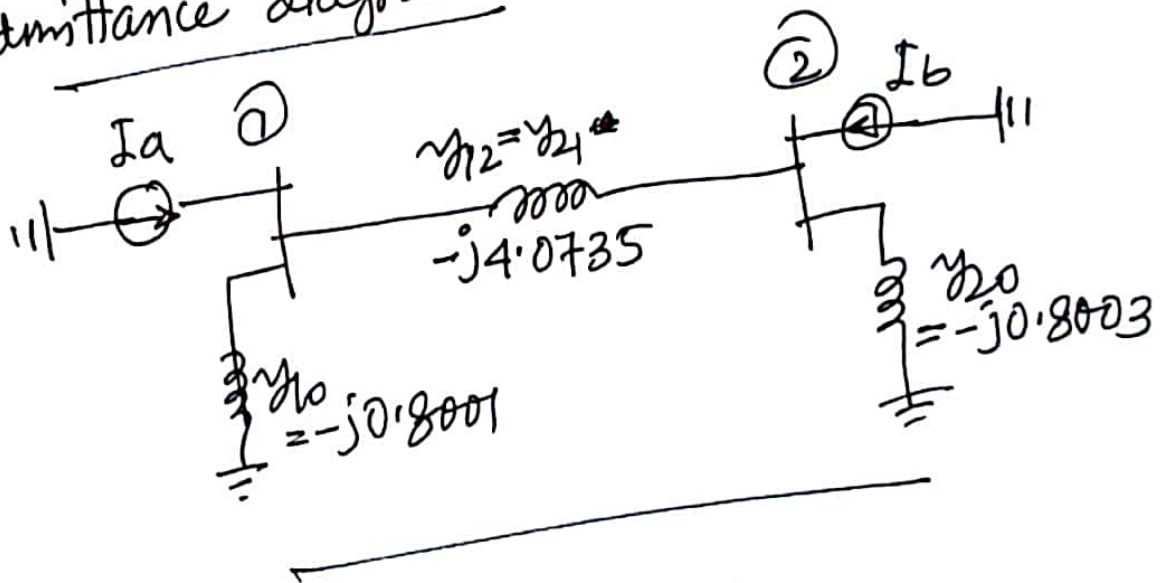

25/02/2021

L3T2 - B (E)


KRON method of node elimination

$$Y_{ij}^{(new)} = Y_{ij}^{(old)} - \left(\frac{Y_{in} Y_{nj}}{Y_{nn}} \right)_{(old)}$$

where, i, j - row, column
 n - node to be eliminated

So far
 4877
 4864

Example

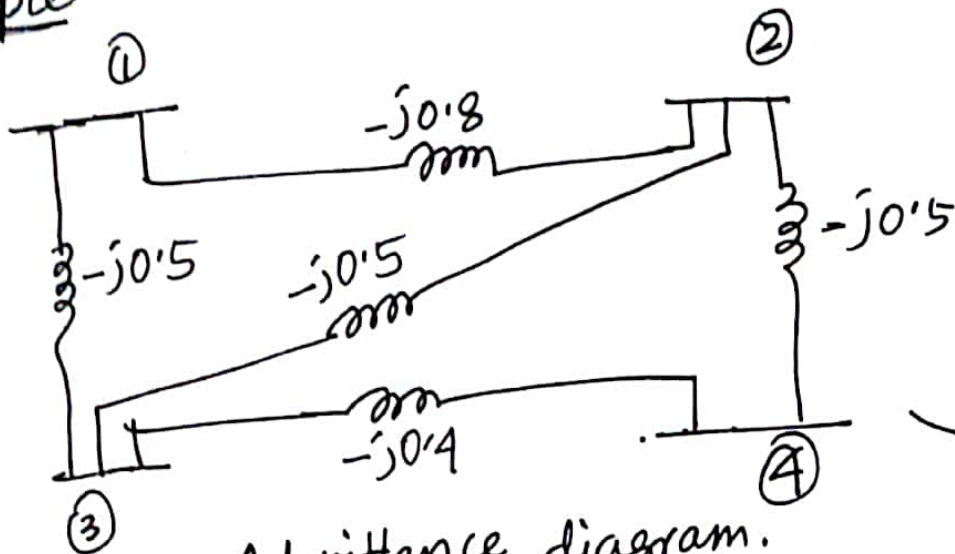

4891
 4871
 4860

Admittance diagram.



Eliminate node 4 from the network and find new bus admittance matrix.

Bus admittance matrix without eliminating node 4, we get

$$Y_{BUS} = \begin{bmatrix} -j1.3 & j0.8 & j0.5 & 0 \\ j0.8 & -j1.8 & j0.5 & j0.5 \\ j0.5 & j0.5 & -j1.4 & j0.4 \\ 0 & j0.5 & j0.4 & -j0.9 \end{bmatrix} \begin{matrix} \\ \\ \\ -r_4 \end{matrix}$$

Here, $n=4$:

$$i=1, j=1; \quad Y_{11}(\text{new}) = Y_{11}(\text{old}) - \left(\frac{Y_{14} Y_{41}}{Y_{44}} \right)_{\text{old}} \\ = -j1.3 - \frac{0 \times 0}{-j0.9} = -j1.3 \quad \text{pu} \quad \begin{array}{r} 4890 \\ 4862 \\ \hline 4890 \\ 4873 \end{array}$$

$$i=2, j=2; \quad Y_{22}(\text{new}) = Y_{22}(\text{old}) - \left(\frac{Y_{24} Y_{42}}{Y_{44}} \right)_{\text{old}} \\ = -j1.8 - \frac{j0.5 \times j0.5}{-j0.9} = -j1.522 \quad \text{pu}$$

$$i=3, j=3; \quad Y_{33}(\text{new}) = Y_{33}(\text{old}) - \left(\frac{Y_{34} Y_{43}}{Y_{44}} \right)_{\text{old}} \\ = -j1.4 - \frac{j0.4 \times j0.4}{-j0.9} = -j1.222 \quad \text{pu}$$


$$i=1, j=2; \quad Y_{12}(\text{new}) = Y_{21}(\text{new}) = Y_{12}(\text{old}) - \left(\frac{Y_{14} Y_{42}}{Y_{44}} \right)_{\text{old}} \\ = j0.8 - \frac{0 \times j0.5}{-j0.9} = j0.8 \quad \text{pu}$$

$$i=1, j=3; \quad Y_{13}(\text{new}) = Y_{31}(\text{new}) = Y_{13}(\text{old}) - \left(\frac{Y_{14} Y_{43}}{Y_{44}} \right)_{\text{old}} \\ = j0.5 - \frac{0 \times j0.4}{-j0.9} = j0.5 \quad \text{pu}$$

$$i=2, j=3; \quad Y_{23}(\text{new}) = Y_{32}(\text{new}) = Y_{23}(\text{old}) - \left(\frac{Y_{24} Y_{43}}{Y_{44}} \right)_{\text{old}} \\ = j0.5 - \frac{j0.5 \times j0.4}{-j0.9} \\ = j0.722 \quad \text{pu}$$

Then new bus admittance matrix after eliminating bus ④, we have —
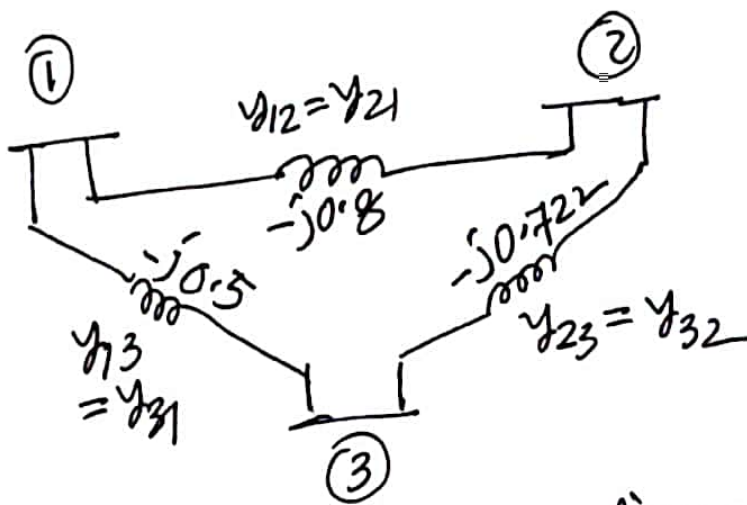
$$Y_{BUS}(new) = \begin{bmatrix} Y_{11} & Y_{12} & Y_{13} \\ Y_{21} & Y_{22} & Y_{23} \\ Y_{31} & Y_{32} & Y_{33} \end{bmatrix} = \begin{bmatrix} -j1.3 & j0.8 & j0.5 \\ j0.8 & -j1.522 & j0.722 \\ j0.5 & j0.722 & -j1.22 \end{bmatrix}$$



$$\begin{aligned} Y_{12} = Y_{21} &= -Y_{12} \\ &= -j0.8 \\ Y_{13} = Y_{31} &= -Y_{13} \\ &= -j0.5 \\ Y_{23} = Y_{32} &= -Y_{23} \\ &= -j0.722 \end{aligned}$$

new admittance diagram

$$Z = \frac{1}{Y}$$

Quiz-2 : 4 March

11:30 - 12:30 PM

contact me