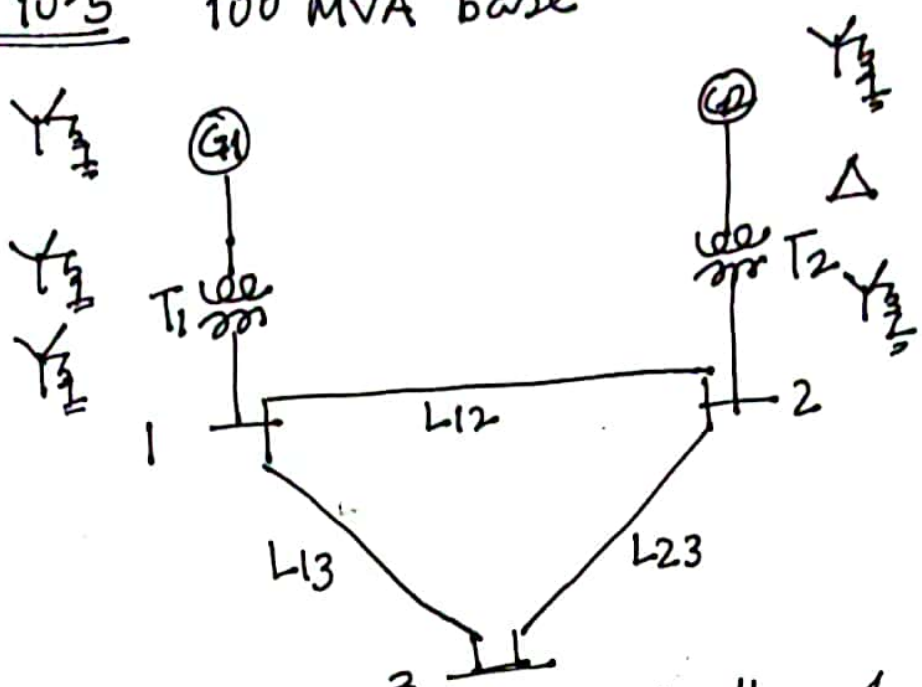


8 April 21
MC-A Eve

Ex. 10-5 100 MVA base



Zero-seq

Each generator is grounded through a reactor of $0.25j$ pu. Fault impedance, $Z_f = j0.1$ pu.


Calculate - fault current for

- ① 3- ϕ balanced fault at bus 3
- ② L-G fault at bus 3
- ③ L-L fault at bus 3
- ④ L-L-G fault at bus 3

Request
H.W.
Bus 1
Bus 2

Solution:

Positive sequence impedance network


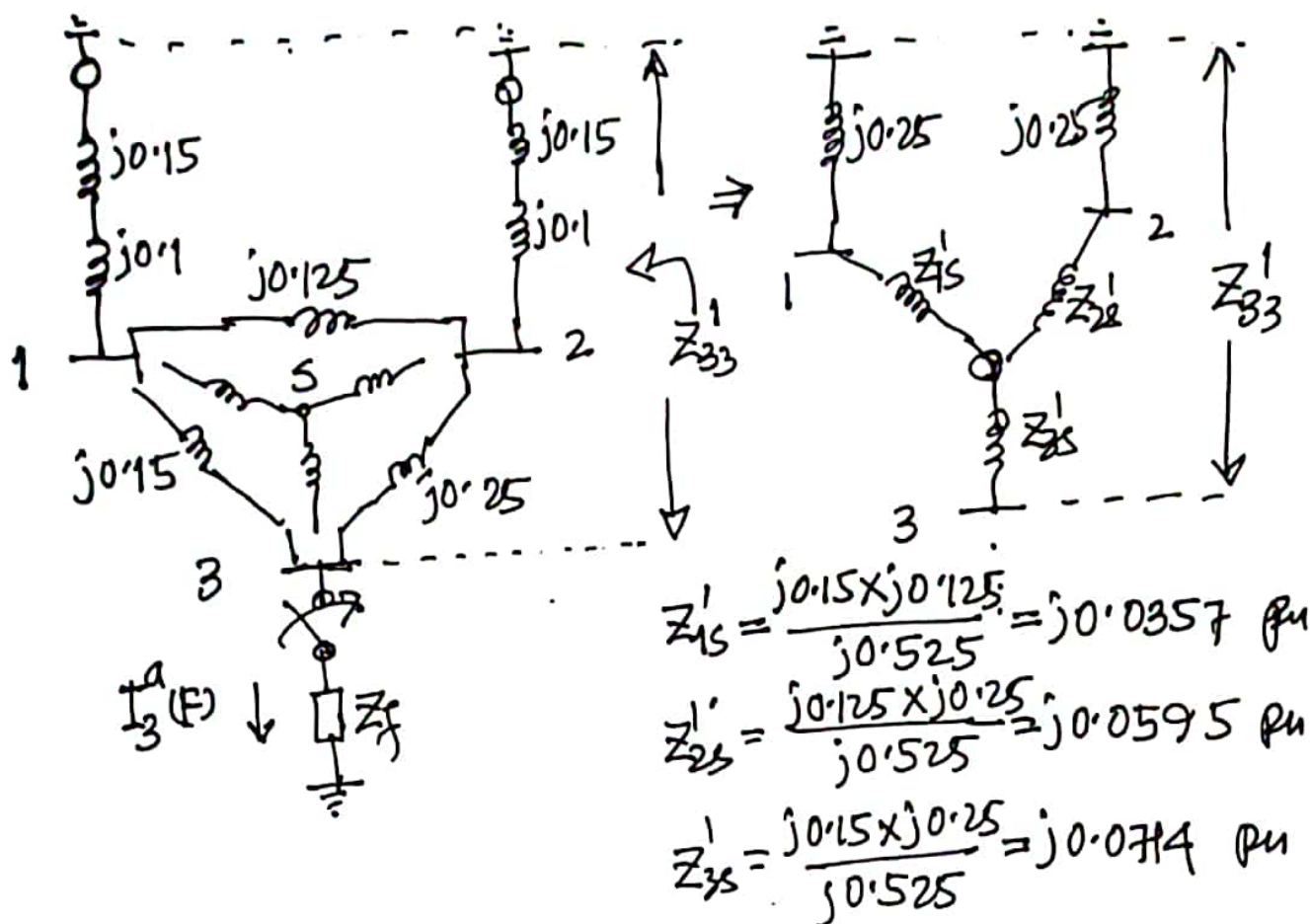


Therefore its equivalent impedance

$$\begin{aligned} Z'_{33} &= Z'_{35} + (j0.25 + Z'_{35}) \parallel (j0.25 + Z'_{23}) \\ &= j0.0714 + (j0.2857 \parallel j0.3095) \\ &= j0.0714 + j0.1486 = j0.22 \text{ pu.} \end{aligned}$$


Since, the negative sequence impedance of each element is same as positive sequence impedance.

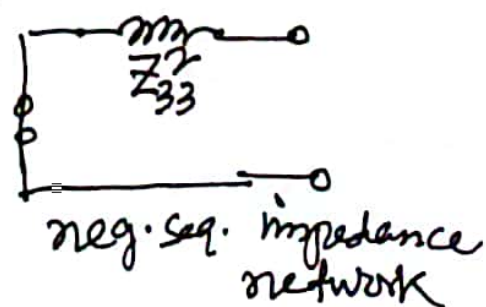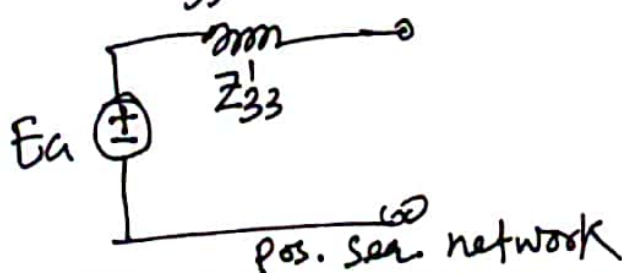Then, $Z'_{33} = Z''_{33} = j0.22 \text{ pu.}$




Zero sequence impedance network

Z^0/X^0

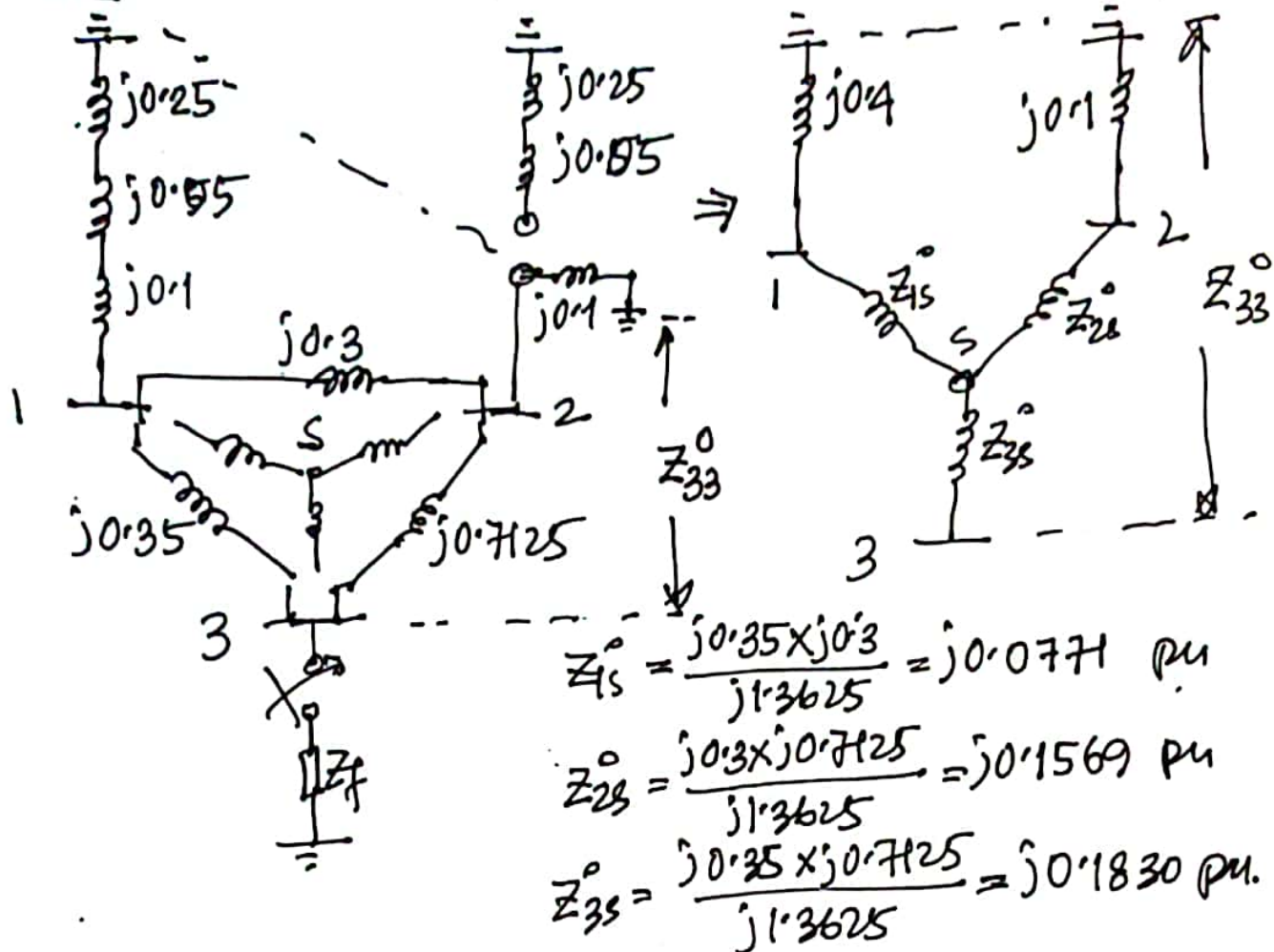

Thevenin's equivalent impedance
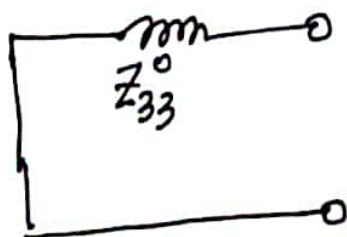
$$\begin{aligned}
 Z_{33}^0 &= Z_{35}^0 + (j0.4 + Z_{35}^0) \parallel (j0.1 + Z_{23}^0) \\
 &= j0.1830 + (j0.4771 \parallel j0.2569) \\
 &= j0.1830 + j0.167 = j0.35 \text{ pu}
 \end{aligned}$$



Zero-seq. network

① 3- ϕ balanced fault at bus 3 / $V_1(0) = V_2 = \dots$

Let pre-fault bus voltages, $V_1(0) = V_2(0) = V_3(0) = 1.0$ pu

$$\text{Fault current, } I_3^a(F) = \frac{V_3^a(0)}{Z_{33}^1 + Z_f} = \frac{1.0}{j0.22 + j0.1} \\ = -j3.125 \text{ pu} \checkmark$$

② L-G fault at bus 3

$$\text{Fault current, } I_3^a(F) = 3 \cdot I_3^{a,0}$$

$$\text{where, } I_3^{a,0} = \frac{V_3^a(0)}{Z_{33}^1 + Z_{33}^2 + Z_{33}^0 + 3Z_f} \\ = \frac{1.0}{j0.22 + j0.22 + j0.35 + 3 \times j0.1} \\ = -j0.9174 \text{ pu.}$$

$$\text{Then, Fault current, } I_3^a(F) = 3 \times (-j0.9174) \\ = -j2.7523 \text{ pu.} \checkmark$$

③ L-L fault at bus 3

$$\text{Fault current, } I_3^b(F) = -j\sqrt{3} \cdot I_3^{a,1}$$

$$\text{where, } I_3^{a,1} = \frac{V_3^a(0)}{Z_{33}^1 + Z_{33}^2 + Z_f} = \frac{1.0}{j0.22 + j0.22 + j0.1} \\ = -j1.852 \text{ pu.}$$

Then, fault current,

$$I_3^b(F) = -j\sqrt{3} \times (-j1.852) = -3.2078 \text{ pu.} \checkmark$$

④ L-L-G fault at bus 3

$$\text{Fault current, } I_3(F) = I_3^b + I_3^c = 3 \cdot I_3^{a,0}$$

$$\text{where, } I_3^{a,0} = - \frac{V_3^a(0) - I_3^{a,1} \times Z_{33}'}{Z_{33}^0 + 3Z_f}$$

$$\text{and, } I_3^{a,1} = \frac{V_3^a(0)}{Z_{33}^1 + \frac{Z_{33}^2 (Z_{33}^0 + 3Z_f)}{Z_{33}^2 + (Z_{33}^0 + 3Z_f)}}$$

$$= \frac{1.0}{j0.22 + \frac{j0.22 \times (j0.35 + 3 \times j0.1)}{j0.22 + (j0.35 + 3 \times j0.1)}}$$

$$\Rightarrow I_3^{a,1} = \frac{1.0}{j0.22 + j0.1644} = -j2.6015 \text{ pu}$$

$$\text{then, } I_3^{a,0} = - \frac{1.0 - (-j2.6015 \times j0.22)}{j0.35 + 3 \times j0.1}$$

$$= - \frac{1.0 - 0.57233}{j0.65}$$

$$= j0.658 \text{ pu.}$$

Finally, fault current,

$$I_3(F) = 3 \times I_3^{a,0} = 3 \times j0.658 = j1.974 \text{ pu}$$

Home work : Fault at

- * Bus - 1 }
- * Bus - 2 }

Ref. Ex. 9.1