

## **ASSIGNMENT**

Course Title: Introduction to Robotics

Course Code: CSE426

## **Submitted To**

Md Hafizul Imran, Senior Lecturer
Department of CSE
Daffodil International University

## **Submitted By**

Purnima Rani Das 191-15-2633 PC-B

Department of CSE

Daffodil International University

Date: 07-12-2022

1. Design a circuit with 3 resistor parallel +2 series +4 parallel+1 Series. 9V battery is connected with 1st 3 parallel resistor and last 1 series resistor sequentially. And complete the circuit wiring on Tinkercad platform. attached screenshot.

