

NAME: Md Tasmim Hasan khan

ID: 191-15-2739

Sec: PC-C

1. Design a circuit with 3 resistor parallel +2 series +4 parallel+1 Series. 9V battery is connected with 1st 3 parallel resistor and last 1 series resistor sequentially. And complete the circuit wiring on Tinkercad platform. attached screenshot.

