




**DIFFERENT
COMBINATIONS OF
RESISTANCES**

CONTENTS

- Series resistances
- Voltage Division Rule .
- Parallel resistances
- Current division rule
- Delta to Wye conversion.
- Wye to delta conversion

Series Combination of Resistors

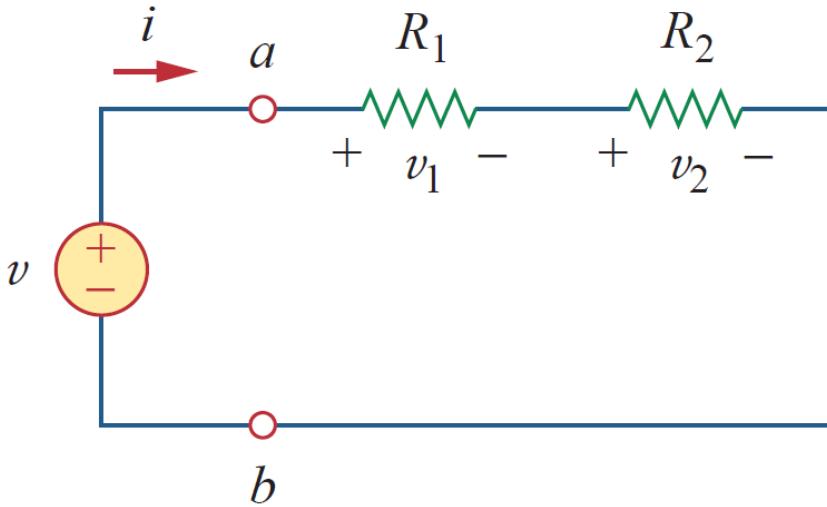

$$v_1 = iR_1, \quad v_2 = iR_2$$

$$v = v_1 + v_2 = i(R_1 + R_2)$$


$$i = \frac{v}{R_1 + R_2}$$

For $V = 10 \text{ V}$; $R_1 = 7 \Omega$, $R_2 = 3\Omega$, The value of i ?

$$i = 1 \text{ A}$$

For $V = 10 \text{ V}$; $R_{eq} = R_1 + R_2 = (7 + 3) \Omega = 10 \Omega$,
The value of I ?

$$i = 1 \text{ A}$$

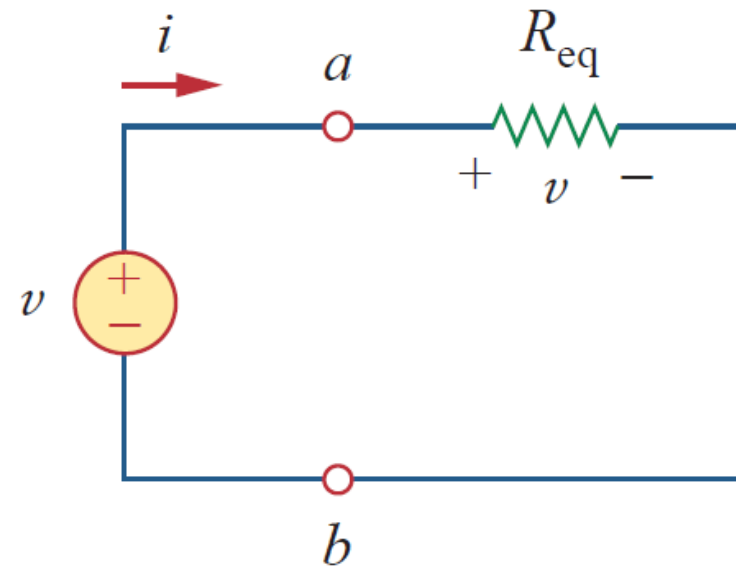


$$R_{eq} = R_1 + R_2$$

$$v = iR_{eq}$$

Series Combination of Resistors

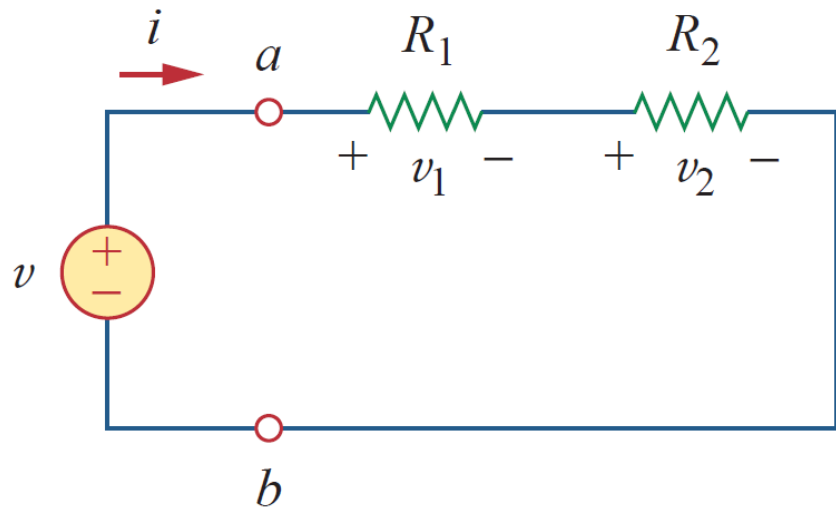
The equivalent resistance of any number of resistors connected in series is the sum of the individual resistances.



$$R_{\text{eq}} = R_1 + R_2 + \cdots + R_N = \sum_{n=1}^N R_n$$

$$R_{\text{eq}} = R_1 + R_2$$

Voltage Division Rule

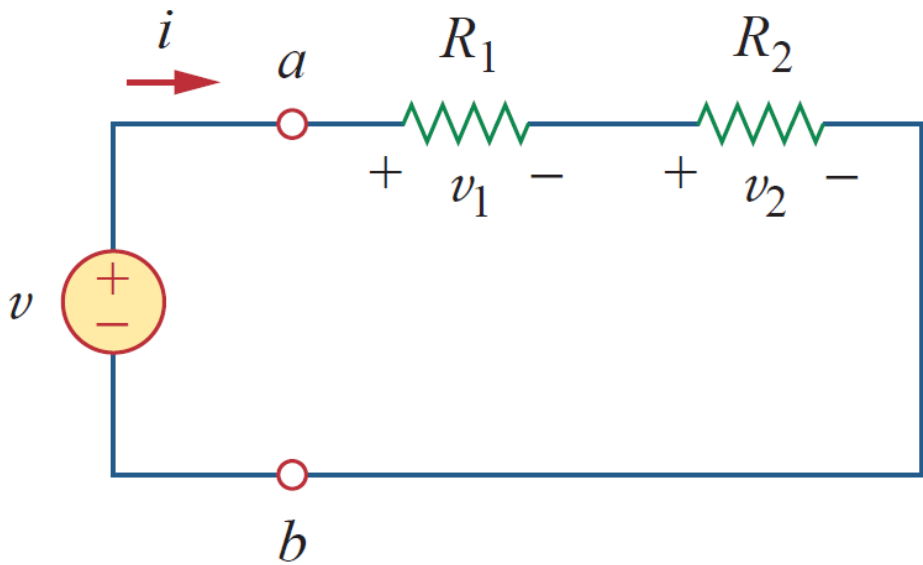

For $V = 10\text{ V}$; $R_1 = 7\ \Omega$, $R_2 = 3\ \Omega$, The value of v_1 and v_2 ?


$$v_1 = iR_1, \quad v_2 = iR_2$$

$$i = \frac{v}{R_1 + R_2}$$

$$v_1 = \frac{R_1}{R_1 + R_2} v, \quad v_2 = \frac{R_2}{R_1 + R_2} v$$

$$v_n = \frac{R_n}{R_1 + R_2 + \cdots + R_N} v$$

Parallel Resistors

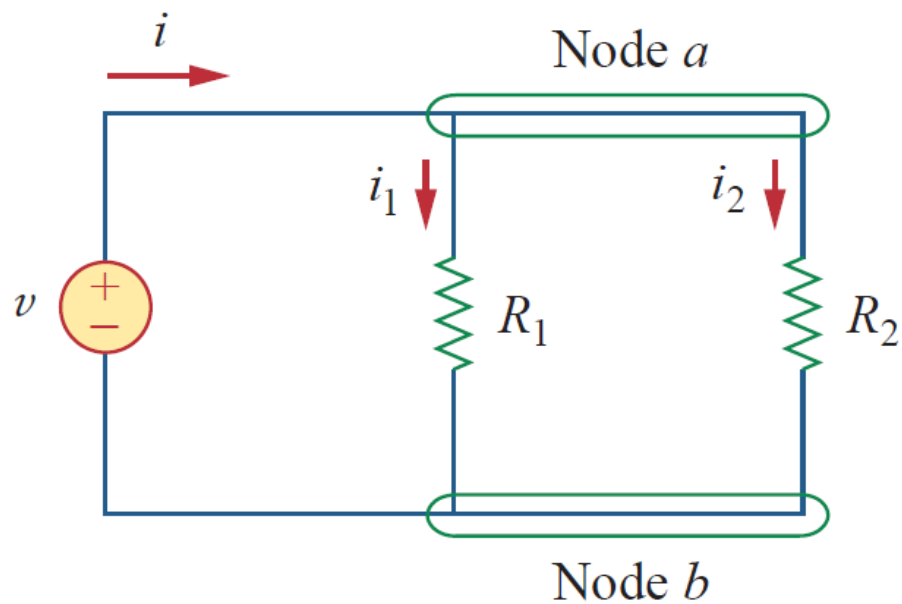

$$v = i_1 R_1 = i_2 R_2 \quad i_1 = \frac{v}{R_1}, \quad i_2 = \frac{v}{R_2}$$

$$i = i_1 + i_2$$



$$i = \frac{v}{R_1} + \frac{v}{R_2} = v \left(\frac{1}{R_1} + \frac{1}{R_2} \right)$$

For $V = 10 \text{ V}$; $R_1 = 7 \Omega$, $R_2 = 3\Omega$, The value of i ?

$$i = 4.76 \text{ A}$$

$$\frac{1}{R_{\text{eq}}} = \frac{1}{R_1} + \frac{1}{R_2}$$

Parallel Resistors

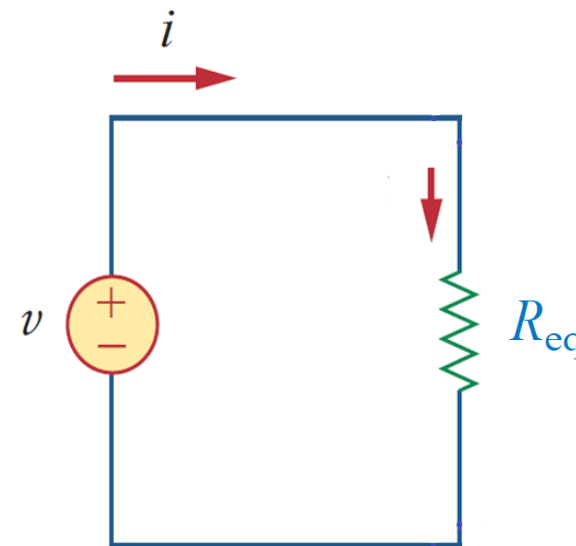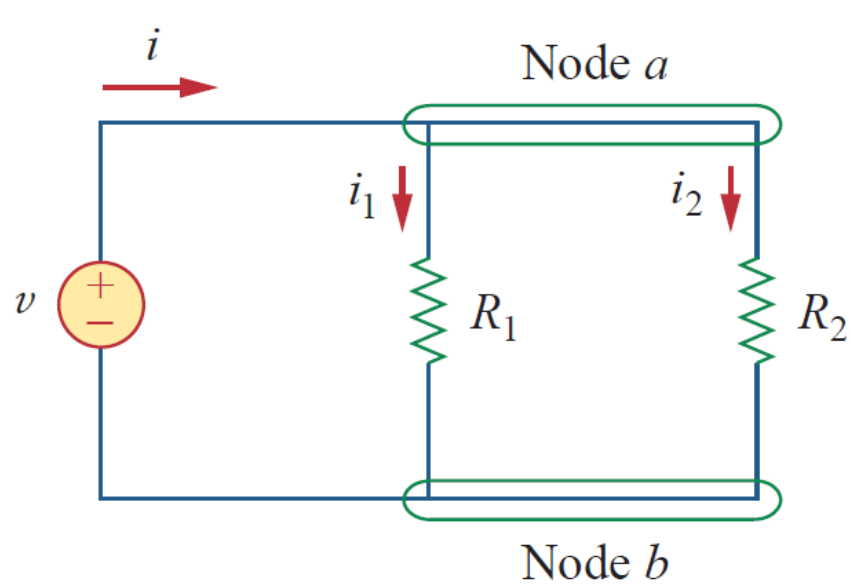

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$$


$$R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$$

For $V = 10\text{ V}$; $R_1 = 7\ \Omega$, $R_2 = 3\ \Omega$, The value of R_{eq} ? $R_{eq} = 2.1\ \Omega$

The value of i ? $i = 4.76\text{ A}$

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_N}$$


Current Division Rule

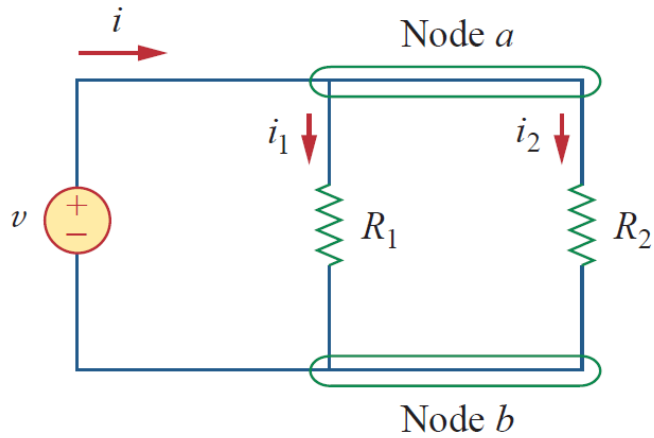

$$v = i_1 R_1 = i_2 R_2 \quad i_1 = \frac{v}{R_1}, \quad i_2 = \frac{v}{R_2}$$

$$v = i R_{\text{eq}} = \frac{i R_1 R_2}{R_1 + R_2}$$
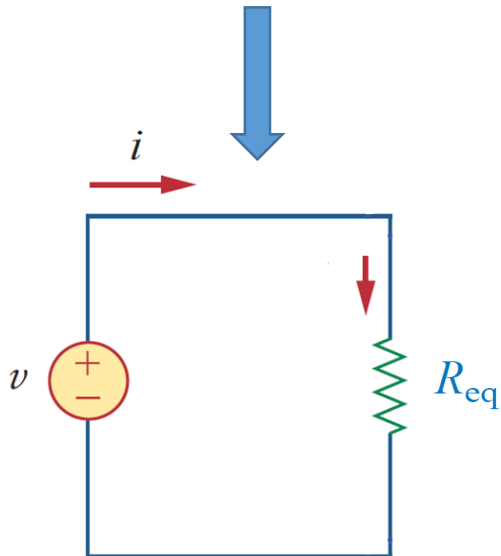
$$R_{\text{eq}} = \frac{R_1 R_2}{R_1 + R_2}$$



$$i_1 = \frac{R_2 i}{R_1 + R_2}, \quad i_2 = \frac{R_1 i}{R_1 + R_2}$$

Voltage & Current Division Rule

$$v_1 = \frac{R_1}{R_1 + R_2} v$$


$$v_2 = \frac{R_2}{R_1 + R_2} v$$

$$i_1 = \frac{\frac{1}{R_1}}{\frac{1}{R_1} + \frac{1}{R_2}} i \quad \rightarrow \quad i_1 = \frac{R_2 i}{R_1 + R_2}$$

$$i_2 = \frac{\frac{1}{R_2}}{\frac{1}{R_1} + \frac{1}{R_2}} i \quad \rightarrow \quad i_2 = \frac{R_1 i}{R_1 + R_2}$$

Mathematical Examples

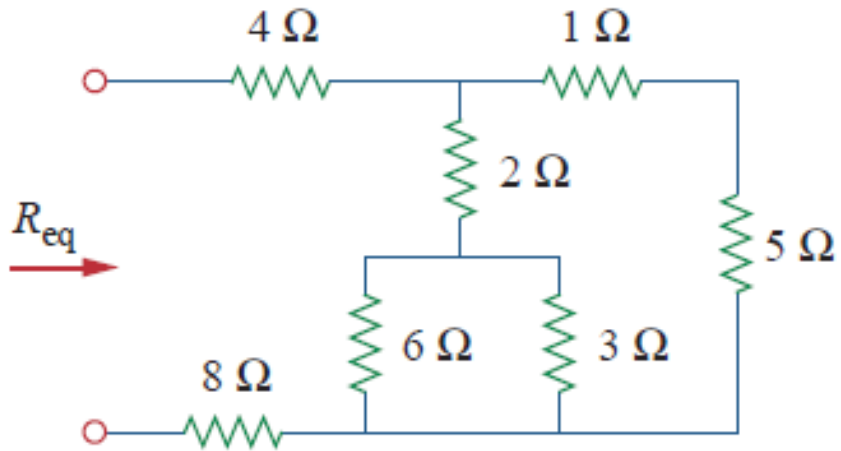Find R_{eq} for the circuit shown in Fig.




$$6\ \Omega \parallel 3\ \Omega = \frac{6 \times 3}{6 + 3} = 2\ \Omega$$

$$1\ \Omega + 5\ \Omega = 6\ \Omega$$

$$2\ \Omega + 2\ \Omega = 4\ \Omega$$





$$4\ \Omega \parallel 6\ \Omega = \frac{4 \times 6}{4 + 6} = 2.4\ \Omega$$
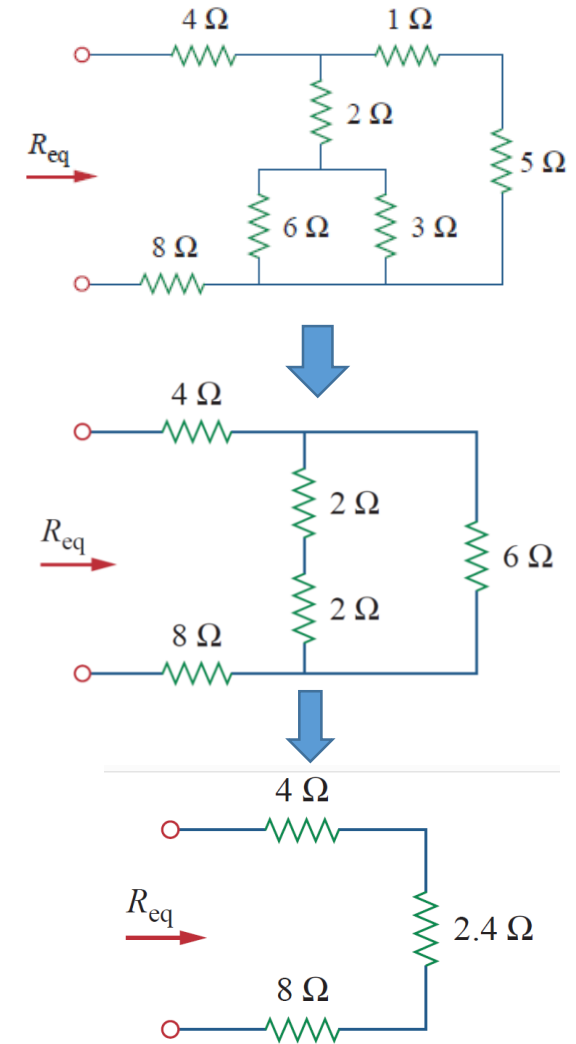
$$R_{eq} = 4\ \Omega + 2.4\ \Omega + 8\ \Omega = 14.4\ \Omega$$



Mathematical Examples

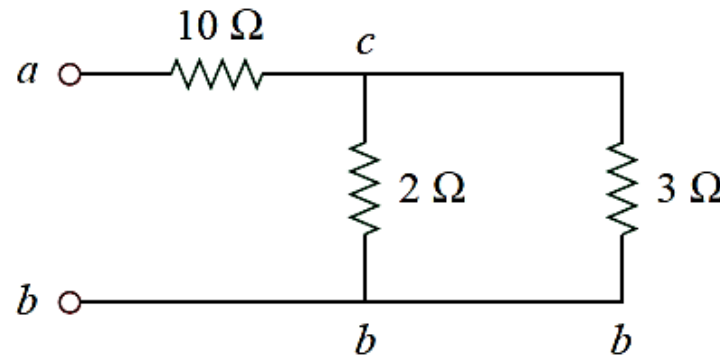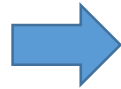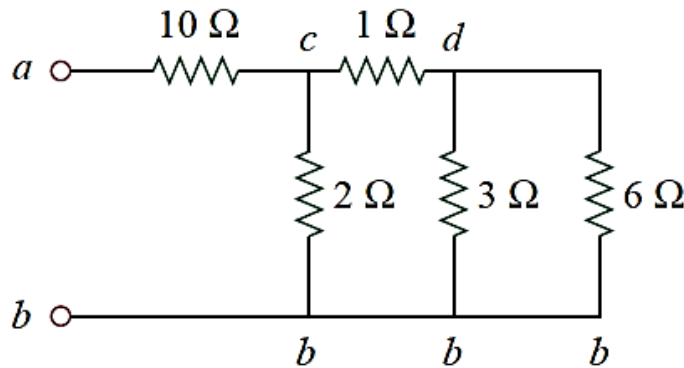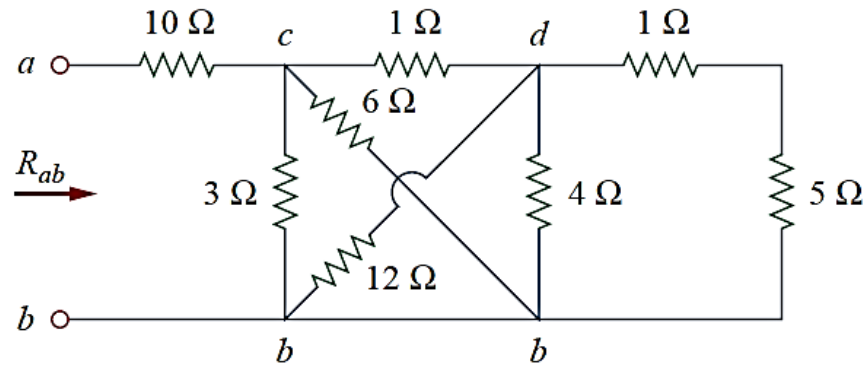Calculate the equivalent resistance R_{ab} in the circuit



$$3 \Omega \parallel 6 \Omega = \frac{3 \times 6}{3 + 6} = 2 \Omega$$

$$12 \Omega \parallel 4 \Omega = \frac{12 \times 4}{12 + 4} = 3 \Omega$$

$$1 \Omega + 5 \Omega = 6 \Omega$$



$$3 \Omega \parallel 6 \Omega = \frac{3 \times 6}{3 + 6} = 2 \Omega$$

$$1 \Omega + 2 \Omega = 3 \Omega$$

$$2 \Omega \parallel 3 \Omega = \frac{2 \times 3}{2 + 3} = 1.2 \Omega$$



$$R_{ab} = 10 + 1.2 = 11.2 \Omega$$

Wye-Delta Transformations

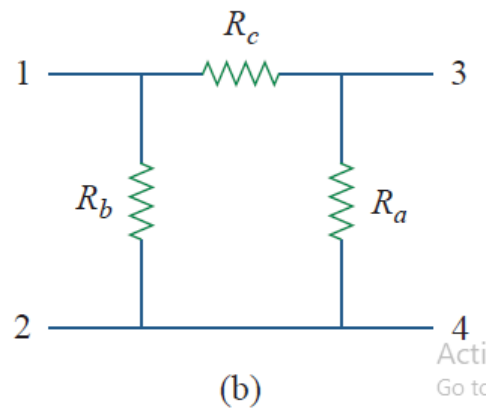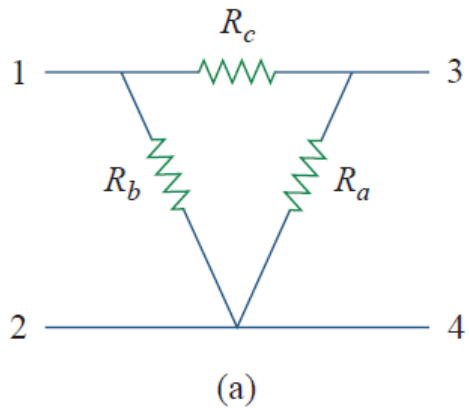

Acti
Go to

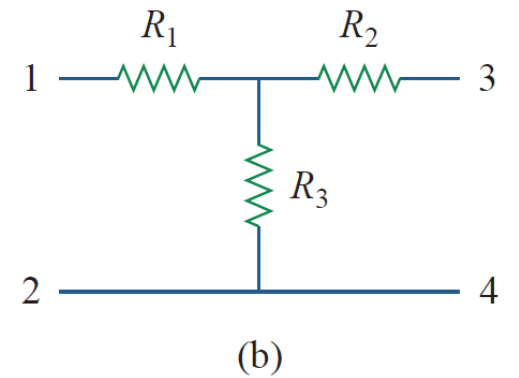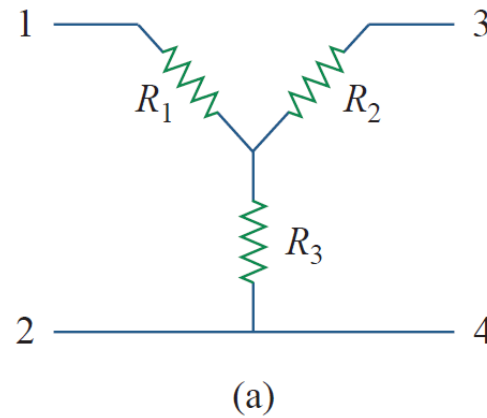Two forms of the same network: (a)
(b) Π .






Two forms of the same network: (a) Y, (b) T.

Delta to Wye Conversion

$$R_1 = \frac{R_b R_c}{R_a + R_b + R_c}$$


$$R_2 = \frac{R_c R_a}{R_a + R_b + R_c}$$
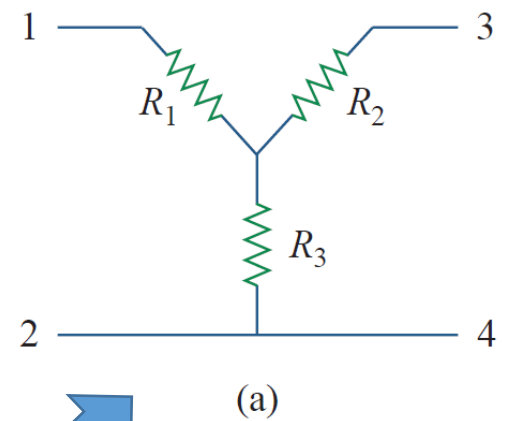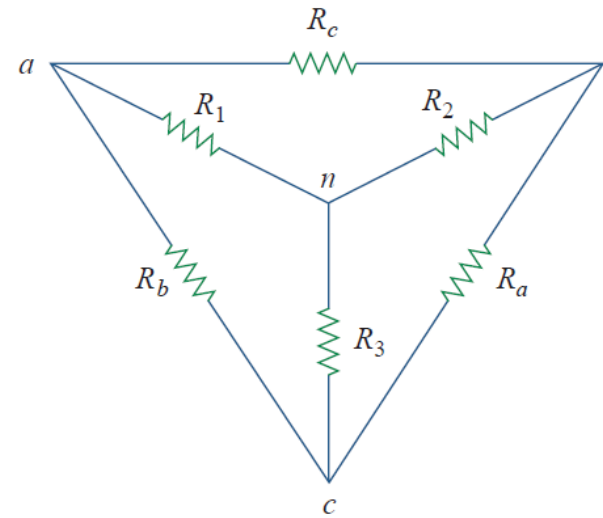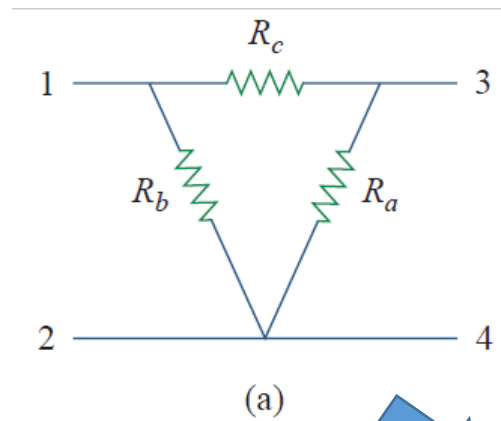
$$R_3 = \frac{R_a R_b}{R_a + R_b + R_c}$$








Delta to Wye Conversion

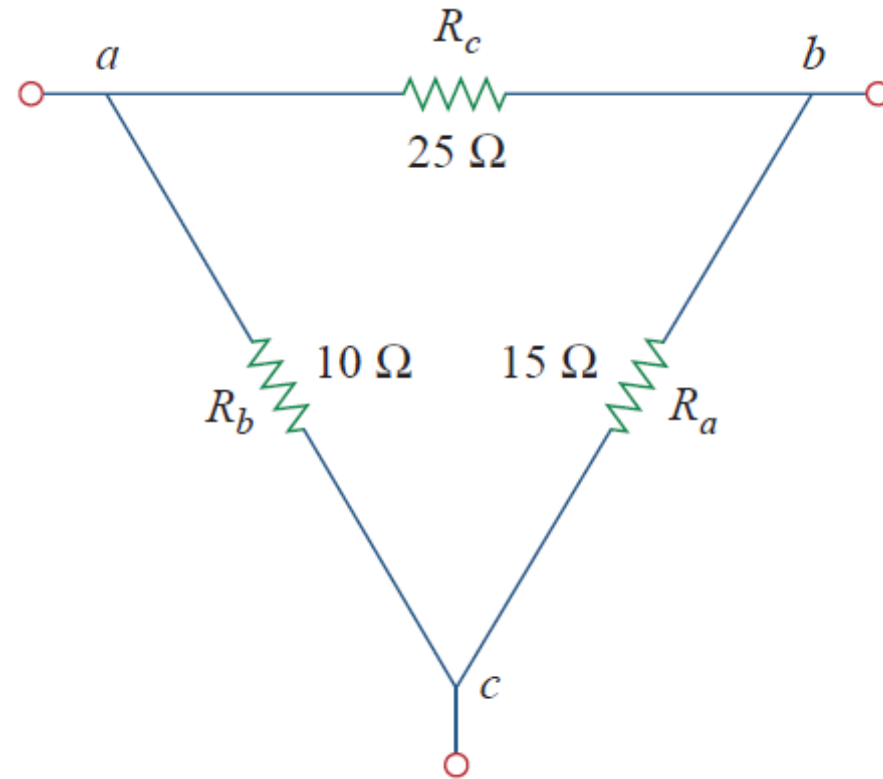Convert the Δ network in Fig. to an equivalent Y network.



(a)

Delta to Wye Conversion

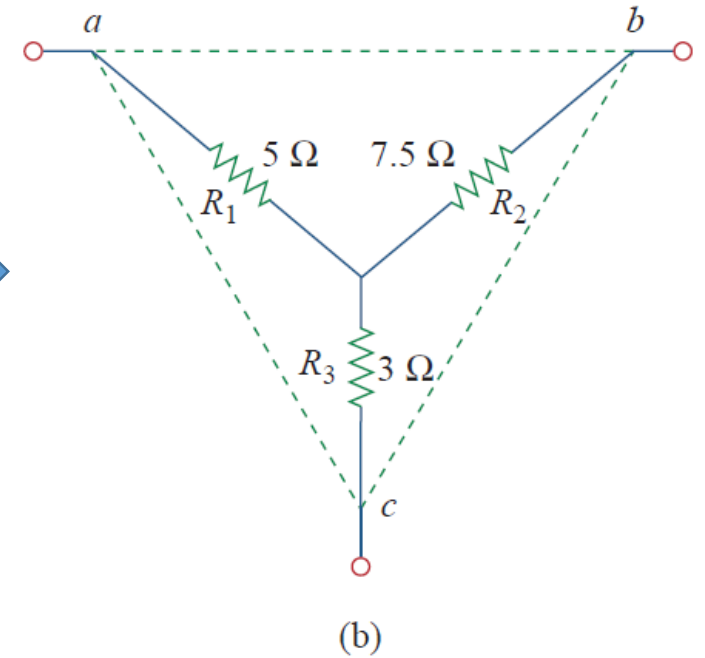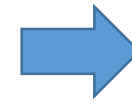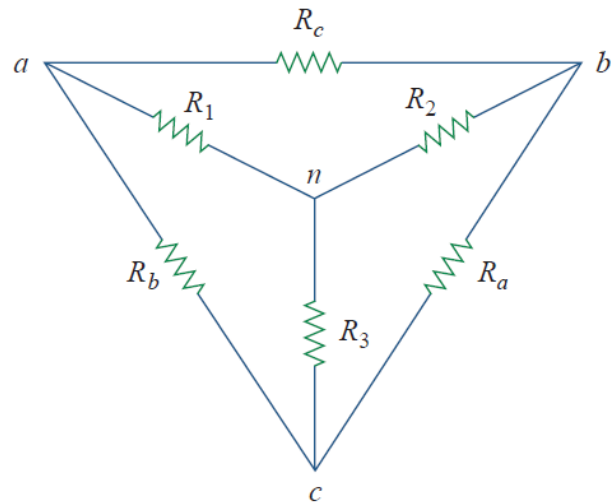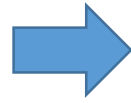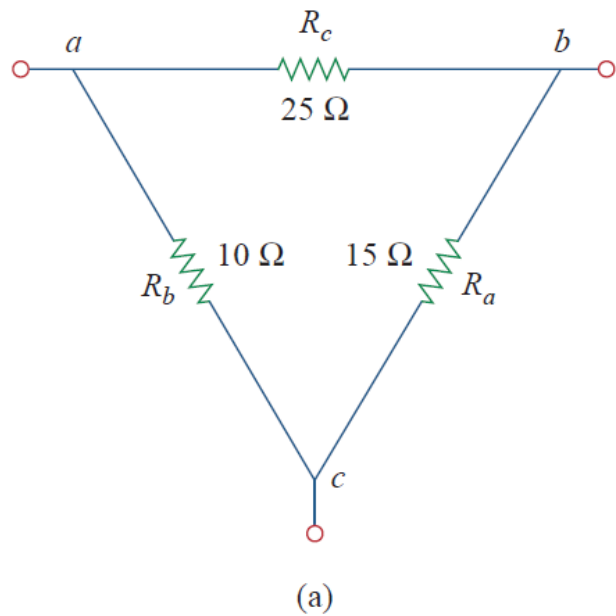

$$R_1 = \frac{R_b R_c}{R_a + R_b + R_c} = \frac{10 \times 25}{15 + 10 + 25} = \frac{250}{50} = 5\ \Omega$$

$$R_2 = \frac{R_c R_a}{R_a + R_b + R_c} = \frac{25 \times 15}{50} = 7.5\ \Omega$$


$$R_3 = \frac{R_a R_b}{R_a + R_b + R_c} = \frac{15 \times 10}{50} = 3\ \Omega$$

Wye to Delta Conversion


$$R_a = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1}$$

$$R_b = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2}$$

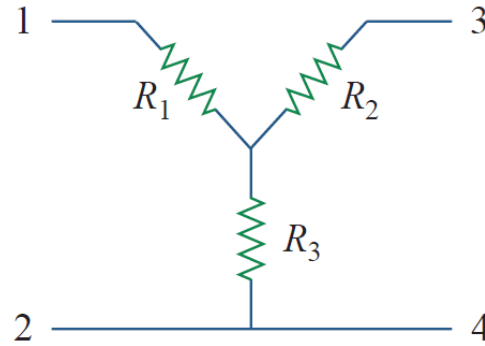
$$R_c = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3}$$



(a)

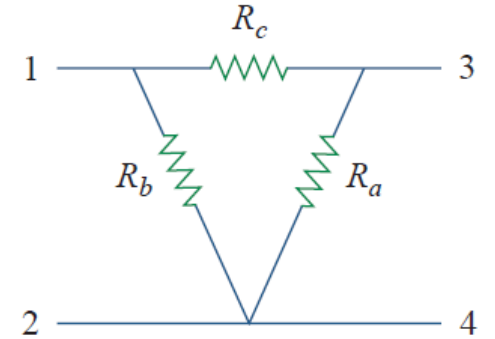


(a)

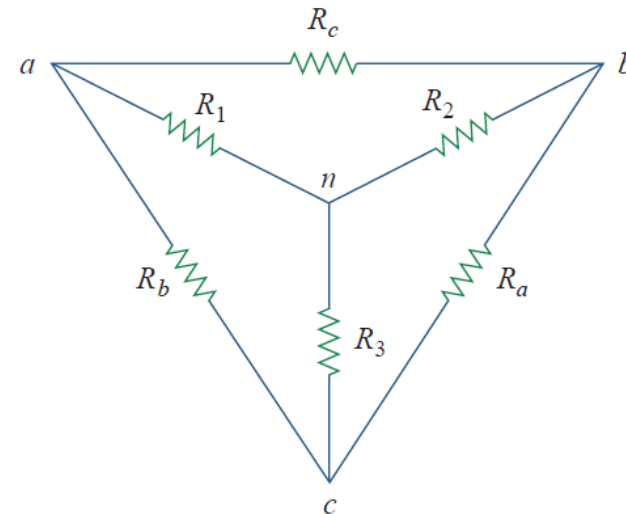





Circuit Solve

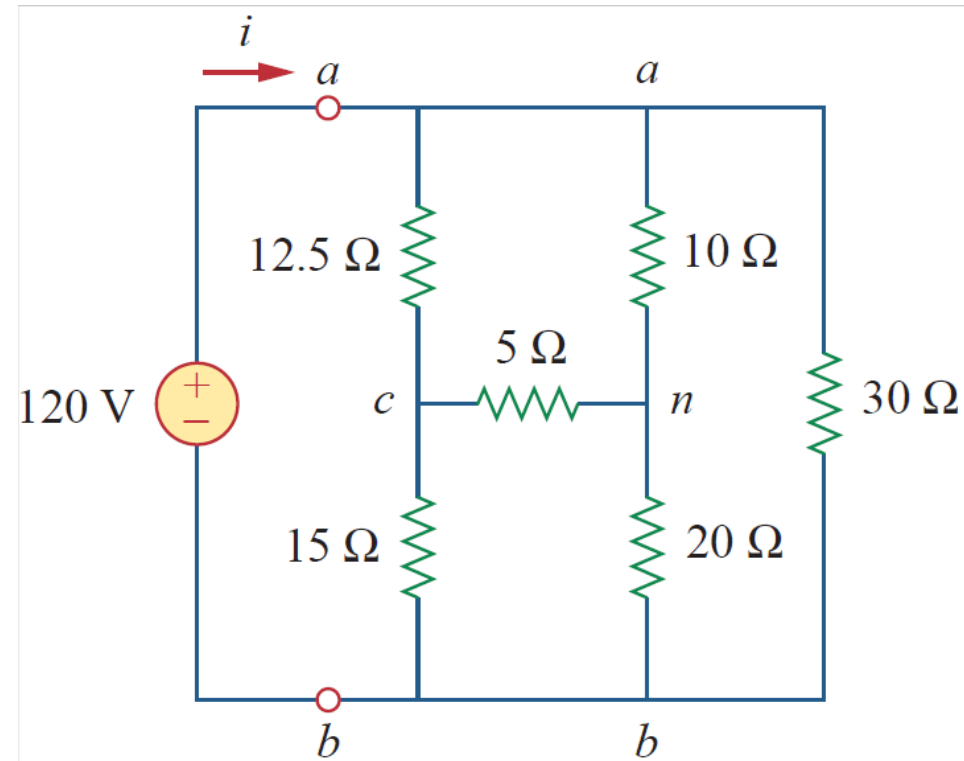Obtain the equivalent resistance R_{ab} for the circuit in Fig. 2.52 and use it to find current i .



Circuit Solve

METHOD-1

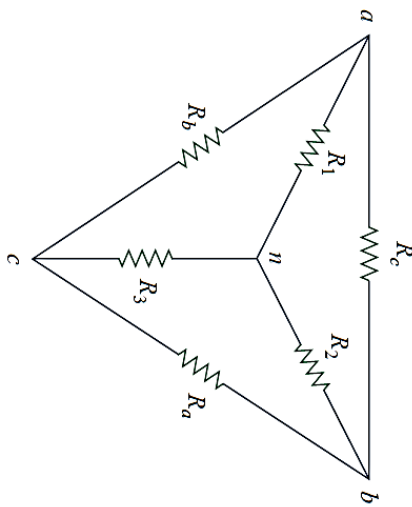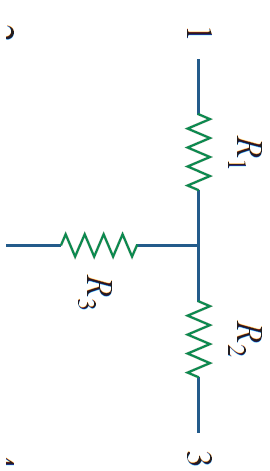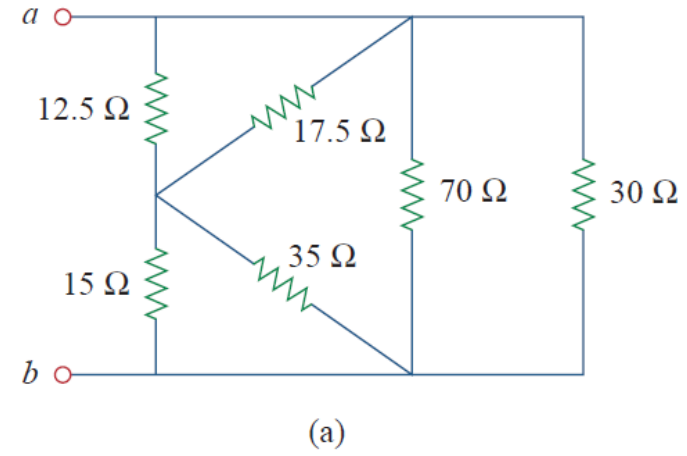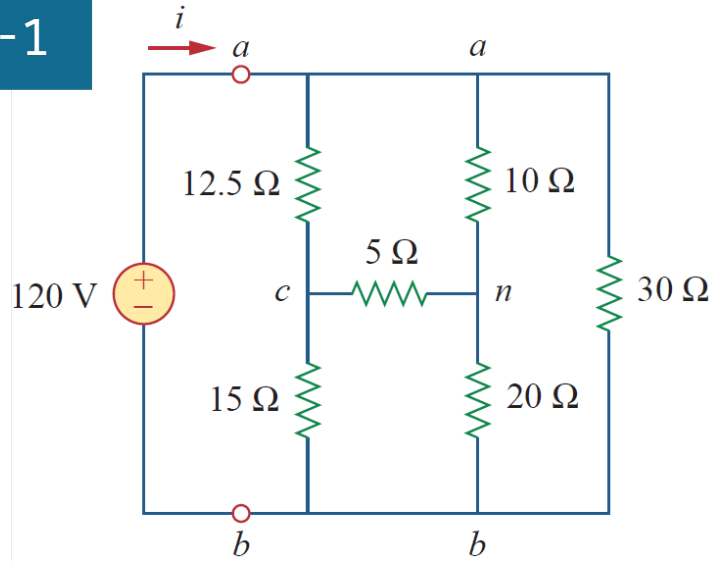

$$R_1 = 10\ \Omega, \quad R_2 = 20\ \Omega, \quad R_3 = 5\ \Omega$$


$$R_a = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1} = \frac{10 \times 20 + 20 \times 5 + 5 \times 10}{10} = \frac{350}{10} = 35\ \Omega$$

$$R_b = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2} = \frac{350}{20} = 17.5\ \Omega$$

$$R_c = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3} = \frac{350}{5} = 70\ \Omega$$

Circuit Solve

METHOD-1

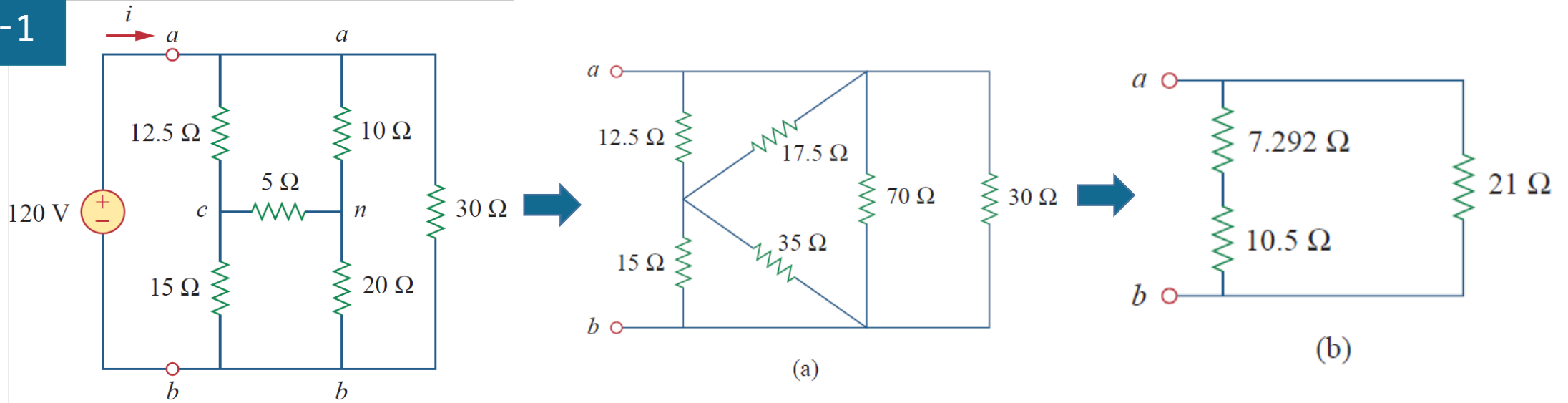

$$70 \parallel 30 = \frac{70 \times 30}{70 + 30} = 21 \Omega$$

$$12.5 \parallel 17.5 = \frac{12.5 \times 17.5}{12.5 + 17.5} = 7.292 \Omega$$



$$15 \parallel 35 = \frac{15 \times 35}{15 + 35} = 10.5 \Omega$$

$$R_{ab} = (7.292 + 10.5) \parallel 21 = \frac{17.792 \times 21}{17.792 + 21} = 9.632 \Omega$$



$$i = \frac{v_s}{R_{ab}} = \frac{120}{9.632} = 12.458 \text{ A}$$

Circuit Solve

METHOD-2

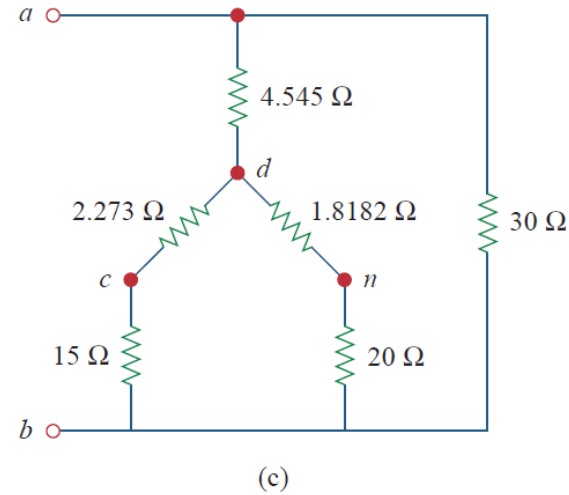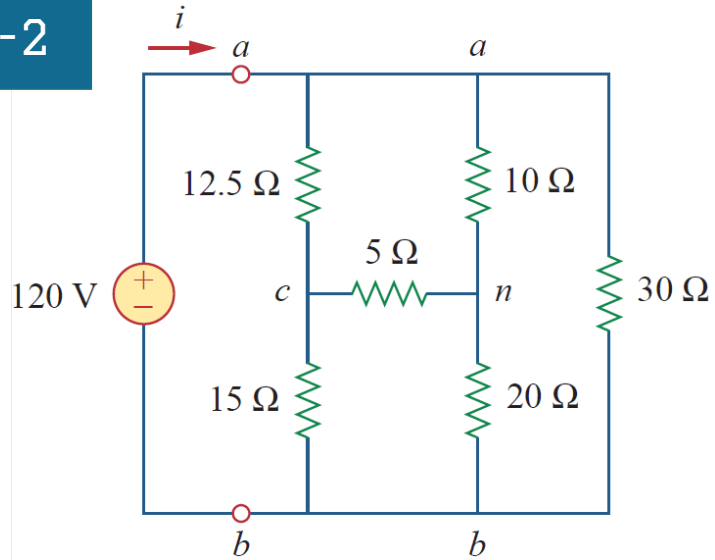
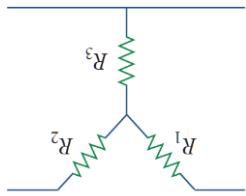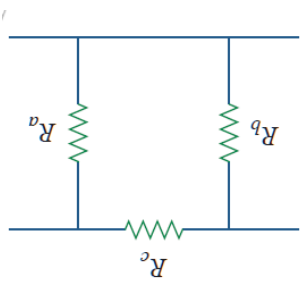
$$i = \frac{v_s}{R_{ab}} = \frac{120}{9.632} = \mathbf{12.458 \text{ A}}$$



$$R_{ad} = \frac{R_c R_n}{R_a + R_c + R_n} = \frac{10 \times 12.5}{5 + 10 + 12.5} = 4.545 \Omega$$

$$R_{cd} = \frac{R_a R_n}{27.5} = \frac{5 \times 12.5}{27.5} = 2.273 \Omega$$

$$R_{nd} = \frac{R_a R_c}{27.5} = \frac{5 \times 10}{27.5} = 1.8182 \Omega$$

$$R_{ab} = \frac{(9.642 + 4.545)30}{9.642 + 4.545 + 30} = \frac{425.6}{44.19} = \mathbf{9.631 \Omega}$$

$$R_{db} = \frac{(2.273 + 15)(1.8182 + 20)}{2.273 + 15 + 1.8182 + 20} = \frac{376.9}{39.09} = 9.642 \Omega$$

Thank you