

Fig 1


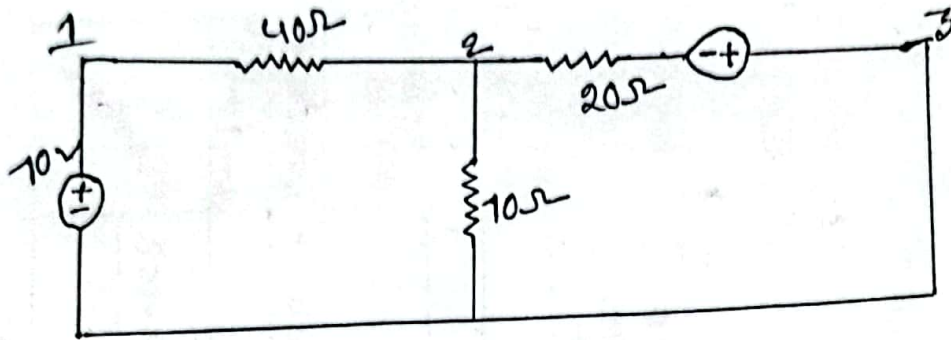


Fig 2

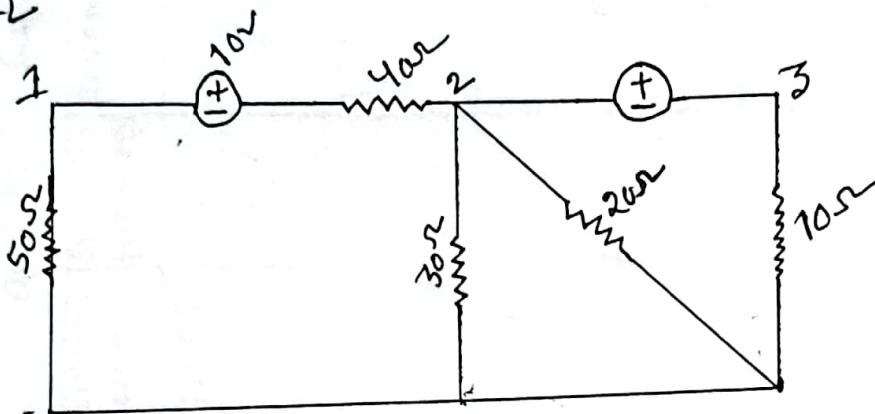

Nodal Analysis

~~equation~~

fig-1) $1 \Rightarrow v_1 = -70 \text{ V} \quad \text{--- (i)}$

using KCL in 2

$$2 \Rightarrow \frac{v_2 - v_1}{10} + \frac{v_2 - 20}{20} = 0$$


$$\Rightarrow \frac{2v_2 - 2v_1 + v_2 - 20}{20} = 0$$

$$\Rightarrow 3v_2 - 2v_1 - 20 \quad \text{--- (ii)}$$

Anal Analysis between (i) and (ii)

$$V_1 = -10V$$

$$V_2 = -25V$$

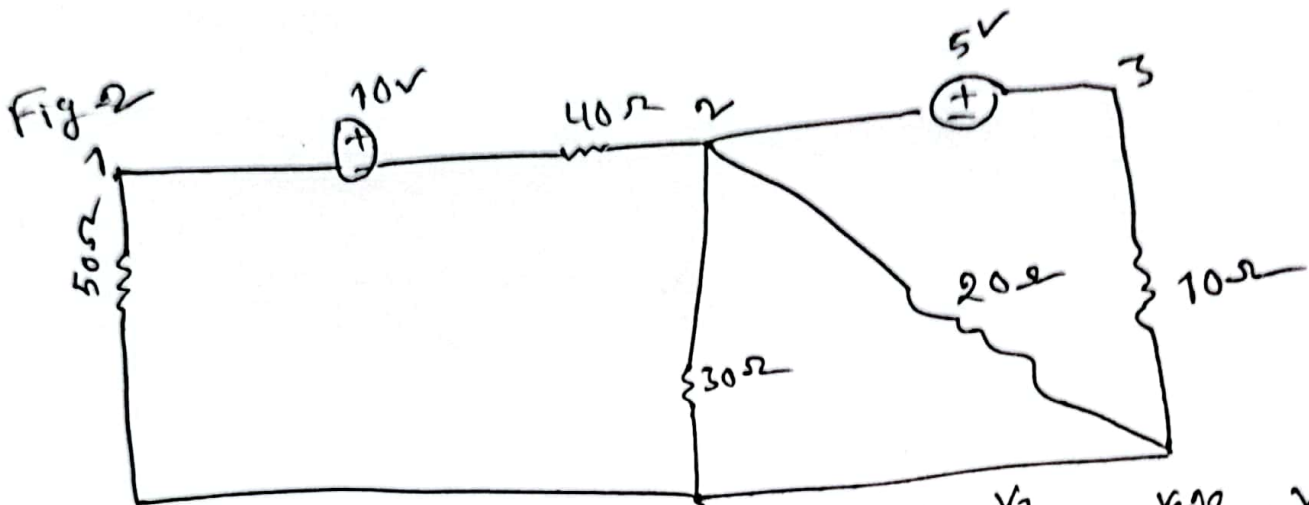

$$1) \Rightarrow \frac{V_1}{50} + \frac{V_1 - V_2}{40} + \frac{V_1 - V_2}{30} = 0$$

$$\Rightarrow \frac{12V_1 + 15V_1 - 300 + 20V_1 - 20V_2}{600} = 0 \Rightarrow \frac{12V_1 + 15V_1 - 300 + 20V_1 - 20V_2}{600} = 0$$

$$\Rightarrow 47V_1 - 20V_2 = 300 \quad (i)$$

$$2) \frac{V_1}{50} + \frac{V_1 - V_2}{40} + \frac{V_1 - V_2}{30} = 0$$

$$\Rightarrow \frac{12V_1 + 15V_1 - 300 + 20V_1 - 20V_2}{600} = 0$$

$$\Rightarrow 47V_1 - 20V_2 = 300$$

$$\text{② } 30 \parallel 20 \Rightarrow \frac{30 \times 20}{30 + 20}$$

$$\Rightarrow 12$$

$$\therefore \frac{V_2 - V_1}{12} + \frac{V_2}{5} + \frac{V_2}{10} = 0$$

$$\Rightarrow \frac{25V_2 - 5V_1 + 12V_2 + 6V_2}{60} = 0$$

$$\Rightarrow 23V_2 + 5V_1 = 0$$

$$\Rightarrow -5V_1 + 23V_2 = 0 \quad (ii)$$

Analysing (i) and (ii)

$$V_1 = 7.0336 \text{ V}$$

$$V_2 = 1.52 \text{ V}$$

