
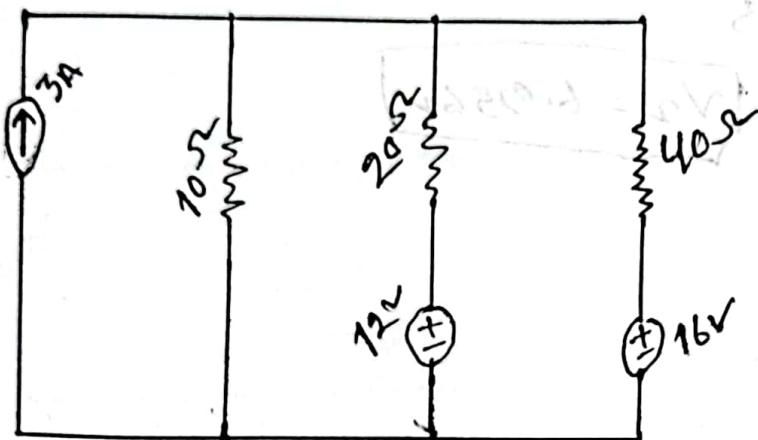


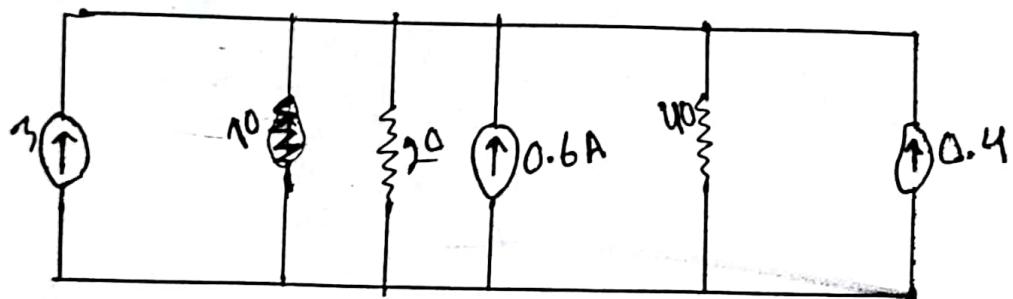2. Use source transformation to reduce the circuit in a single voltage source and a single resistor.



Solution:-



by transforming to voltage source to current source we get

$$I_2 = \frac{12}{20}$$

$$= 0.6 \text{ A}$$

and by transforming voltage source 3 to current source we get $I_3 = \frac{16}{40} = 0.4 \text{ A}$

$$\therefore \text{Total current, } I = I_1 + I_2 + I_3 \\ = 3 + 0.6 + 0.4 \\ =$$

\therefore equivalent resistance \rightarrow


$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

$$= \frac{1}{10} + \frac{1}{20} + \frac{1}{40}$$

$$\frac{1}{R_{eq}} = \frac{7}{40}$$

$$R_{eq} = \frac{40}{7} = 5.714$$

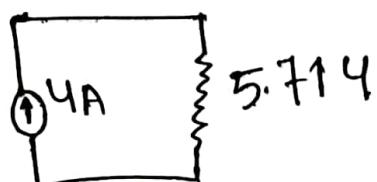After transforming on the source the new circuit is,



Ans.