



CIRCUIT THEORMS

PART : 02

Contents


- Thevenin Theorem
- Norton Theorem.
- Maximum Power Transfer

Thevenin Theorem



Thevenin's theorem states that a linear two-terminal circuit can be replaced by an equivalent circuit consisting of a voltage source V_{Th} in series with a resistor R_{Th} , where V_{Th} is the open-circuit voltage at the terminals and R_{Th} is the input or equivalent resistance at the terminals when the independent sources are turned off.

- A **linear circuit** is one whose output is linearly related (or directly proportional) to its input.


Thevenin Theorem

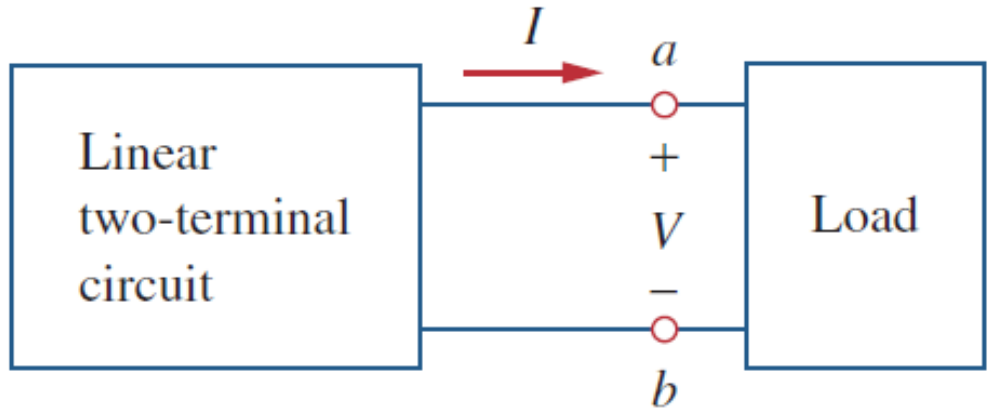

(a)

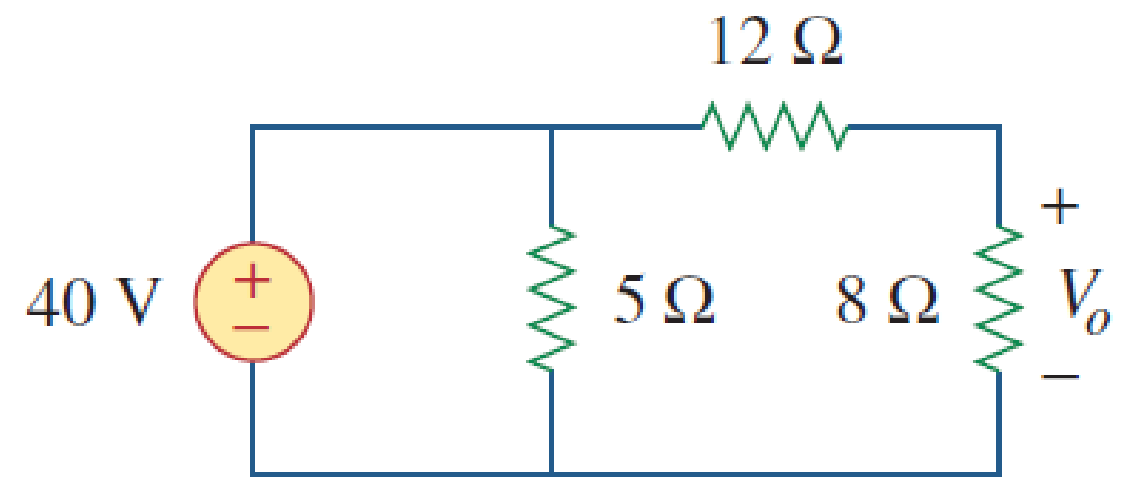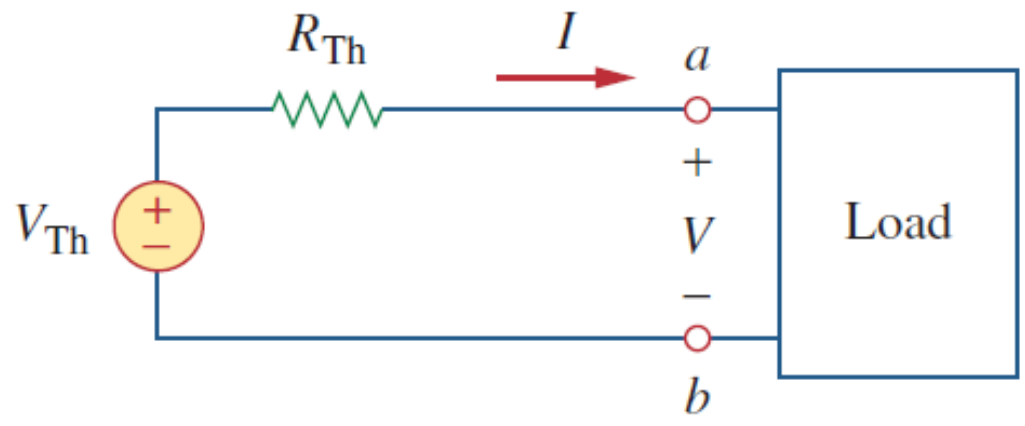


Thevenin Resistance R_{Th}

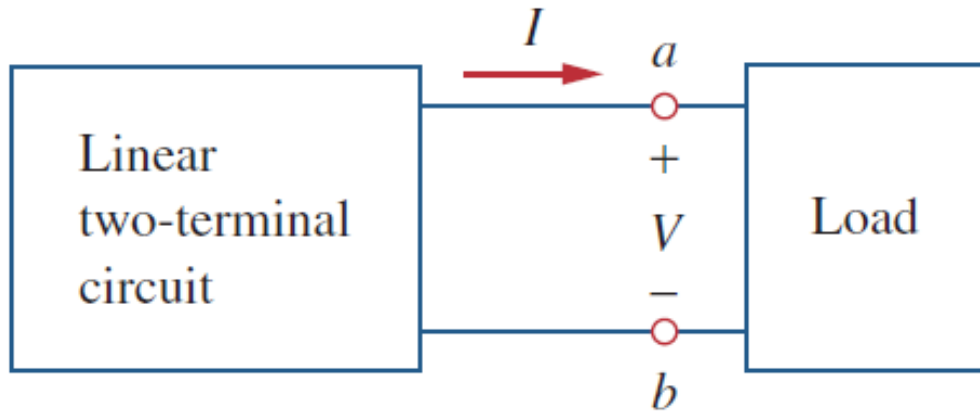


CASE-1 : No dependent Sources in the Network

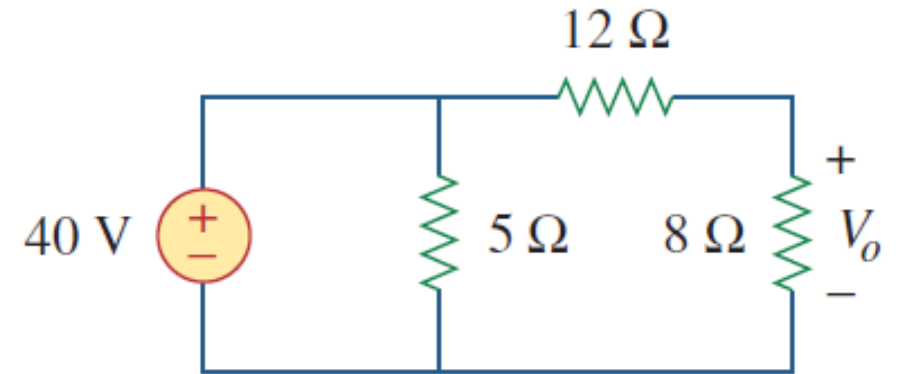If the network has no dependent sources, we turn off all independent sources. R_{Th} is the input resistance of the network looking between terminals a and b .




Thevenin Resistance R_{Th}

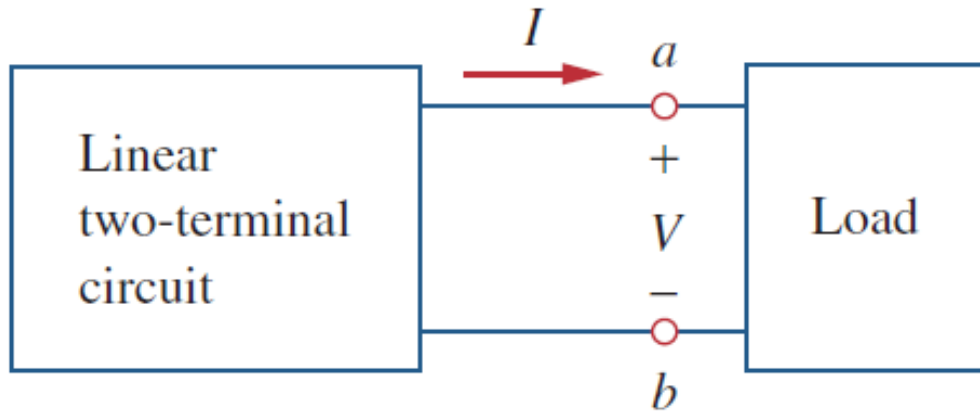


CASE-2 : Dependent Sources are present in the Network

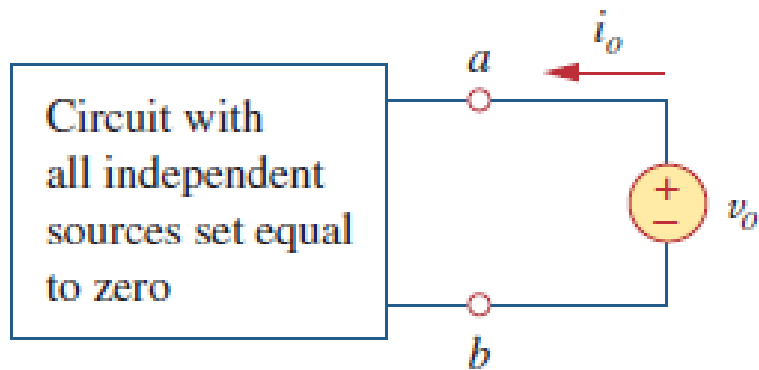If the network has dependent sources, we turn off all independent sources.



$$R_{Th} = \frac{v_o}{i_o}$$

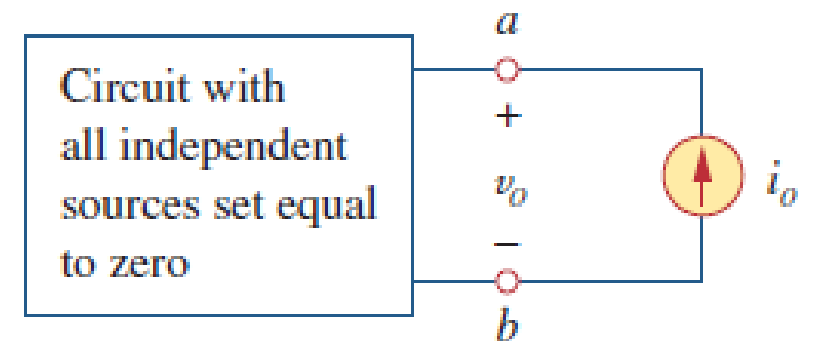

$$R_{Th} = \frac{v_o}{i_o}$$

Thevenin Theorem

Find the Thevenin equivalent circuit of the circuit shown in Fig. 4.27, to the left of the terminals a - b . Then find the current through $R_L = 6, 16,$ and 36Ω .

Example 4.8


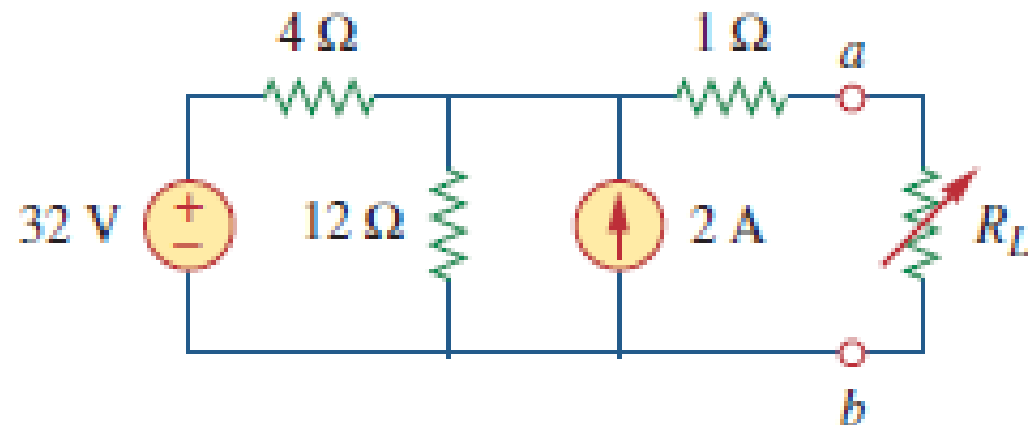
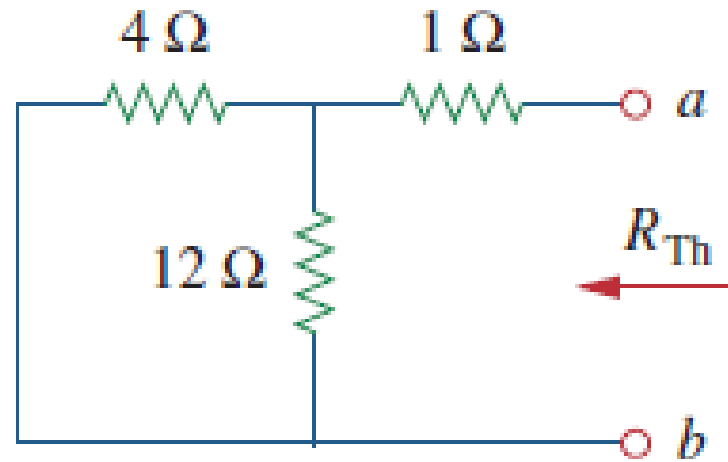



Figure 4.27
For Example 4.8.

Thevenin Theorem

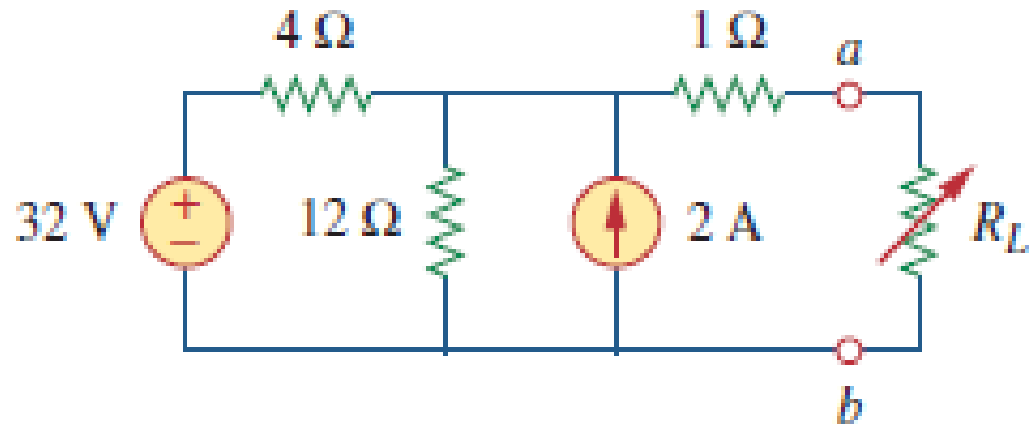

$$R_{Th} = 4 \parallel 12 + 1 = \frac{4 \times 12}{16} + 1 = 4 \Omega$$

Thevenin Theorem

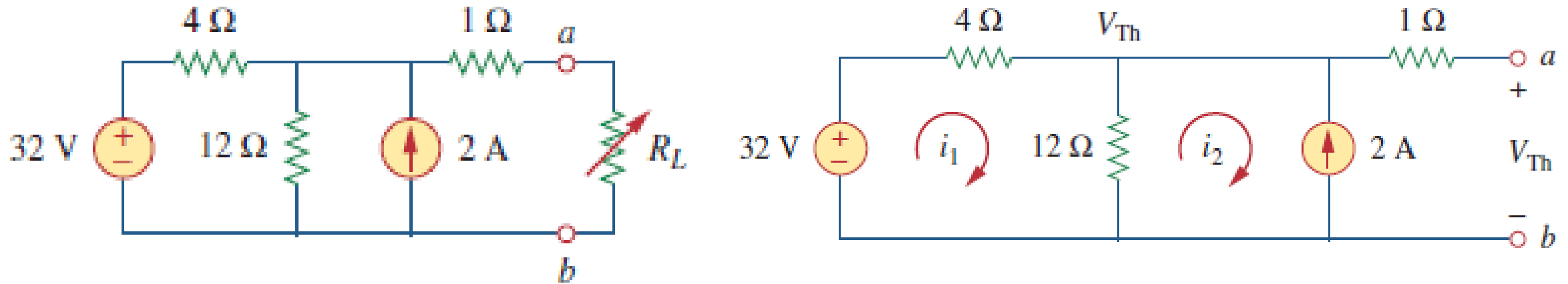

$$-32 + 4i_1 + 12(i_1 - i_2) = 0, \quad i_2 = -2 \text{ A}$$


Solving for i_1 , we get $i_1 = 0.5 \text{ A}$. Thus,

$$V_{\text{Th}} = 12(i_1 - i_2) = 12(0.5 + 2.0) = 30 \text{ V}$$


Thevenin Theorem

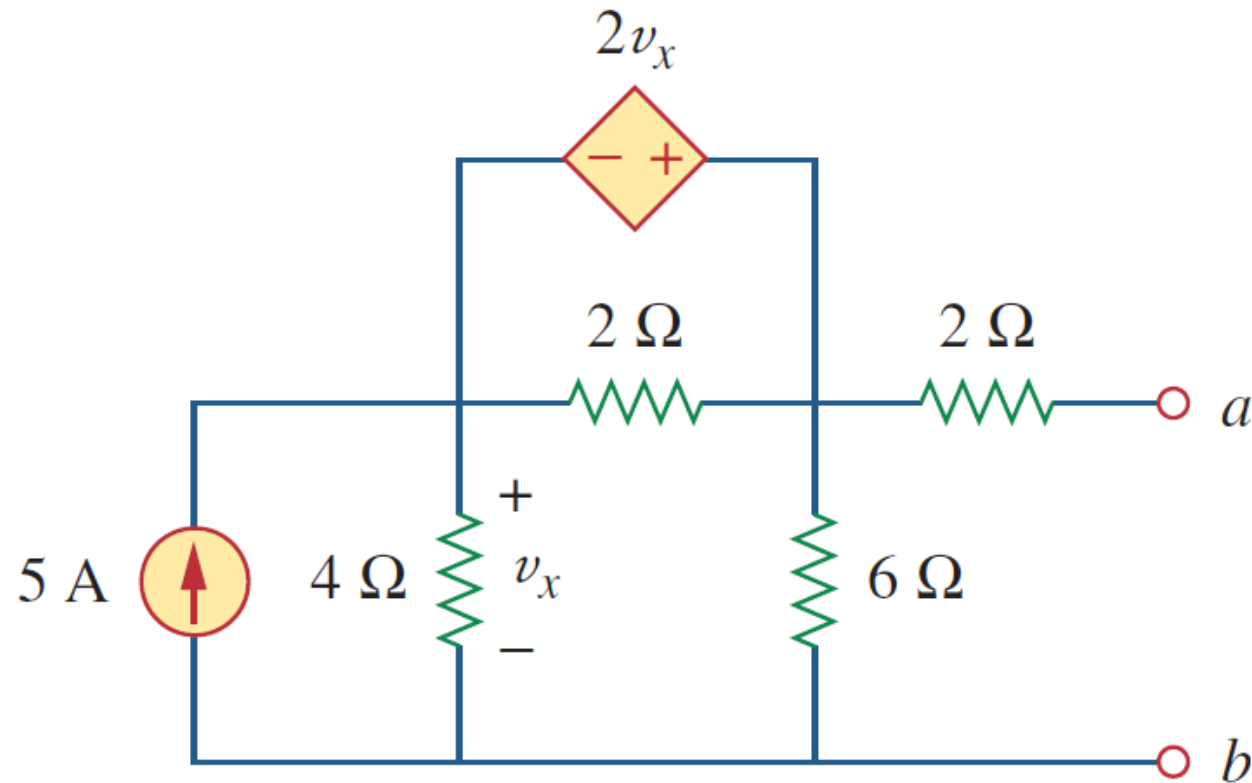Example 4.9

Find the Thevenin equivalent of the circuit in Fig. 4.31 at terminals a - b .



Thevenin Theorem

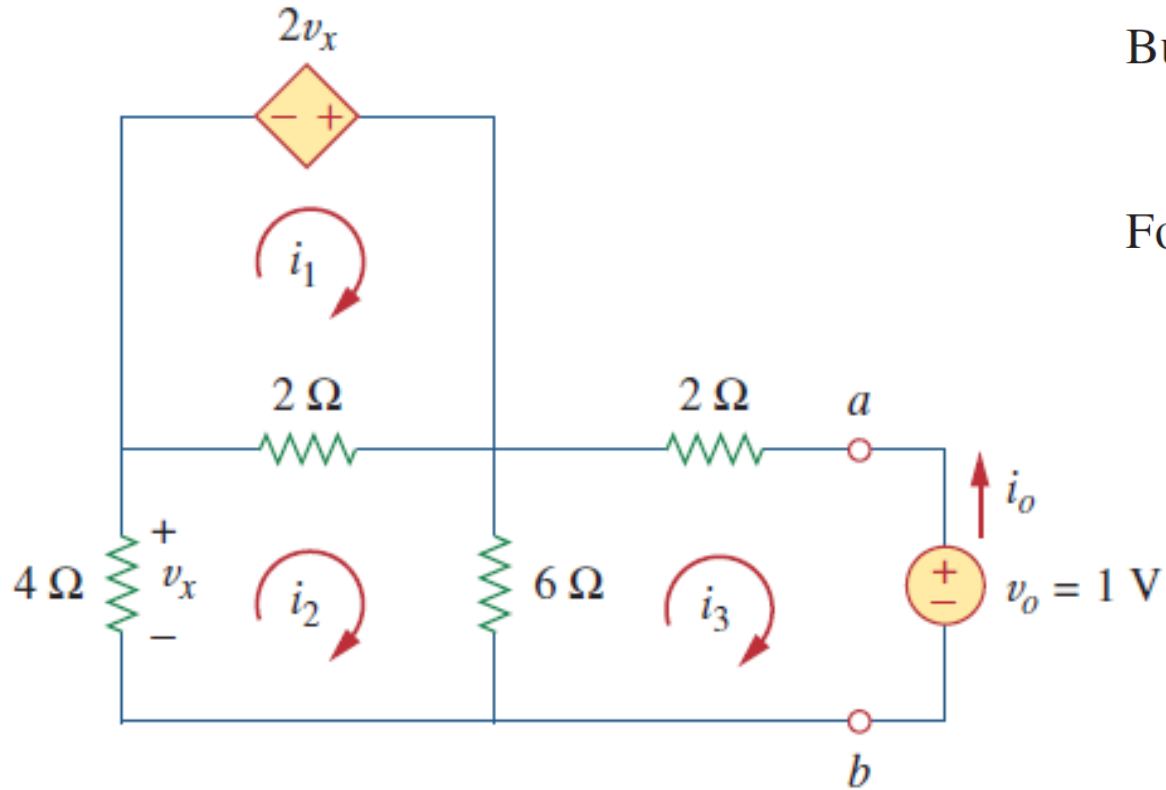

$$-2v_x + 2(i_1 - i_2) = 0 \quad \text{or} \quad v_x = i_1 - i_2$$

But $-4i_2 = v_x = i_1 - i_2$; hence,

$$i_1 = -3i_2$$

For loops 2 and 3, applying KVL produces

$$4i_2 + 2(i_2 - i_1) + 6(i_2 - i_3) = 0$$

$$6(i_3 - i_2) + 2i_3 + 1 = 0$$


Solving these equations gives

$$i_3 = -\frac{1}{6} \text{ A}$$

But $i_o = -i_3 = 1/6 \text{ A}$. Hence,

$$R_{\text{Th}} = \frac{1 \text{ V}}{i_o} = 6 \Omega$$

Thevenin Theorem

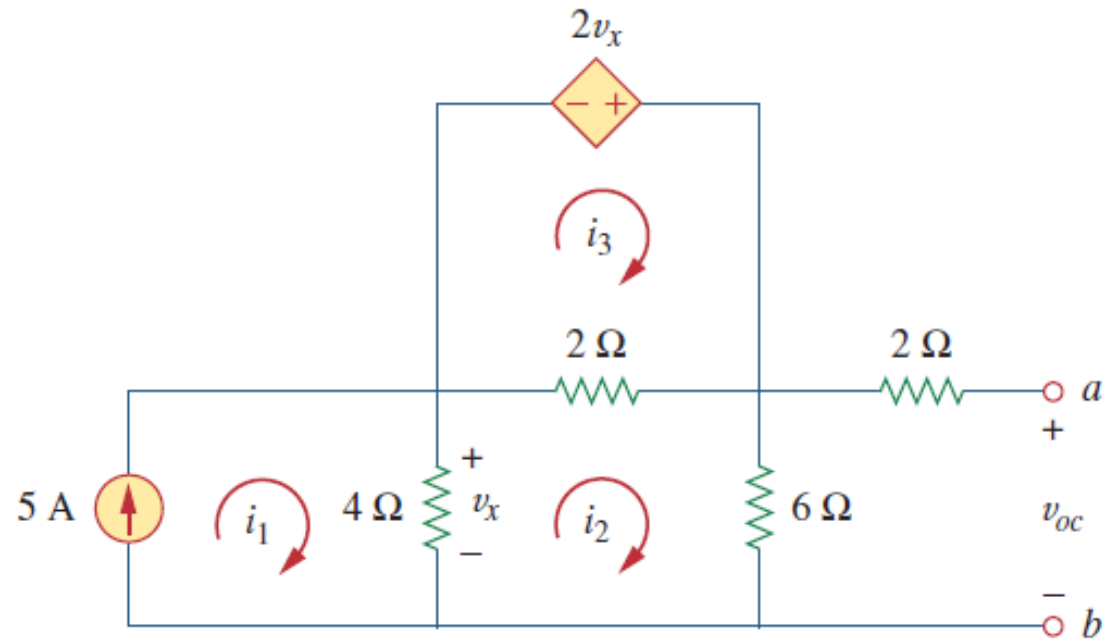

$$i_1 = 5 \quad (4.9.4)$$

$$-2v_x + 2(i_3 - i_2) = 0 \quad \Rightarrow \quad v_x = i_3 - i_2 \quad (4.9.5)$$


$$4(i_2 - i_1) + 2(i_2 - i_3) + 6i_2 = 0$$

or

$$12i_2 - 4i_1 - 2i_3 = 0 \quad (4.9.6)$$

But $4(i_1 - i_2) = v_x$. Solving these equations leads to $i_2 = 10/3$.
Hence,
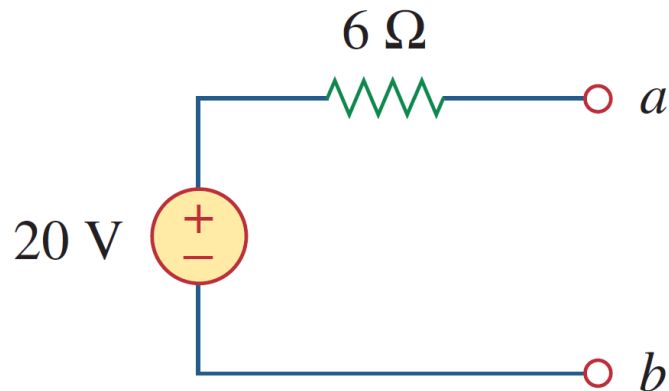
$$V_{Th} = v_{oc} = 6i_2 = 20 \text{ V}$$




Norton Theorem

Norton's theorem states that a linear two-terminal circuit can be replaced by an equivalent circuit consisting of a current source I_N in parallel with a resistor R_N , where I_N is the short-circuit current through the terminals and R_N is the input or equivalent resistance at the terminals when the independent sources are turned off.

The Thevenin and Norton equivalent circuits are related by a source transformation.

Norton Theorem

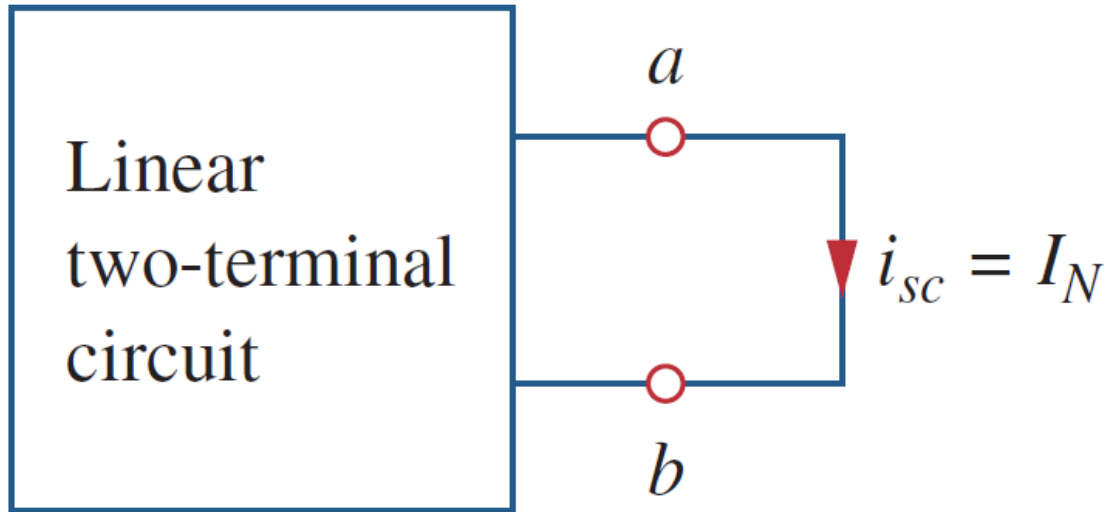

$$V_{Th} = v_{oc}$$

$$I_N = i_{sc}$$



$$R_{Th} = \frac{v_{oc}}{i_{sc}} = R_N$$

$$I_N = \frac{V_{Th}}{R_{Th}}$$

Norton Theorem

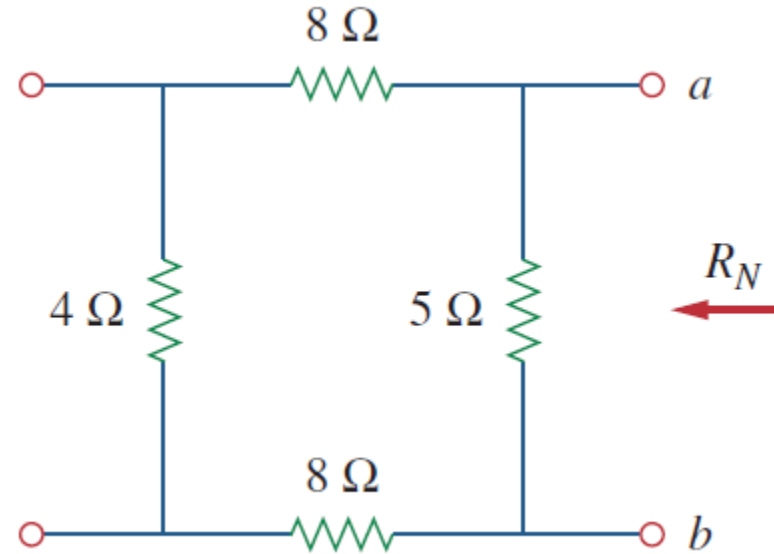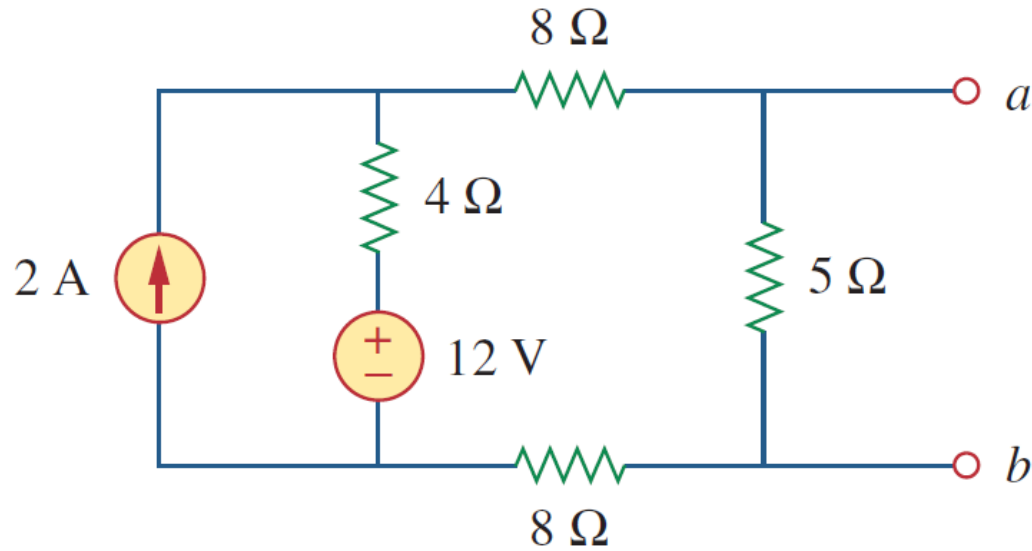
Example 4.11

Find the Norton equivalent circuit of the circuit in terminals a - b .



$$R_N = 5 \parallel (8 + 4 + 8) = 5 \parallel 20 = \frac{20 \times 5}{25} = 4 \Omega$$

Norton Theorem

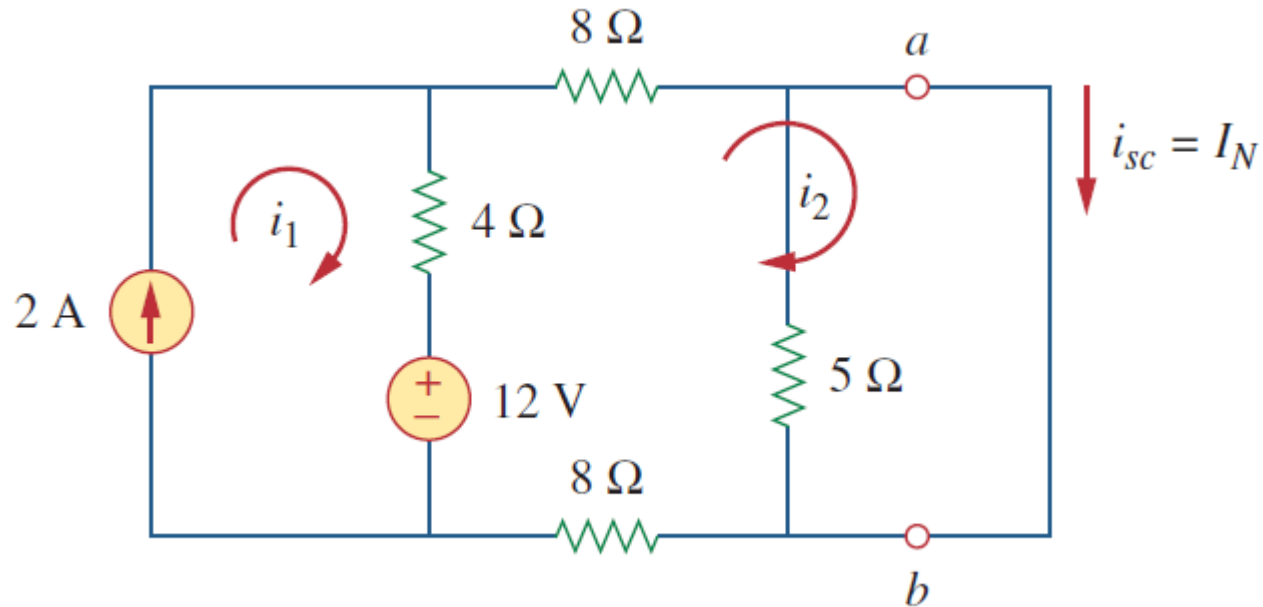



$$i_1 = 2\text{ A}, \quad 20i_2 - 4i_1 - 12 = 0$$

From these equations, we obtain

$$i_2 = 1\text{ A} = i_{sc} = I_N$$

Norton Theorem

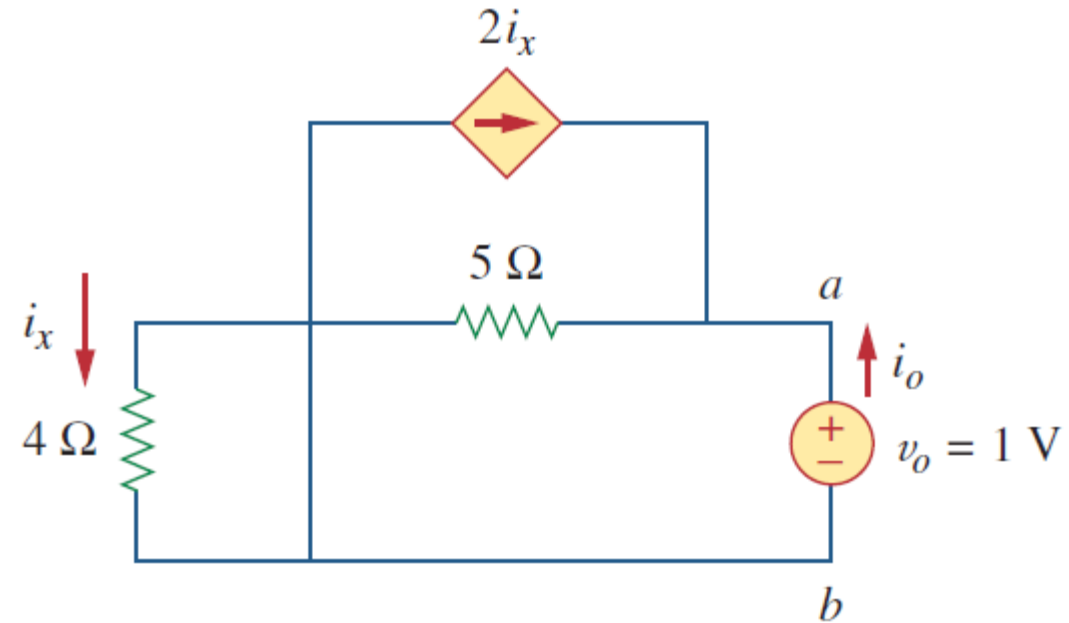
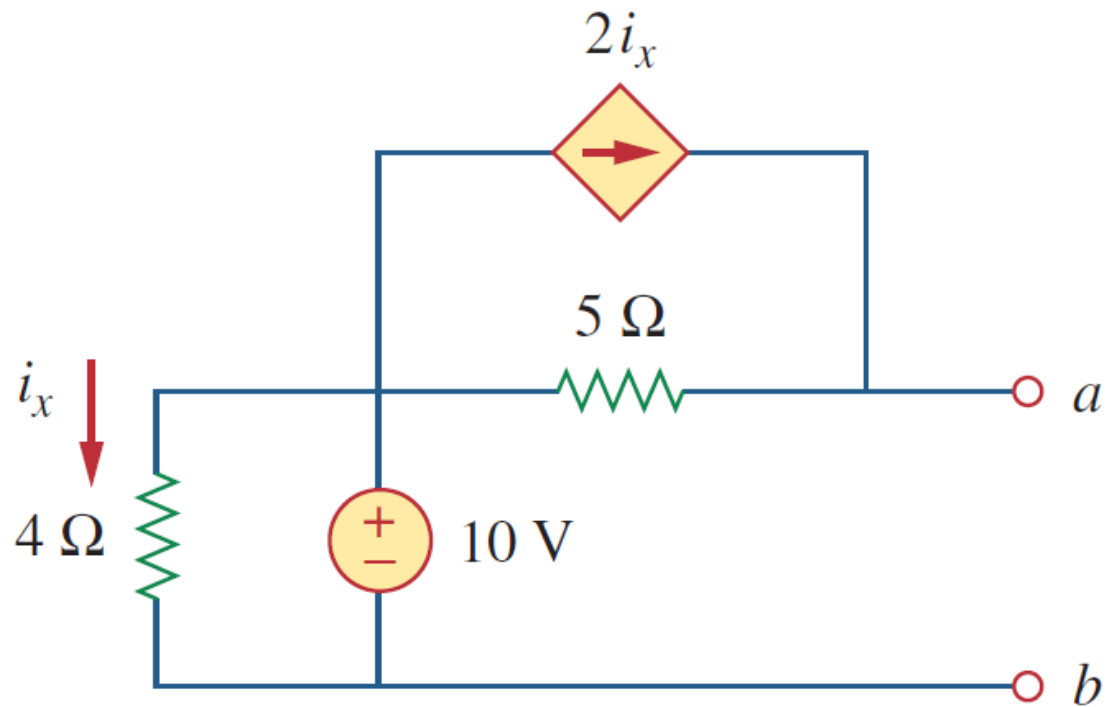
Using Norton's theorem, find R_N and I_N of the circuit in terminals a - b .



Hence, $i_x = 0$. At node a , $i_o = \frac{1V}{5\Omega} = 0.2$ A, and

$$R_N = \frac{v_o}{i_o} = \frac{1}{0.2} = 5 \Omega$$

Norton Theorem

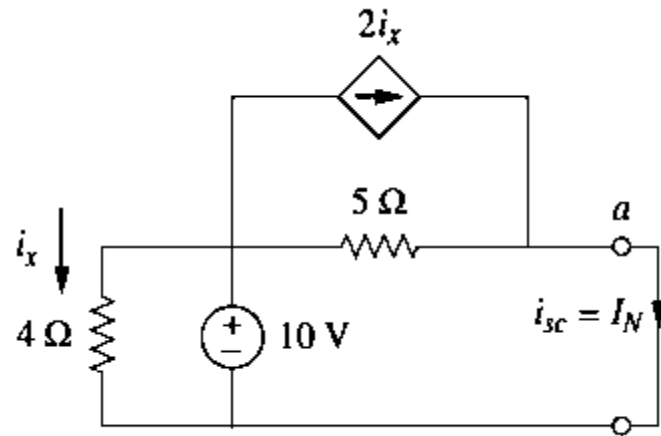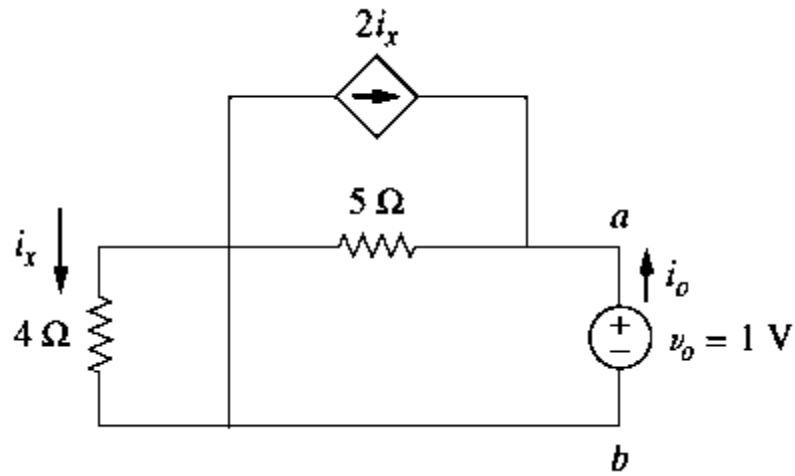

$$i_x = \frac{10}{4} = 2.5 \text{ A}$$

At node a , KCL gives

$$i_{sc} = \frac{10}{5} + 2i_x = 2 + 2(2.5) = 7 \text{ A}$$

Thus,

$$I_N = 7 \text{ A}$$

Maximum Power Transfer theorem


Maximum power is transferred to the load when the load resistance equals the Thevenin resistance .

$$R_L = R_{Th}$$


$$P_{\max} = \frac{V_{Th}^2}{4R_{Th}}$$

Maximum Power Transfer theorem

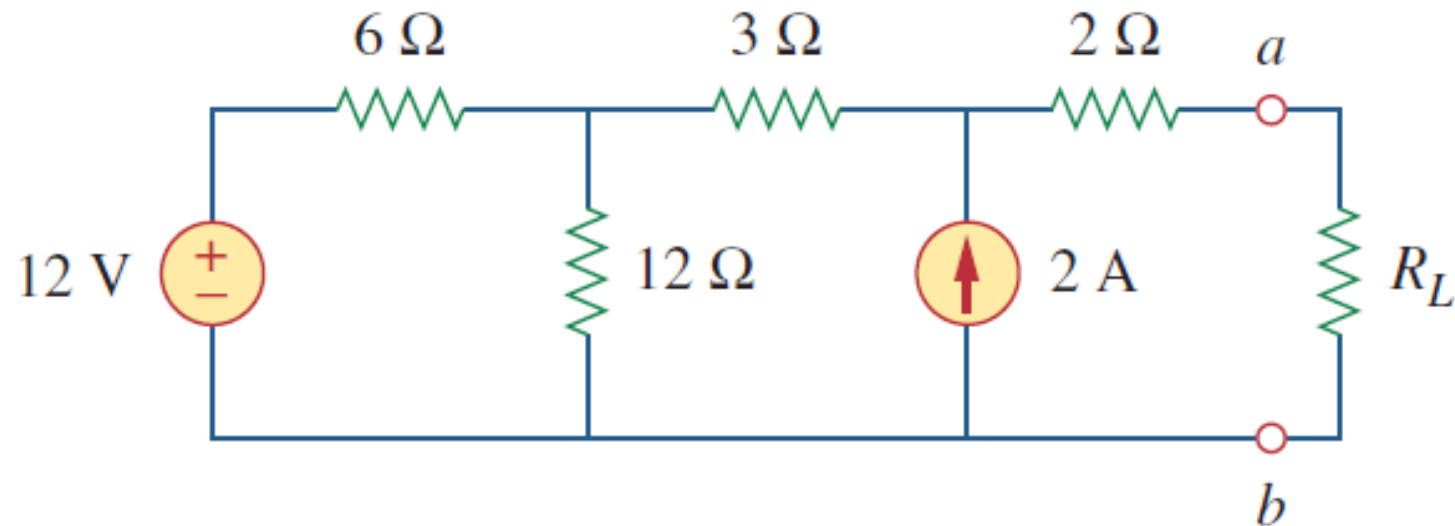Find the value of R_L for maximum power transfer in the circuit of Fig. 4.50. Find the maximum power.



Maximum Power Transfer theorem

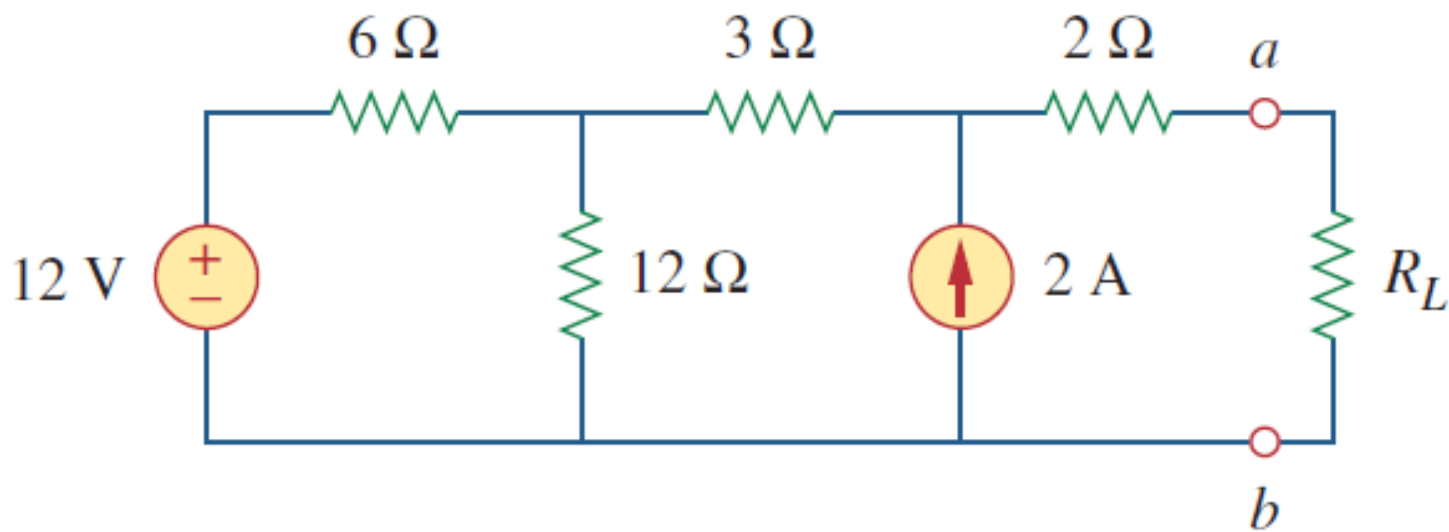

$$R_{Th} = 9 \Omega$$

$$V_{Th} = 22 V$$

$$P_{\max} = \frac{V_{Th}^2}{4R_L} = \frac{22^2}{4 \times 9} = 13.44 \text{ W}$$



THANK YOU