

Lesson 06

Boolean Algebra and Logic Gate

Samsul Alam

Sr. Lecturer, DBA, DIU







Review from Previous Lesson



i Do it!



Today's Class Agenda

-  Axioms
-  Theorems
-  Operation
-  Logic gates
-  Boolean function
-  Truth table



i Do it!



Boolean axioms

- Boolean algebra: an algebraic system of logic introduced by **George Boole** in **1854**.
- The **axioms** (postulates) of an algebra are the basic **assumptions** from which all theorems of the algebra can be proved.
- The axioms are independent; none can be proved from the others.
- Boolean algebra is calculated using only addition and multiplication by following these rules:
 - $0+0=0, 0+1=1, 1+0=1, 1+1=1$
 - $0.0=0, 0.1=0, 1.0=0, 1.1=1$



i Do it!



Theorems

- Theorem 1 (Idempotency)
 - (a) $x + x = x$; (b) $x \cdot x = x$
- Theorem 2
 - (a) $x + 1 = 1$; (b) $x \cdot 0 = 0$
- Theorem 3 (Absorption)
 - (a) $yx + x = x$; (b) $(y + x)x = x$
- Theorem 4 (Involution)
 - $\bar{\bar{x}} = x$
 - $x \bar{x} = 0$
- Theorem 5 (Associativity)
 - (a) $x + (y + z) = (x + y) + z$; (b) $x(yz) = (xy)z$
- Theorem 6 (De Morgan)
 - (a) $\overline{x + y} = \bar{x} \cdot \bar{y}$ (b) $\overline{x \cdot y} = \bar{x} + \bar{y}$
- Theorem 7
 - $E(x_1, x_2, \dots, x_n) = E_d(\bar{x}_1, \bar{x}_2, \dots, \bar{x}_n)$
- Theorem 8 (De Morgan (generalized))
 - $\overline{(x_1 + x_2 + \dots + x_n)} = \bar{x}_1 \bar{x}_2 \dots \bar{x}_n$
 - $\overline{(x_1 \cdot x_2 \cdot \dots \cdot x_n)} = \bar{x}_1 + \bar{x}_2 + \dots + \bar{x}_n$
- Other theorems:
 - $x + \bar{x} = 1$
 - $x + yz = (x + y)(x + z)$



i Do it!



Boolean Algebra Operation

- $$\begin{aligned} & A B + \bar{A} B + A \bar{B} \\ &= B (A + \bar{A}) + A \bar{B} \\ &= B \cdot 1 + A \bar{B} \\ &= B + A \bar{B} \\ &= (B + A) (B + \bar{B}) \\ &= (B + A) \cdot 1 \\ &= A + B \end{aligned}$$

- $$\begin{aligned} & A \bar{B} + \overline{(\bar{A} + B)} + C \bar{C} \\ &= A \bar{B} + \overline{(\bar{A} + B)} + 0 \\ &= A \bar{B} + (\bar{\bar{A}} \cdot \bar{B}) \\ &= A \bar{B} + A B \\ &= A (\bar{B} + B) \\ &= A \cdot 1 \\ &= A \end{aligned}$$

- $$\begin{aligned} X &= \overline{(A + C) (B + D)} \\ &= \overline{(A + C)} + \overline{(B + D)} \\ &= \bar{A} \bar{C} + \bar{B} \bar{D} \\ &= \bar{A} C + B \bar{D} \end{aligned}$$

- $$\begin{aligned} & XY + XZ + \bar{X}Z + ZX \\ &= XY + XZ + \bar{X}Z \\ &= XY + Z (X + \bar{X}) \\ &= XY + Z \cdot 1 \\ &= XY + Z \end{aligned}$$

- $$\begin{aligned} & \bar{X}YZ + X\bar{Y}Z + XY\bar{Z} + XYZ \\ &= (\bar{X}YZ + XYZ) + (X\bar{Y}Z + XYZ) + (XY\bar{Z} + XYZ) \\ &= YZ (\bar{X} + X) + XZ (\bar{Y} + Y) + XY (\bar{Z} + Z) \\ &= YZ \cdot 1 + XZ \cdot 1 + XY \cdot 1 \\ &= YZ + XZ + XY \end{aligned}$$



i Do it!



Boolean Algebra Operation...

- Prove the following equations:

- $XYZ + XY\bar{Z} + X\bar{Y}Z + X\bar{Y}\bar{Z} = C$

$$\text{L.H.S} = XYZ + XY\bar{Z} + X\bar{Y}Z + X\bar{Y}\bar{Z}$$

$$= XY\bar{Z} + XY\bar{Z} + X\bar{Y}\bar{Z}$$

$$= XZ (\bar{Y} + Y) + X\bar{Y}\bar{Z}$$

$$= XZ \cdot 1 + X\bar{Y}\bar{Z}$$

$$= XZ + X\bar{Y}\bar{Z}$$

$$= Z (X + \bar{X})$$

$$= C \cdot 1$$

$$= C = \text{R.H.S.}$$

L.H.S. = R.H.S. (Proved)

- $\overline{(M + N)(M + N)} = \bar{M}\bar{N} + MN$

- L.H.S. = $\overline{(M + N)(M + N)}$

$$= \overline{(M + N)} + \overline{(M + N)}$$

$$= \bar{M}\bar{N} + \bar{M}\bar{N}$$

$$= \bar{M}\bar{N} + MN = \text{R.H.S.}$$

- L.H.S. = R.H.S. (Proved)

$$(X + Y)(\bar{X} + Z)(Y + Z) = (X + Y)(\bar{X} + Z)$$

- L.H.S. = $(X + Y)(\bar{X} + Z)(Y + Z)$

$$= (X\bar{X} + XZ + Y\bar{X} + YZ)(Y + Z)$$

$$= (0 + XZ + Y\bar{X} + YZ)(Y + Z)$$

$$= (XZ + Y\bar{X} + YZ)(Y + Z)$$

$$= XYZ + X\bar{Y}Y + YYZ + XZZ + X\bar{Y}Z + YZZ$$

$$= XYZ + Y\bar{X} + YZ + XZ + X\bar{Y}Z + YZ$$

$$= XYZ + Y\bar{X} + YZ + XZ + X\bar{Y}Z$$

$$= YZ(1 + \bar{X} + X) + X\bar{Y} + XZ$$

$$= YZ + X\bar{Y} + XZ$$

- R.H.S. = $(X + Y)(\bar{X} + Z)$

$$= X\bar{X} + XZ + \bar{X}Y + YZ$$

$$= 0 + XZ + \bar{X}Y + YZ$$

$$= YZ + \bar{X}Y + XZ$$

$$= \text{R.H.S.}$$

L.H.S. = R.H.S. (Proved)



i Do it!



Exercise

1. $X = \overline{(A + B + C) B C}$
2. $(A + \bar{A}B) + (A + B)$
3. $\overline{X(X + Y) \cdot Y(Y + X)}$
4. $(\bar{B}\bar{C} + \bar{A}\bar{D})(\bar{A}\bar{B} + \bar{C}\bar{D})$
5. $\overline{(A + B + C) \bar{B} \bar{C}}$

Prove the following equations:

1. $A + \bar{A}B + \bar{A}\bar{B} = 1$
2. $\overline{(A + B + CD)} = \bar{A}\bar{B}(\bar{C} + D)$
3. $\overline{(A + B)} \overline{(A + B)} = 0$
4. $(X + Y + Z) \bar{Y}\bar{Z} = X \bar{Y}\bar{Z}$
5. $XYZ + X \bar{Y}\bar{Z} + X Y \bar{Z} = X(Y + C)$
6. $\overline{(A + C)} + \overline{(B + D)} = A \bar{C} + \bar{B} D$



i Do it!



Answer key

1. $\bar{A} + B + \bar{C}$
2. $A + B$
3. $\bar{X} \cdot \bar{Y}$
4. 0
5. 0



i Do it!



Logic gate






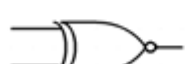

Logic gates are the basic building blocks of any digital system. It is an **electronic circuit** having one or more than one input and only one output. The relationship between the input and the output is based on a certain **logic**. Based on this, logic gates are named as **AND** gate, **OR** gate, **NOT** gate etc.



i Do it!



Logic gate...

Logic Gate	Symbol	Description	Boolean
AND		Output is at logic 1 when, and only when all its inputs are at logic 1, otherwise the output is at logic 0.	$X = A \cdot B$
OR		Output is at logic 1 when one or more are at logic 1. If all inputs are at logic 0, output is at logic 0.	$X = A + B$
NAND		Output is at logic 0 when, and only when all its inputs are at logic 1, otherwise the output is at logic 1	$X = \overline{A \cdot B}$
NOR		Output is at logic 0 when one or more of its inputs are at logic 1. If all the inputs are at logic 0, the output is at logic 1.	$X = \overline{A + B}$
XOR		Output is at logic 1 when one and Only one of its inputs is at logic 1. Otherwise is it logic 0.	$X = A \oplus B$
XNOR		Output is at logic 0 when one and only one of its inputs is at logic 1. Otherwise it is logic 1. Similar to XOR but inverted.	$X = \overline{A \oplus B}$
NOT		Output is at logic 0 when its only input is at logic 1, and at logic 1 when its only input is at logic 0. That's why it is called and INVERTER	$X = \overline{A}$



i Do it!



Boolean Function using Digital Circuit

- **Boolean Expression/Function**

Example: $F(x, y) = x + y'z$


- **Truth Table**

All possible combinations of input variables

- **Logic Circuit**



x	y	z	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

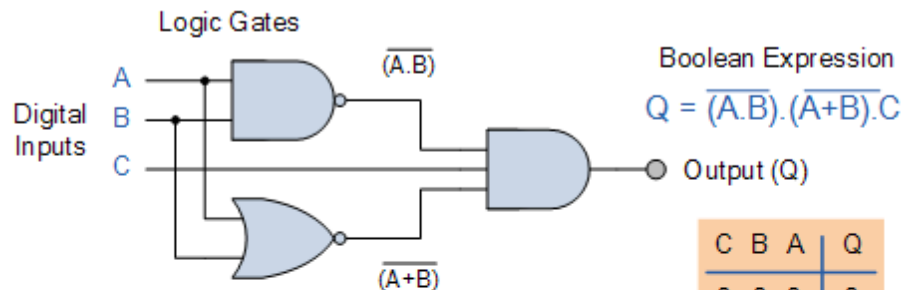

Typical Truth Table

C	B	A	Q
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	0

For Exercise:

$$Y = \bar{A} B \overline{(A + C)}$$

$$X = \bar{A} \bar{B} + C$$

$$X = \bar{A} + \bar{B} + C$$

$$X = (A + B) C$$

$$X = (A + \bar{A} B + (A + B))$$

$$X = A \bar{B} + \bar{C}$$


$$Y = A + BC$$

$$F = \bar{A} \bar{B} . \bar{B} \bar{C} . \bar{C} \bar{A}$$




i Do it!

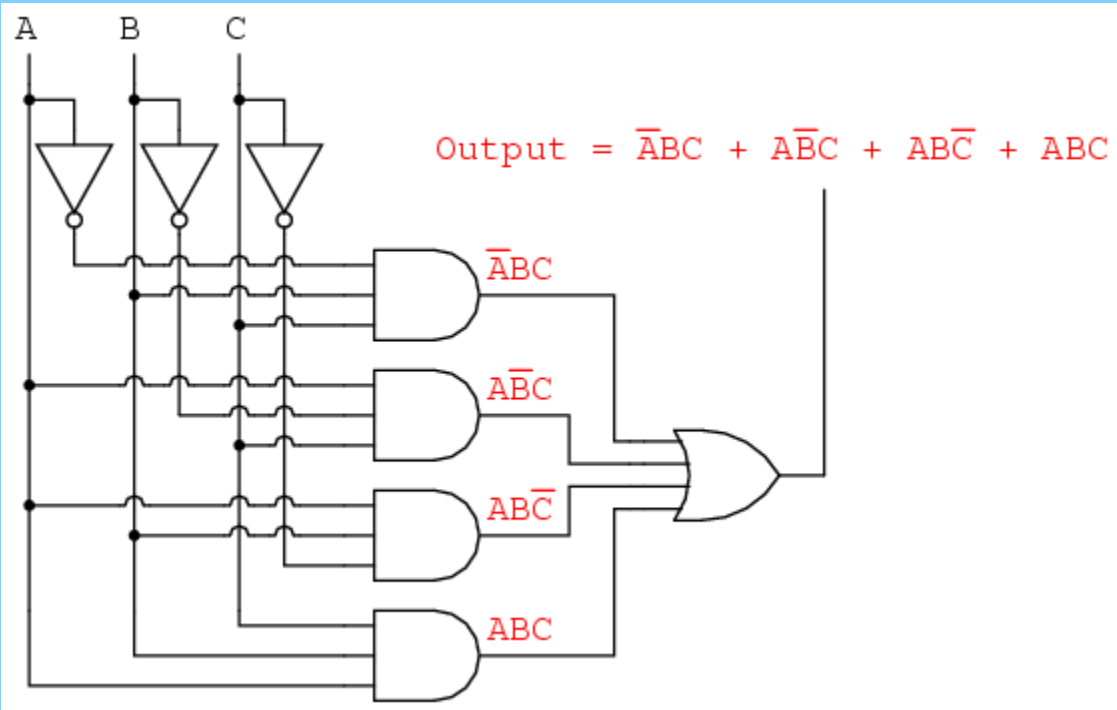Boolean Function using Digital Circuit...



For Exercise:

$$YCi + XCi + XY$$

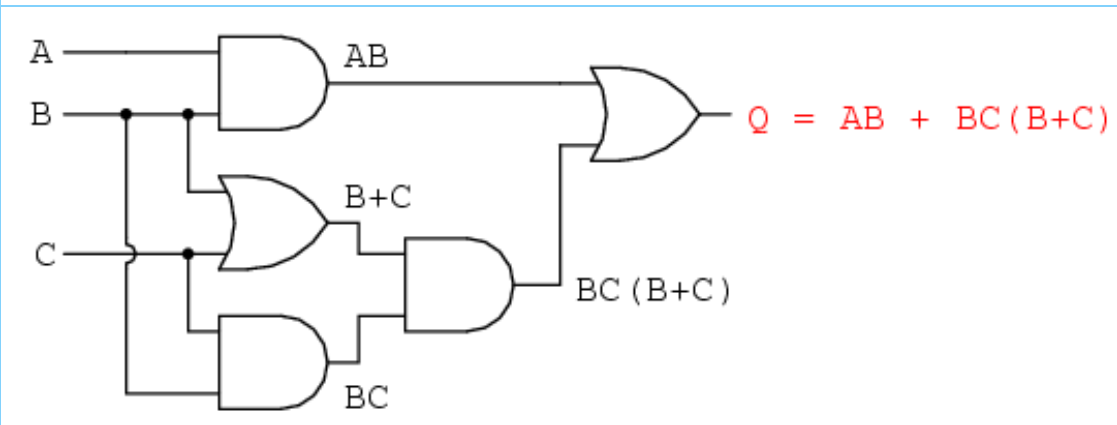

i Do it!



Truth table

- Any boolean function can be represented by a truth table. The number of rows in the table is 2^n , where n is the number of variables in the function.
- $X = (A + \bar{B}) C$

A	B	C	\bar{B}	$A + \bar{B}$	$X = (A + \bar{B}) C$
0	0	0	1	1	0
0	0	1	1	1	1
0	1	0	0	0	0
0	1	1	0	0	0
1	0	0	1	1	0
1	0	1	1	1	1
1	1	0	0	1	0
1	1	1	0	1	1



i Do it!



References

- Peter Norton, M. (2004). *Peter Norton's intro to computers 6/E*. McGraw-Hill Education.
- Rahman, M. L., Kaiser, M. S., Rahman, M. A., & Hossain, M. A. (2017). *Computer Fundamentals and ICT* (1st ed.). Daffodil International University Press.
- Different sites found in internet



Next Lesson: Lesson 07 on Types of Storage Devices

- Based on today's discussion, activity will be assigned to you. You have to make a solution to the problem.**
- At the end there will be a short assessment test based on Lecture lesson-06**



Discussion Questions and Learning Summary!





The End of Lesson-6

Thanks!