



Daffodil
International
University

Microwave Engineering

ETE 415

LECTURE 4
SMITH CHART

The Smith Chart

- It was developed by **Phillip H. Smith** in the 1930s.
- Began its existence as a very useful **graphical calculator** for the analysis and design of TLs.
- Remains a useful tool today to visualize the results of TL analysis, oftentimes combined with computer analysis and visualization as an aid in design.
- Based on the **normalized TL impedance** defined as

$$\tilde{z} \equiv \frac{Z(z)}{Z_0} = \frac{1 + \Gamma(z)}{1 - \Gamma(z)}$$

where \tilde{z} is the total TL impedance at z and

$$\Gamma(z) = \frac{\tilde{z} - 1}{\tilde{z} + 1} = \Gamma_L e^{+j2\beta z}$$

generalized reflection coefficient at z .

Substituting $\Gamma(z) \equiv \Gamma_r(z) + j\Gamma_i(z)$, gives

$$\tilde{z} = \frac{1 + \Gamma(z)}{1 - \Gamma(z)} \Rightarrow \tilde{z}(z) = \frac{1 + (\Gamma_r + j\Gamma_i)}{1 - (\Gamma_r + j\Gamma_i)}$$

The Smith Chart

- Now, we will define $\tilde{z}(z) \equiv r + jx$ and separate the above equation into its real and imaginary parts

$$\begin{aligned}\tilde{z}(z) \equiv r + jx &= \frac{1 + (\Gamma_r + j\Gamma_i)}{1 - (\Gamma_r + j\Gamma_i)} \cdot \frac{1 - (\Gamma_r + j\Gamma_i)^*}{1 - (\Gamma_r + j\Gamma_i)^*} \\ &= \frac{1 + j2\Gamma_i - (\Gamma_r^2 + \Gamma_i^2)}{1 - 2\Gamma_r + \Gamma_r^2 + \Gamma_i^2}\end{aligned}$$

- Equating the real and imaginary parts

$$r = \frac{1 - (\Gamma_r^2 + \Gamma_i^2)}{(1 - \Gamma_r)^2 + \Gamma_i^2} \quad \text{and} \quad x = \frac{2\Gamma_i}{(1 - \Gamma_r)^2 + \Gamma_i^2} \quad \triangle!$$

- Rearranging both of these leads us to the final two equations

$$\left(\Gamma_r - \frac{r}{1+r}\right)^2 + \Gamma_i^2 = \left(\frac{1}{1+r}\right)^2$$

resistance circles

$$(\Gamma_r - 1)^2 + \left(\Gamma_i - \frac{1}{x}\right)^2 = \left(\frac{1}{x}\right)^2$$


reactance circles

The Smith Chart: Resistance Circles

Plot (4) in the $\Gamma_r - \Gamma_i$ plane:


$$\left(\Gamma_r - \frac{r}{1+r}\right)^2 + \Gamma_i^2 = \left(\frac{1}{1+r}\right)^2$$

Complex $\Gamma(z)$ plane

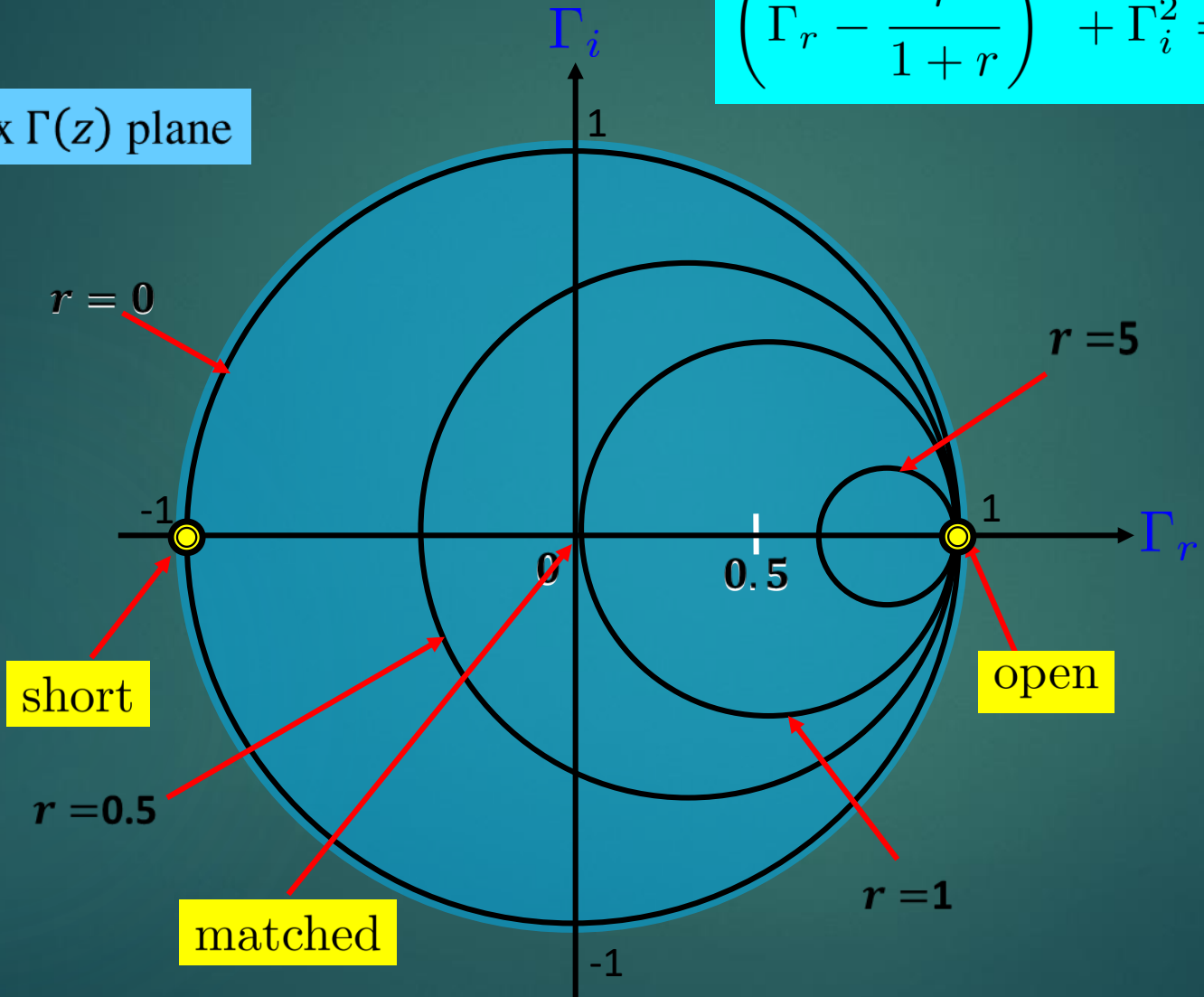

resistance circles have centers lying on the Γ_r axis (with $\Gamma_i = 0$) 4

The Smith Chart: Resistance Circles

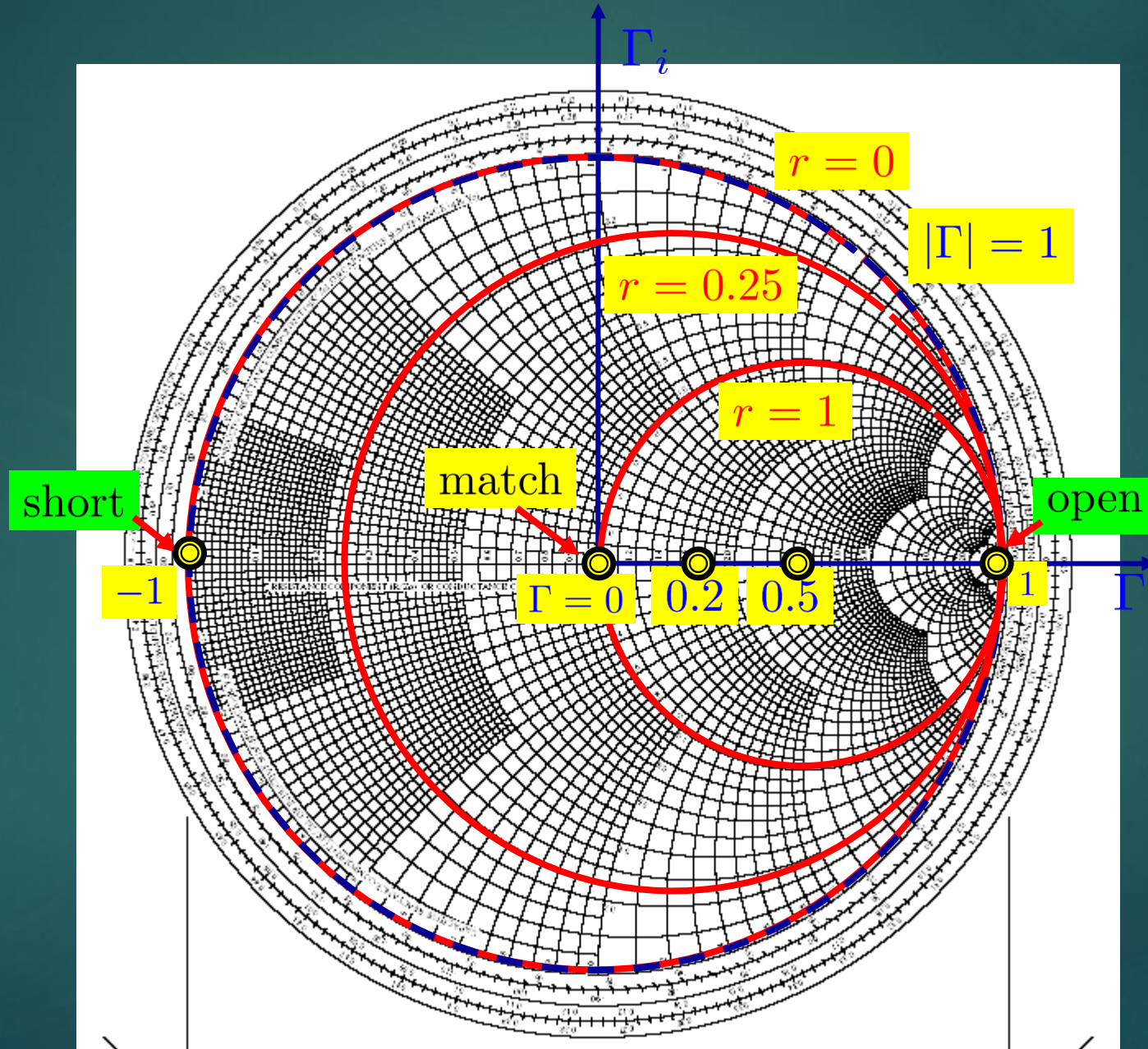


The Smith Chart: Reactance Circles


Plot (5) in the $\Gamma_r - \Gamma_i$ plane:

$$(\Gamma_r - 1)^2 + \left(\Gamma_i - \frac{1}{x}\right)^2 = \left(\frac{1}{x}\right)^2$$

Complex $\Gamma(z)$ plane

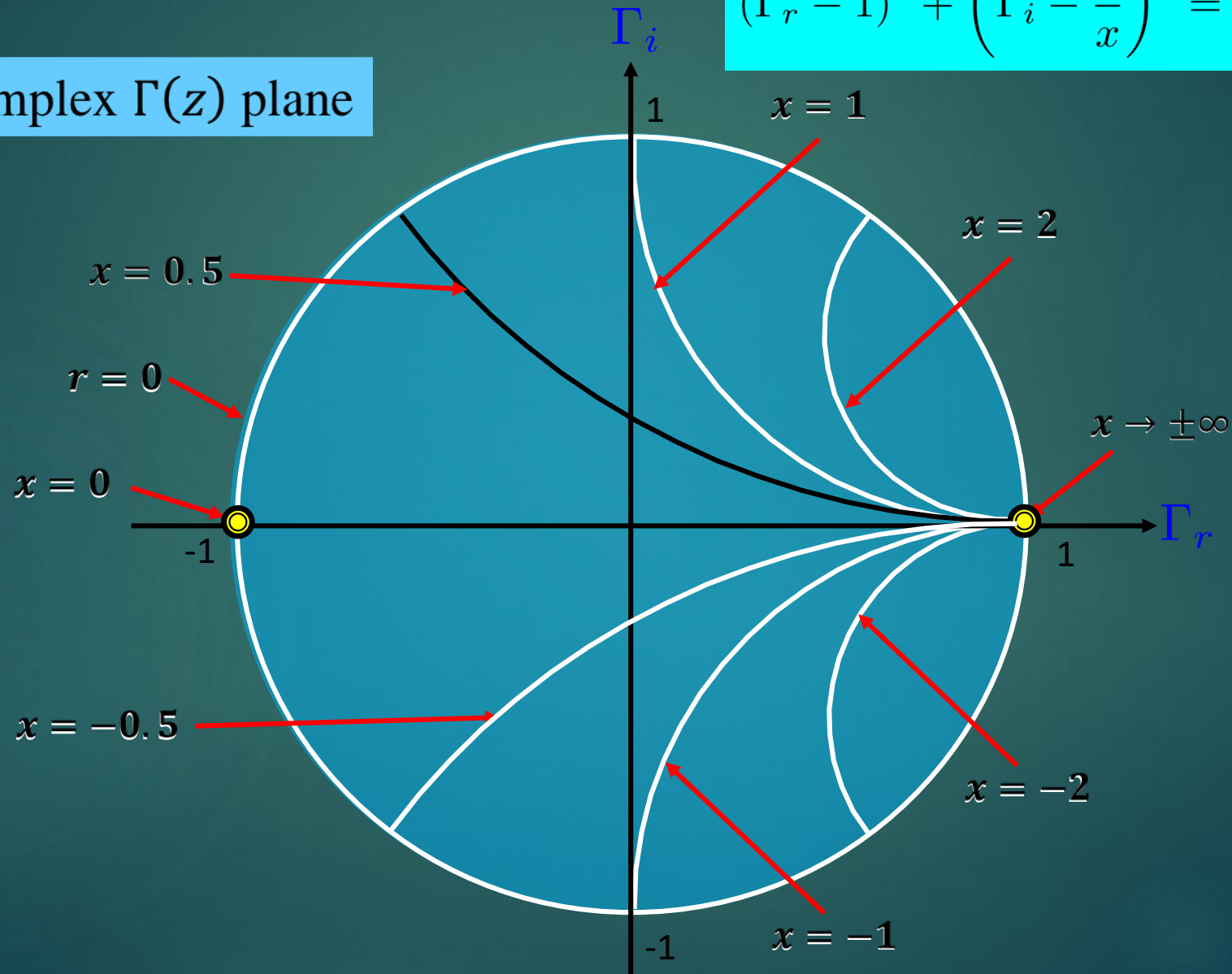

The Smith Chart: Reactance Circles

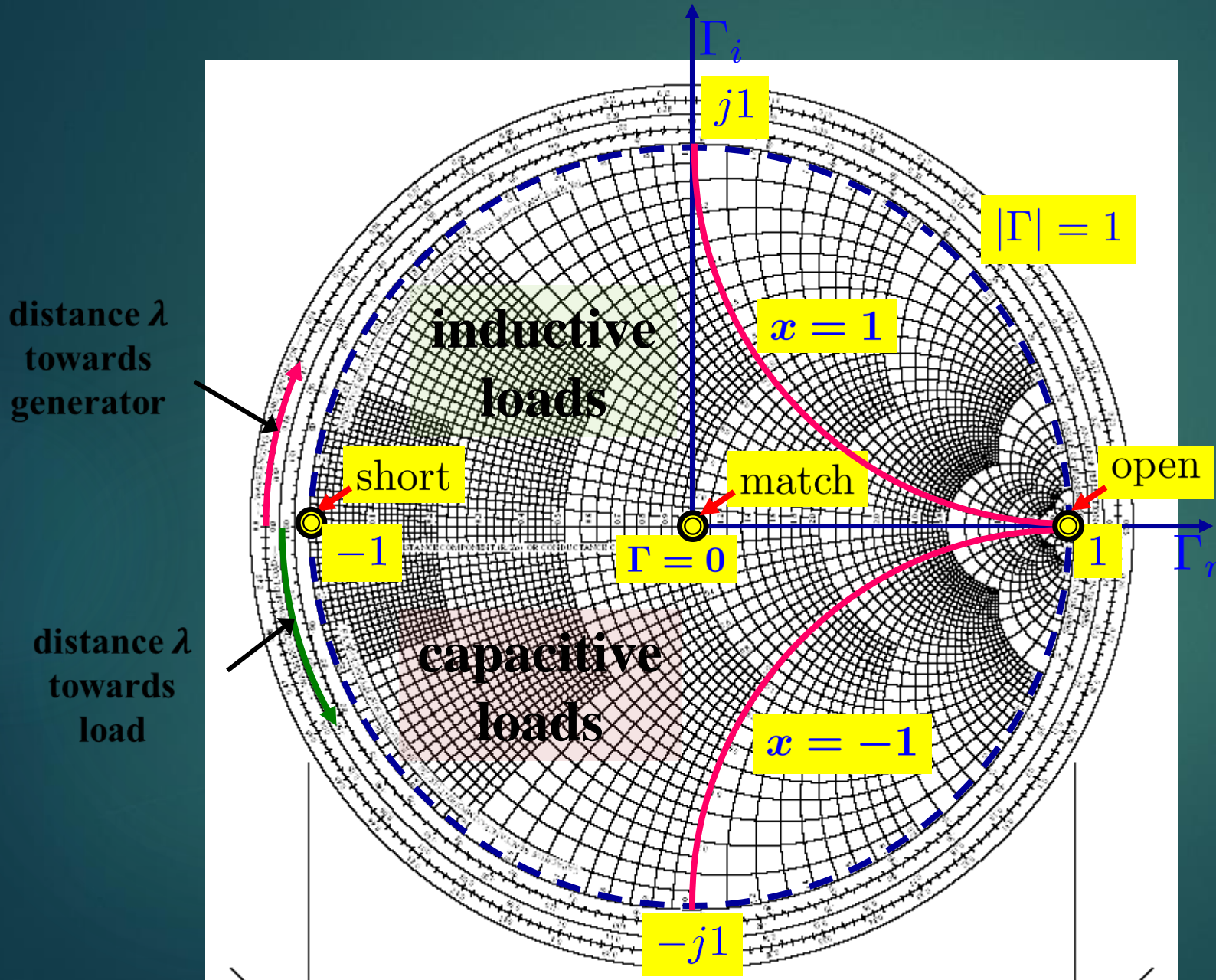

The Smith Chart: Nomographs

At the bottom of Smith chart (**left side**), nomograph is added to read out with a ruler the following


➔ **(1st ruler) above:** SWR

below: SWR in dB, $20 \log_{10} \text{SWR}$

➔ **(2nd ruler) above:** return loss in dB, $-20 \log_{10} |\Gamma|$

below: power reflection $|\Gamma|^2(P)$

➔ **(3rd ruler) above:** reflection coefficient $|\Gamma|$ (E or I)

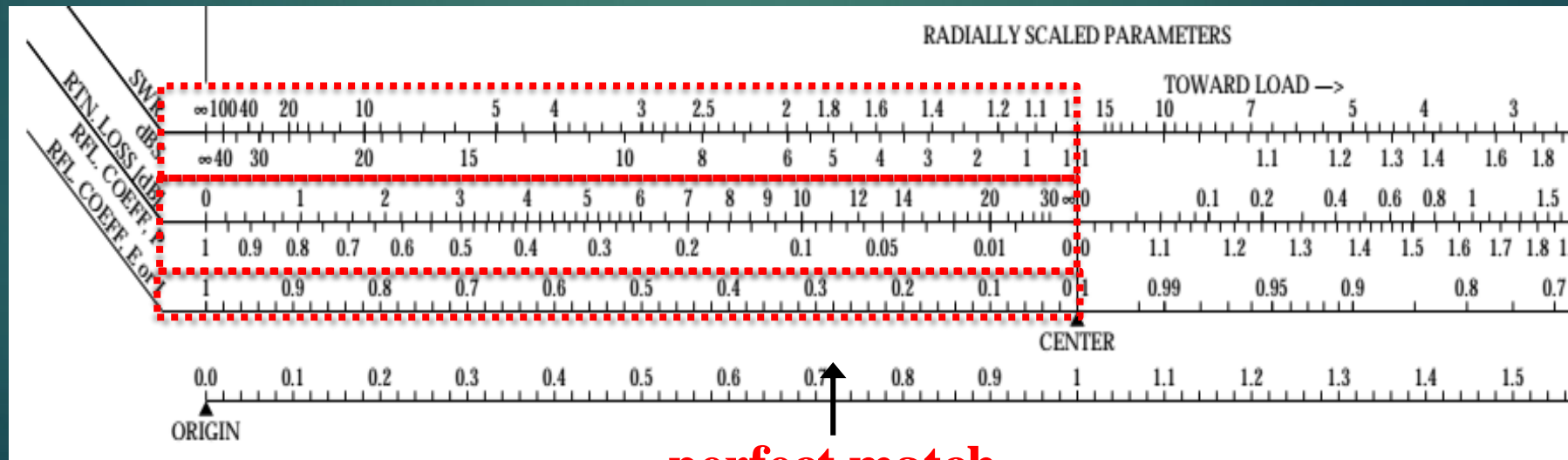

perfect match

Given $Z(-\ell) \Rightarrow$ Find $\Gamma(-\ell)$

- Normalize the impedance

$$\tilde{z}(-\ell) = \frac{Z(-\ell)}{Z_0} = \frac{R}{Z_0} + j \frac{X}{Z_0} = r + jx$$

- Find the circle of constant **normalized resistance r** .
- Find the arc of constant **normalized reactance x** .
- The **intersection** of the two curves indicates the reflection coefficient in the complex plane.

The chart provides directly the magnitude and the phase angle of $\Gamma(-\ell)$.

- Example:** Find $\Gamma(-\ell)$, given

$$Z(-\ell) = 25 + j100 \Omega \text{ with } Z_0 = 50 \Omega$$

1. Normalization

$$\tilde{z}(-\ell) = (25 + j100)/50 = 0.5 + j2.0$$


3. Find normalized reactance arc $x = 2.0$

2. Find normalized resistance circle $r = 0.5$

4. This vector represents the reflection coefficient

$$|\Gamma(-\ell)| = 0.8246$$
$$\angle\Gamma(-\ell) = 50.906^\circ$$

3rd ruler $|\Gamma|$

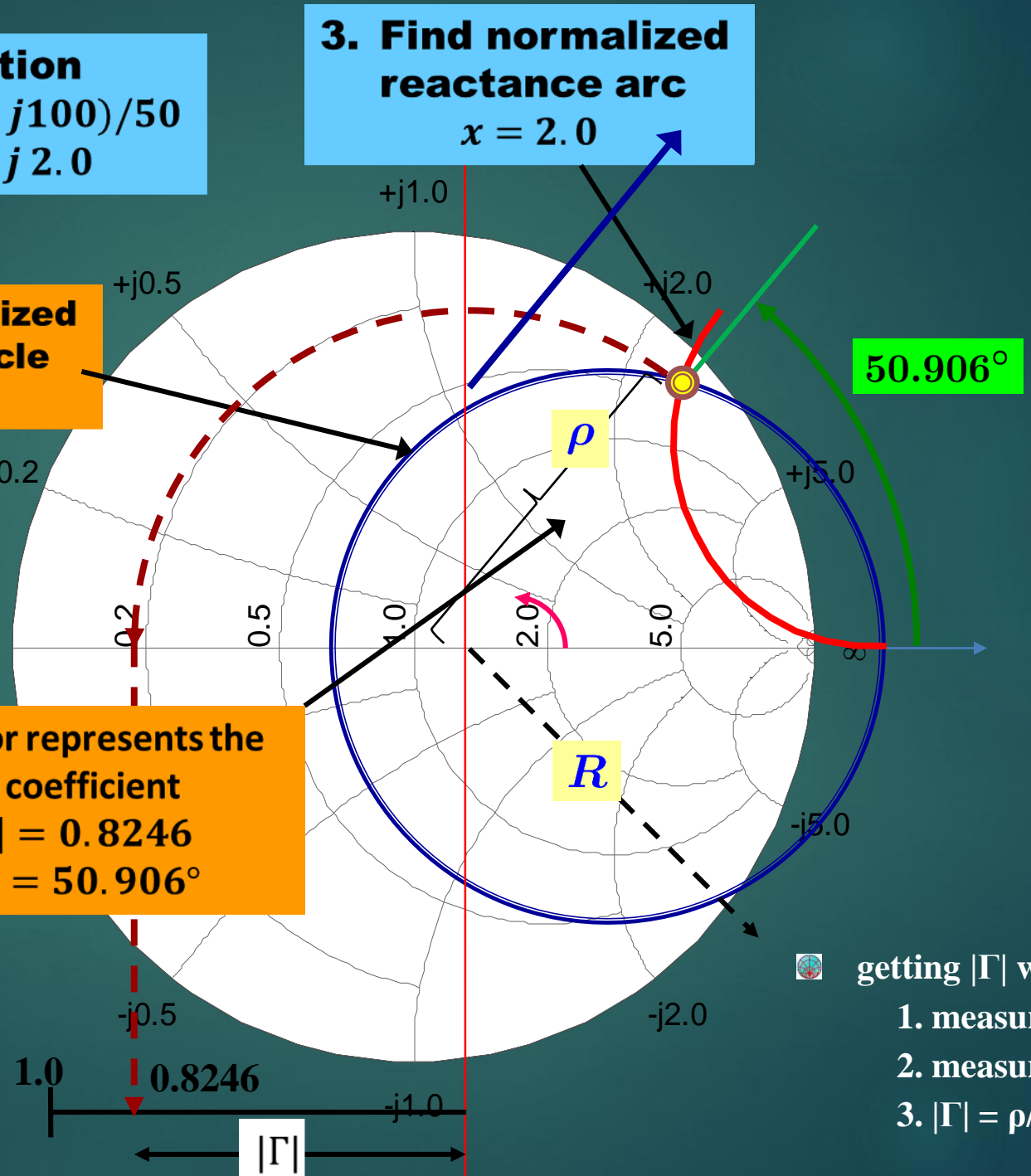

- getting $|\Gamma|$ with a ruler:
1. measure R
 2. measure ρ
 3. $|\Gamma| = \rho/R$

Plotting Γ and Reading Out Impedance


- Determine the complex point representing the given reflection coefficient $\Gamma(-\ell)$ on the chart.
- Read the values of the normalized resistance r and of the normalized reactance x that correspond to the reflection coefficient point.
- The normalized impedance is

$$\tilde{z}(-\ell) = r + jx$$


and the actual impedance is

$$Z(-\ell) = Z_0 \tilde{z}(-\ell) = Z_0(r + jx)$$

Example: $\Gamma = 0.62 \angle 83^\circ$

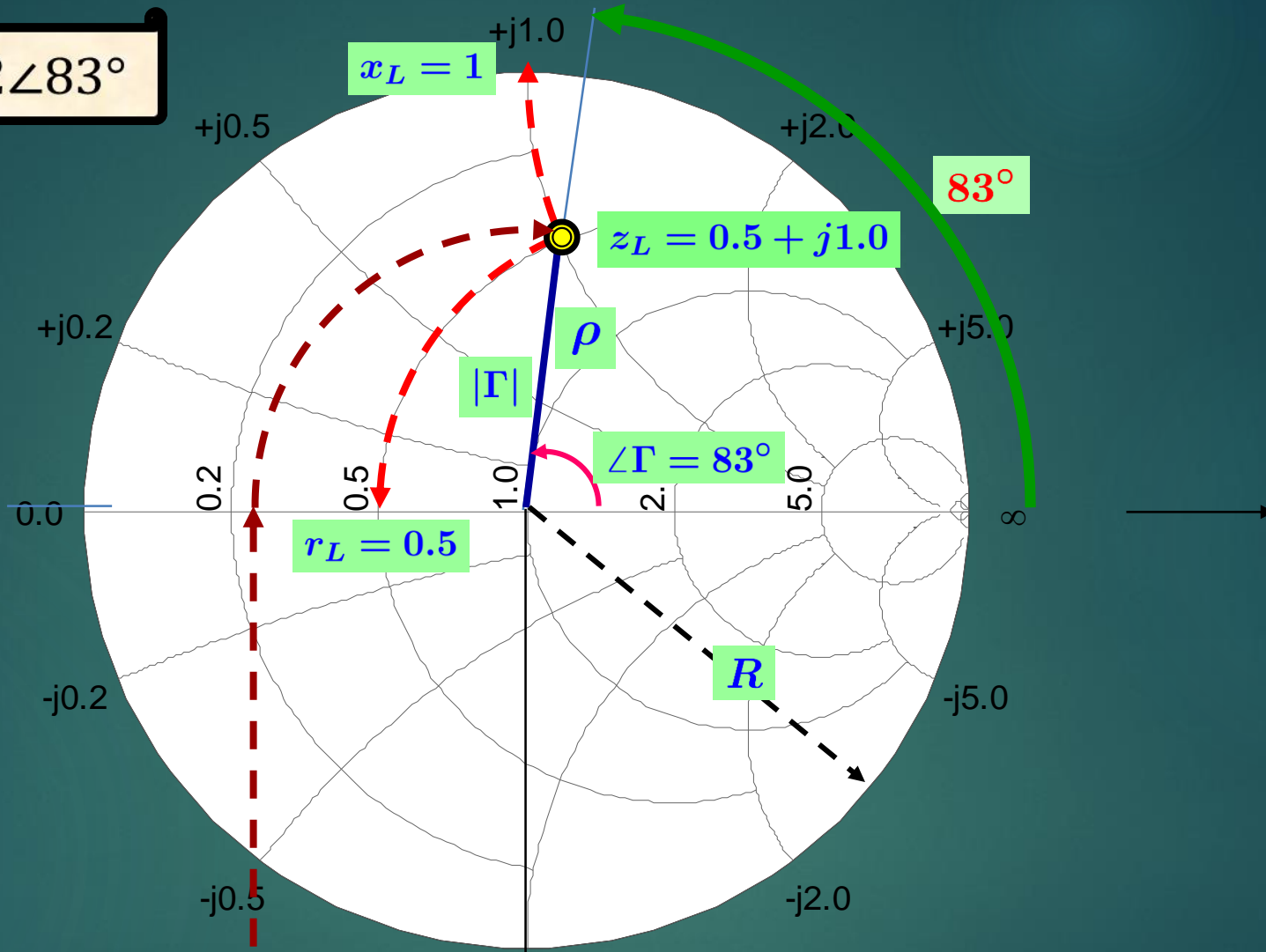

3rd ruler

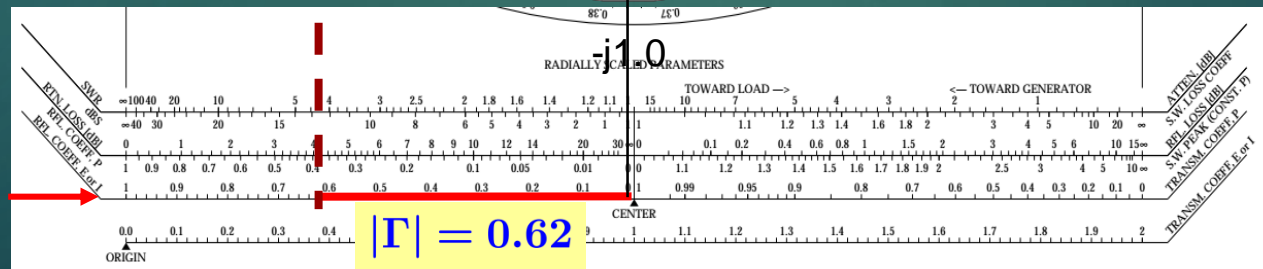

Tracking Impedance Changes with ℓ

■ At $z = -\ell$, $\Gamma(-\ell) = \Gamma_L e^{-j2\beta\ell}$

■ **NOTE:** the magnitude of the reflection coefficient is constant along a loss-less TL terminated by a specified load, since

$$|\Gamma(-\ell)| = |\Gamma_L e^{-j2\beta\ell}| = |\Gamma_L|$$

$$Z(-\ell) = Z_0 \frac{1 + \Gamma_L e^{-j2\beta\ell}}{1 - \Gamma_L e^{-j2\beta\ell}} \Rightarrow \tilde{z}(-\ell) = \frac{1 + \Gamma_L e^{-j2\beta\ell}}{1 - \Gamma_L e^{-j2\beta\ell}}$$

■ compare with at load ($z = 0$)


$$\tilde{z}_L(0) = \frac{1 + \Gamma_L}{1 - \Gamma_L}$$

■ on Smith chart, the point corresponding to $\tilde{z}(-\ell)$ is rotated by $-2\beta\ell$ (**decreasing angle, clockwise rotation**) with respect to the point corresponding to $\tilde{z}(0)$ along the circle of $|\Gamma(-\ell)| = |\Gamma_L|$ (**toward generator**).



Example: $Z_L = 25 + j100 \Omega$, $Z_0 = 50 \Omega$. Find $Z(-\ell)$, $\Gamma(-\ell)$ for $\ell = 0.18\lambda$

Circle with constant $|\Gamma|$

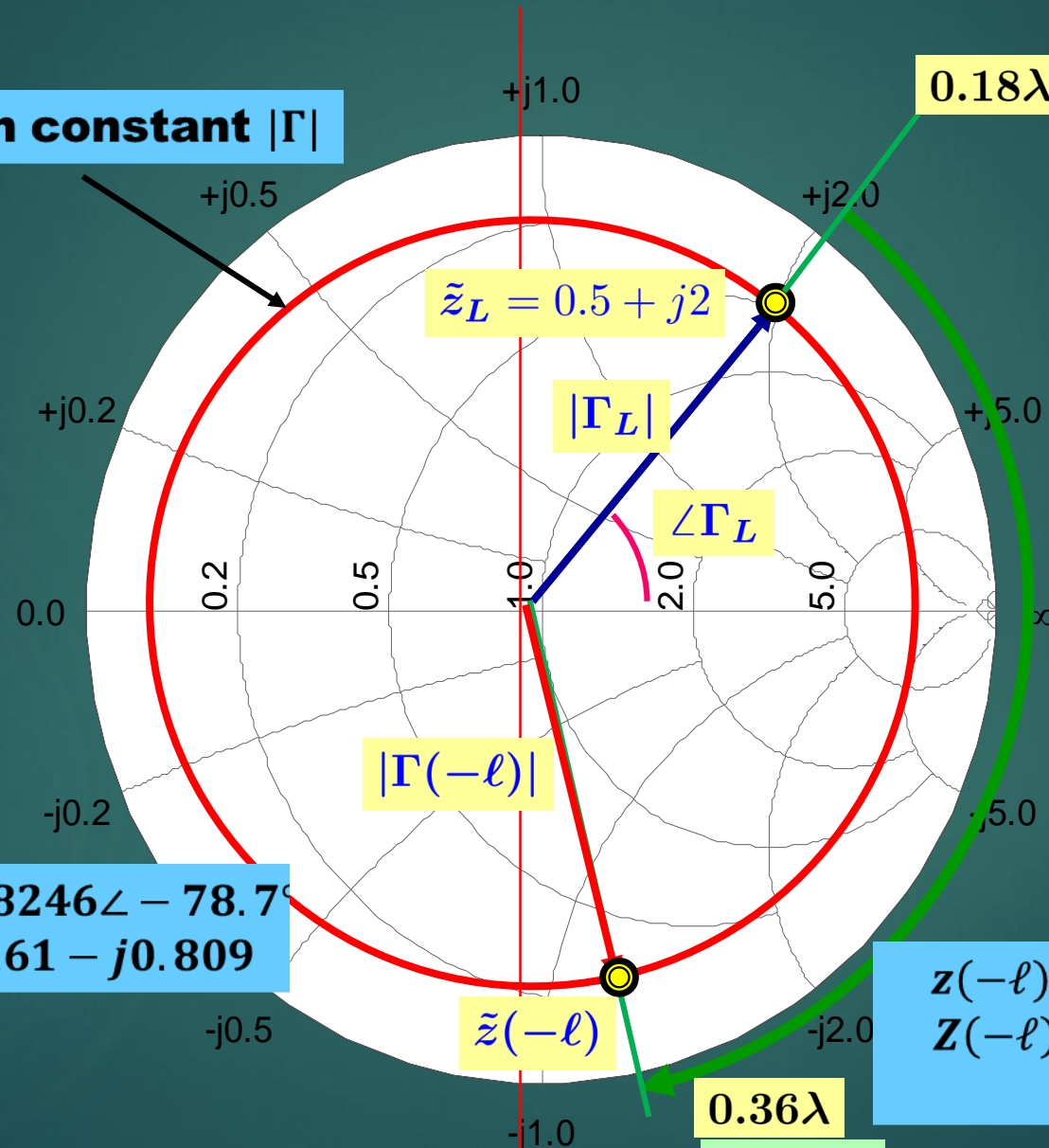

$$\begin{aligned} \theta &= 2\beta\ell \\ &= 2 \frac{2\pi}{\lambda} 0.18\lambda \\ &= 2.262 \text{ rad} \\ &= 129.6^\circ \end{aligned}$$

$$\begin{aligned} |\Gamma(-\ell)| &= 0.8246 \angle -78.7^\circ \\ &= 0.161 - j0.809 \end{aligned}$$

$$\begin{aligned} z(-\ell) &= 0.236 - j1.192 \\ Z(-\ell) &= z(-\ell) \times Z_0 \\ &= 11.79 - j59.6 \Omega \end{aligned}$$

Read Out Distance to Load


Known load
 $Z_L = 75 + j75 \Omega$

Known
 $Z_0 = 50 \Omega$

Measured
 $Z_{in} = 23 - j34 \Omega$

Unknown distance
 to load in terms of λ
 $D_n = D/\lambda$
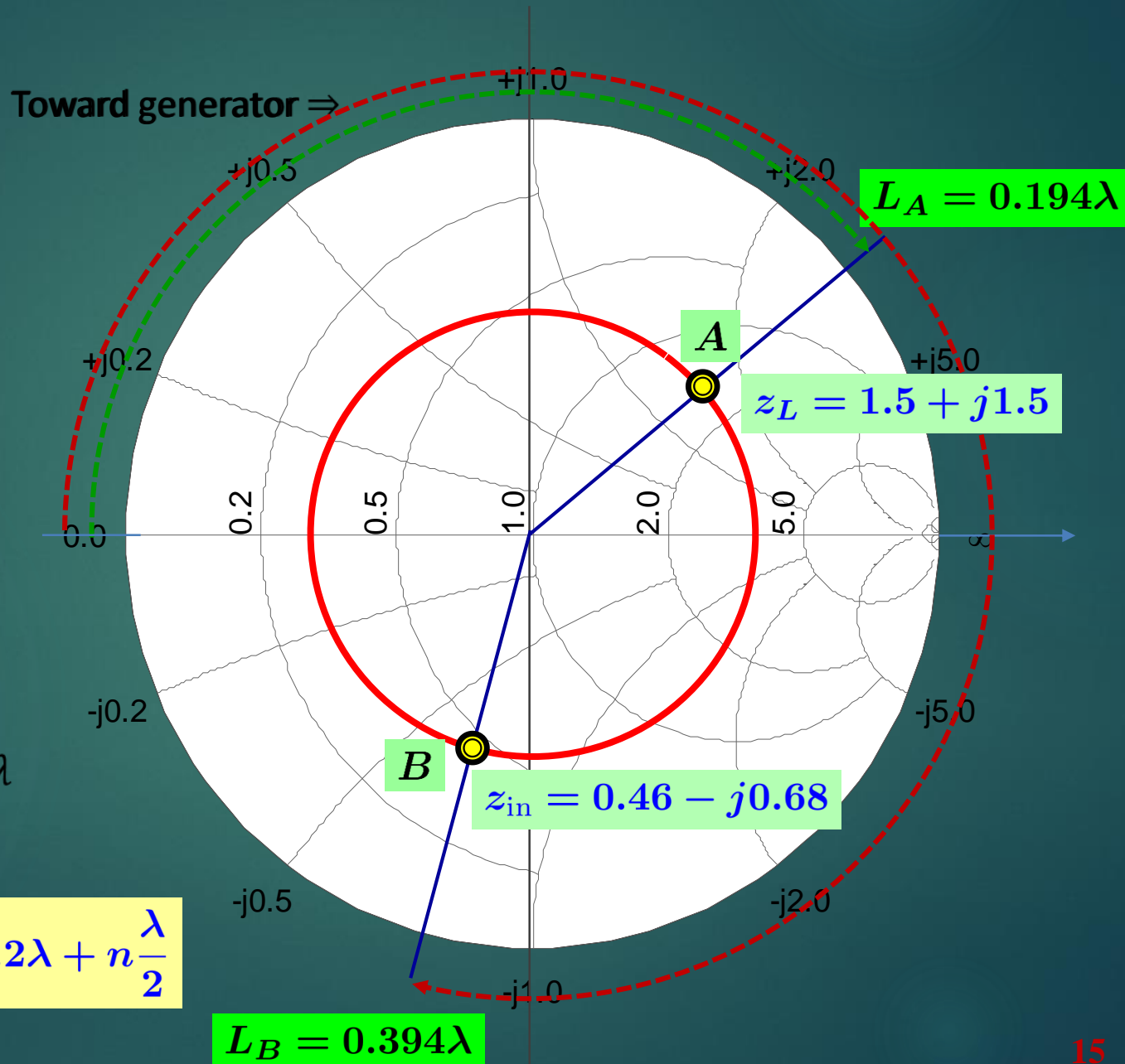
$$D_n = L_B - L_A = 0.2\lambda + n\frac{\lambda}{2}$$



Given Γ_L and $Z_L \Rightarrow$ Find VSWR

✎ The **VSWR** is defined as

$$\text{VSWR} = \frac{V_{\max}}{V_{\min}} = \frac{1 + |\Gamma_L|}{1 - |\Gamma_L|}$$

✎ The normalized impedance at a maximum location of the standing wave pattern is given by


$$\tilde{z}(-\ell_{\max}) = \frac{1 + \Gamma(-\ell_{\max})}{1 - \Gamma(-\ell_{\max})} = \frac{1 + |\Gamma_L|}{1 - |\Gamma_L|} = \text{VSWR}$$



✎ This quantity is always real and ≥ 1 .

The VSWR is simply obtained on the Smith chart, by reading the value of the **(real) normalized impedance**, at the **location** ℓ_{\max} where is real and positive.

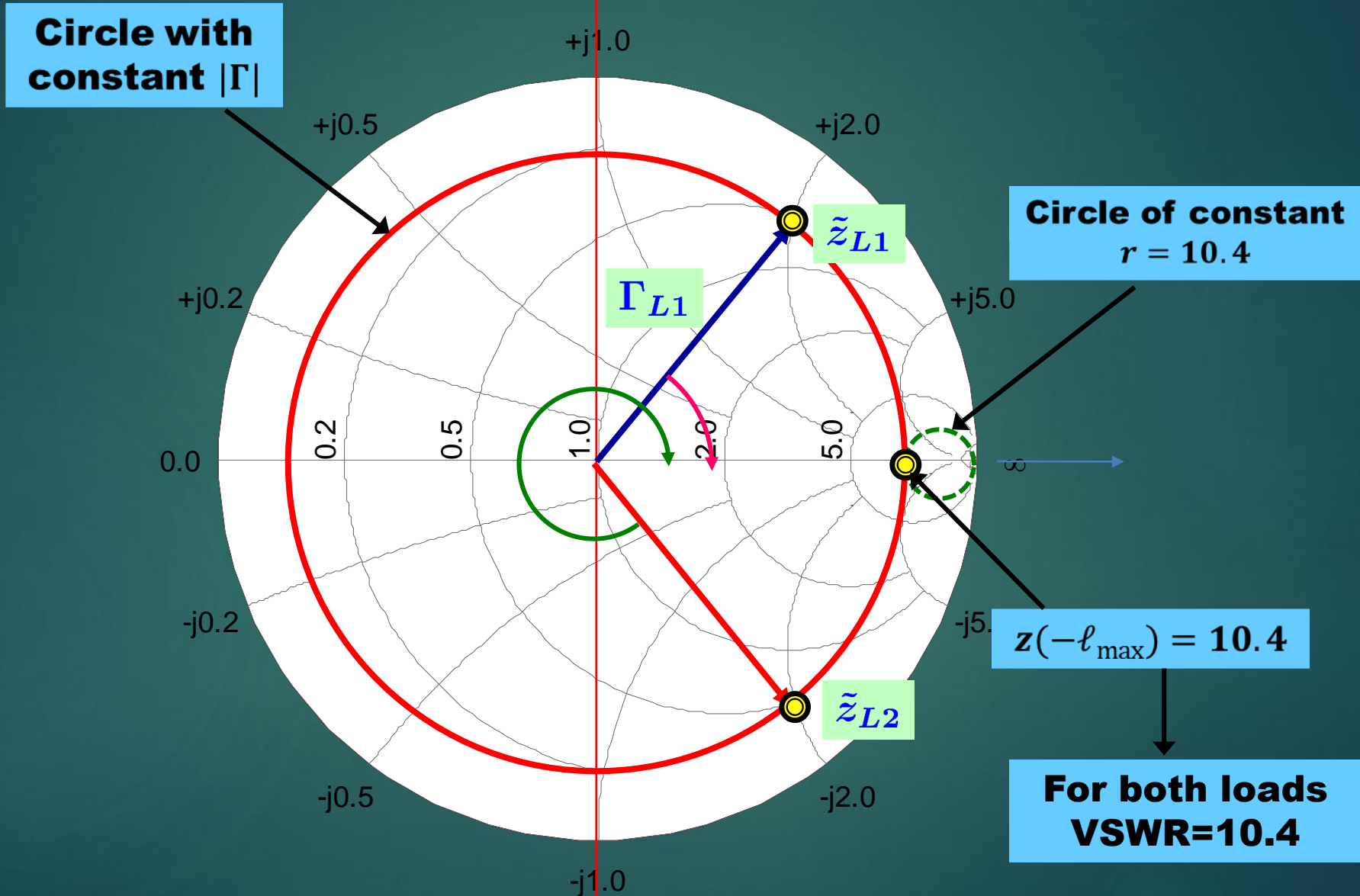Find the VSWR for $Z_{L1} = 25 + j100 \Omega$; $Z_{L2} = 25 - j100 \Omega$, $Z_0 = 50 \Omega$




Given Γ_L and $Z_L \Rightarrow$ Find ℓ_{max} and ℓ_{min}

- Identify on the Smith chart the **load reflection coefficient** Γ_L or the **normalized load impedance** Z_L .
- Draw the circle of **constant reflection coefficient amplitude** $|\Gamma(-\ell)| = |\Gamma_L|$. The circle intersects the real axis of the reflection coefficient at two points which identify ℓ_{max} (when $\Gamma(-\ell)$ Real positive) and ℓ_{min} (when $\Gamma(-\ell)$ Real negative).
- The **angles**, between the vector Γ_L and the real axis, also provide a way to compute ℓ_{max} and ℓ_{min} .

Find ℓ_{\max} and ℓ_{\min} for $Z_L = 25 + j100 \Omega$, $Z_0 = 50 \Omega$

$\Im m(Z_L) > 0$

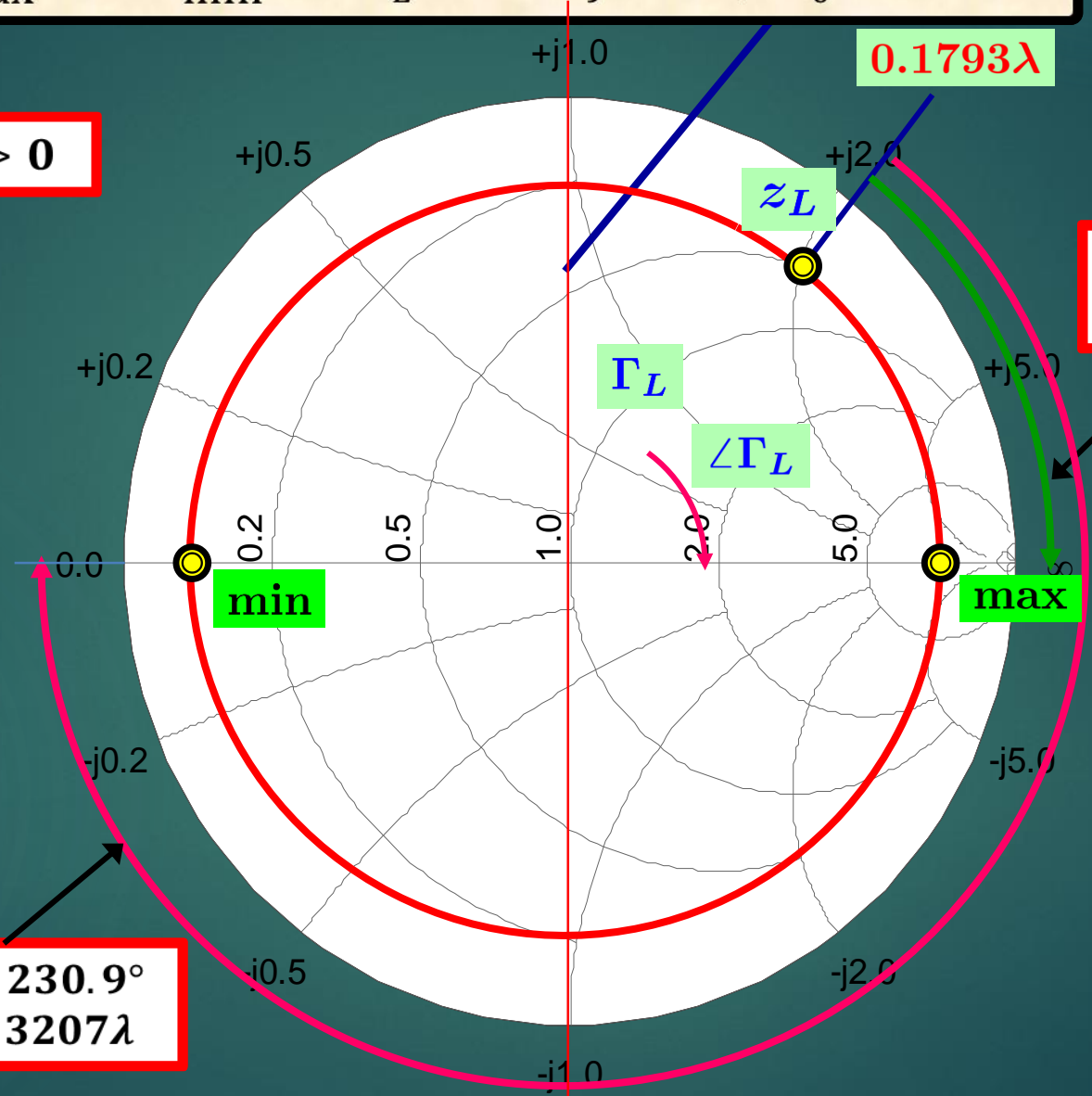

0.1793λ


$2\beta\ell_{\max} = 50.9^\circ$
 $\ell_{\max} = 0.0707\lambda$

$2\beta\ell_{\min} = 230.9^\circ$
 $\ell_{\min} = 0.3207\lambda$

Find ℓ_{\max} and ℓ_{\min} for $Z_L = 25 - j100 \Omega$, $Z_0 = 50 \Omega$

$\Im m(Z_L) < 0$

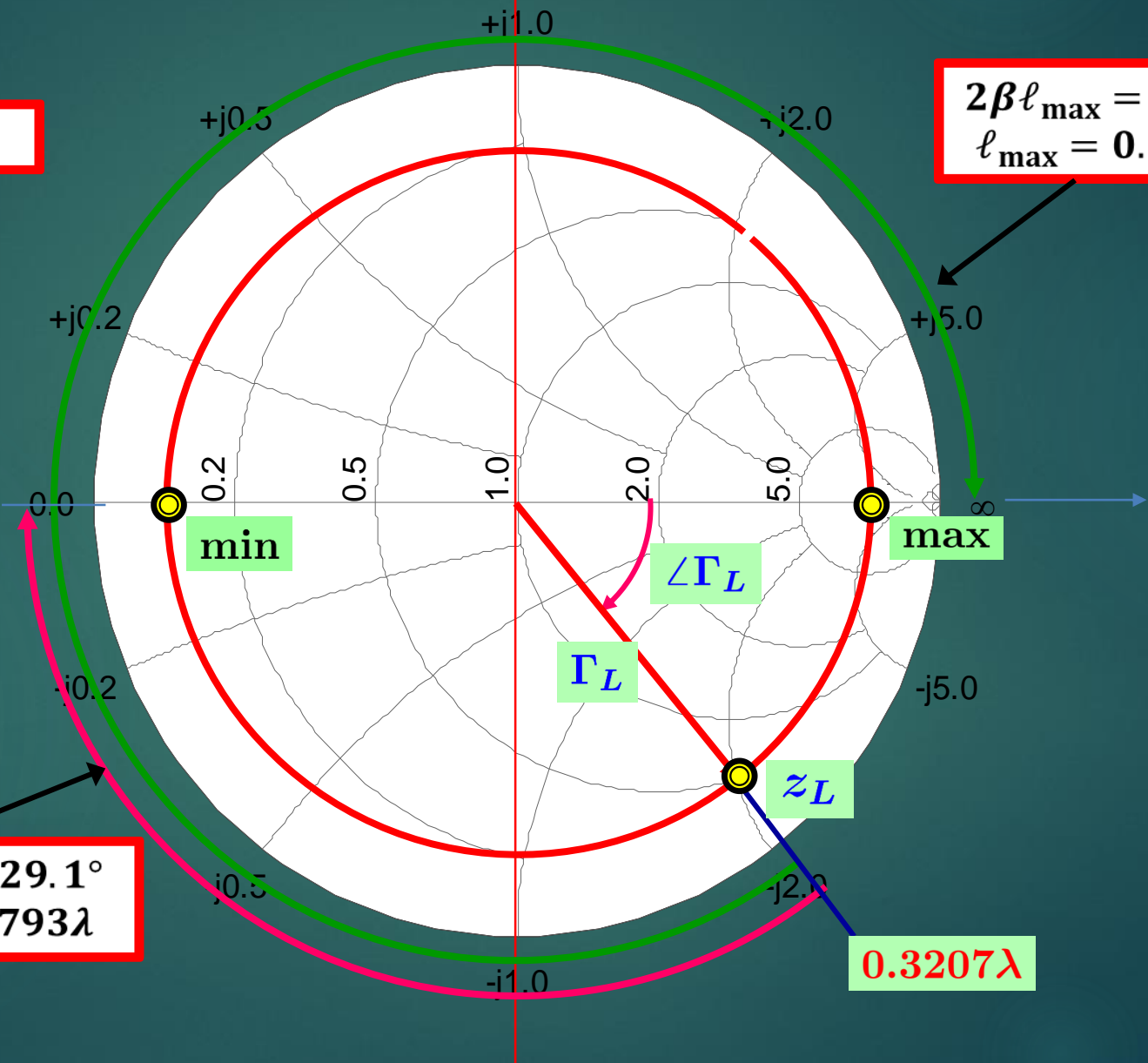$2\beta\ell_{\max} = 309.1^\circ$
 $\ell_{\max} = 0.4293\lambda$



$2\beta\ell_{\min} = 129.1^\circ$
 $\ell_{\min} = 0.1793\lambda$

0.3207λ

Switching Between Impedance and Admittance

- Consider the definition of the negative generalized reflection coefficient

$$\begin{aligned} -\Gamma(z) &= \Gamma_L e^{j(2\beta z + \pi)} = \Gamma_L e^{j\left(2\beta z + \frac{2\beta\lambda}{4}\right)} \\ &= \Gamma_L e^{j2\beta\left(z + \frac{\lambda}{4}\right)} = \Gamma\left(z + \frac{\lambda}{4}\right) \end{aligned}$$

- The **normalized TL admittance**

$$\tilde{y}(z) \equiv \frac{1}{\tilde{z}(z)} = \frac{1 - \Gamma(z)}{1 + \Gamma(z)} = \frac{1 + \Gamma\left(z + \frac{\lambda}{4}\right)}{1 - \Gamma\left(z + \frac{\lambda}{4}\right)} = \tilde{z}\left(z + \frac{\lambda}{4}\right)$$




- But what is $z + \lambda/4$? It's a **half rotation** around the Smith chart.
- Keep in mind $\tilde{z}\left(z + \frac{\lambda}{4}\right) = \tilde{y}(z)$ is only valid for normalized impedance and admittance. The actual values are given by

$$Z\left(z + \frac{\lambda}{4}\right) = Z_0 \cdot \tilde{z}\left(z + \frac{\lambda}{4}\right) \text{ and } Y(z) = Y_0 \cdot \tilde{y}(z) = \frac{\tilde{y}(z)}{Z_0}$$

Example:- $Z_L = 25 + j100 \Omega$, $Z_0 = 50 \Omega$ Find Y_L

Circle with constant $|\Gamma|$

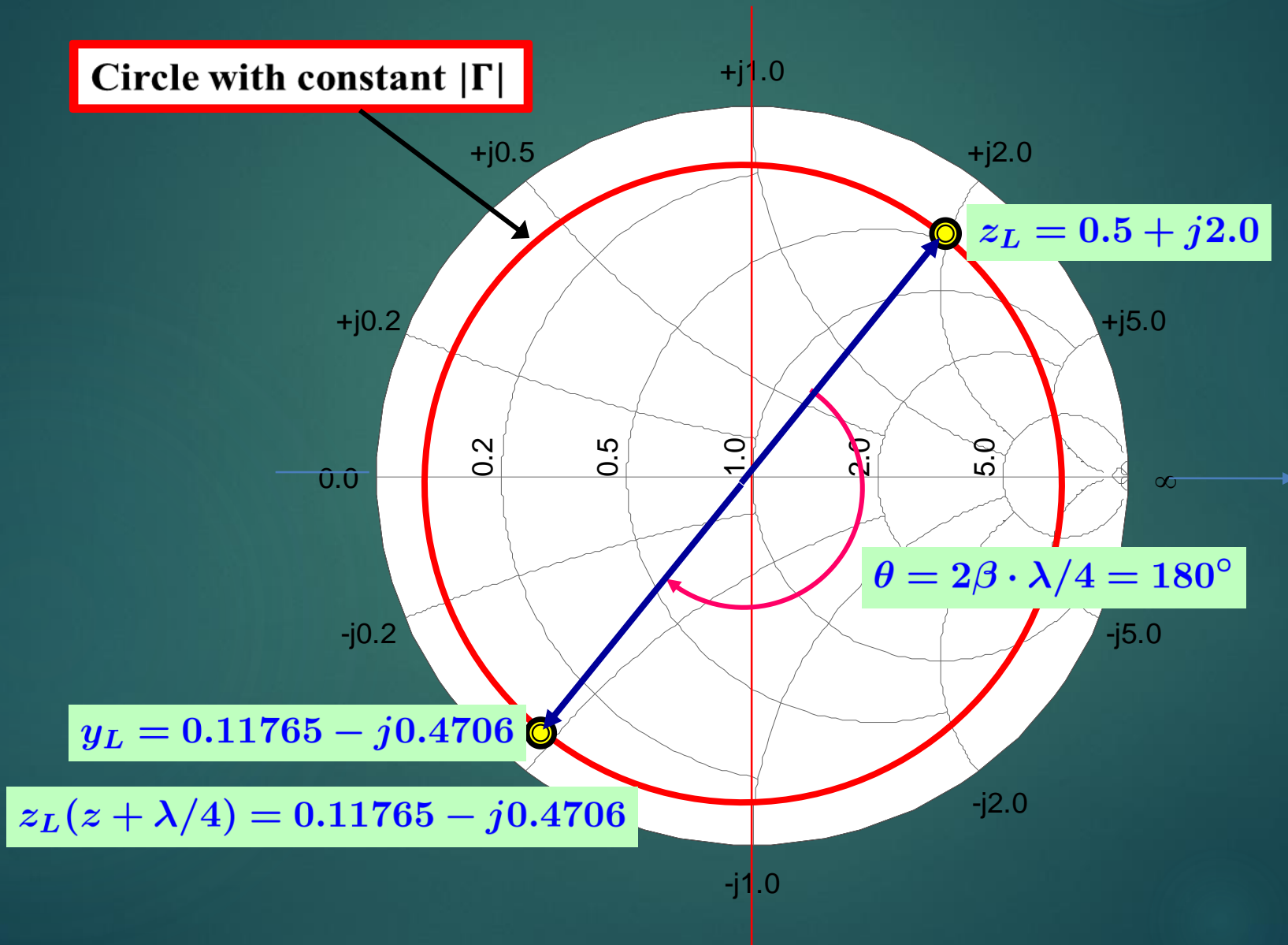

Thank you Very Much !!!