



Daffodil
International
University

Microwave Engineering

ETE 415

LECTURE 5
IMPEDANCE MATCHING

Impedance Matching


- Impedance matching (or simply “**matching**”) one portion of a circuit to another is an immensely important part of MW engineering.
- Additional circuitry between the two parts of the original circuit may be needed to achieve this matching.

Why is impedance matching so important?


- **Maximum power** is delivered to a load when the TL is matched at both the load and source ends.
- With a properly matched TL, more signal power is transferred to the load, which increases the **sensitivity** of the device and improve the signal-to-noise ratio of the system.
- Some equipment (such as certain amplifiers) can be **damaged** when too much power is reflected back to the source.
- **Minimize** reflections.

Impedance Matching

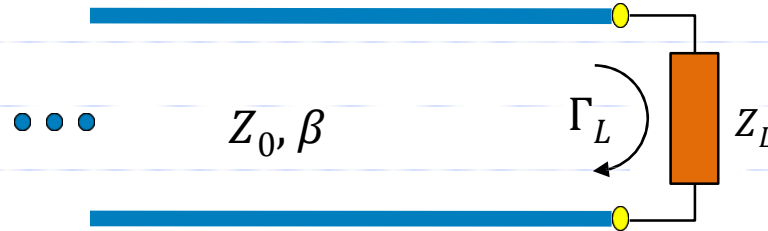- Consider the case of an arbitrary load that terminates a TL:



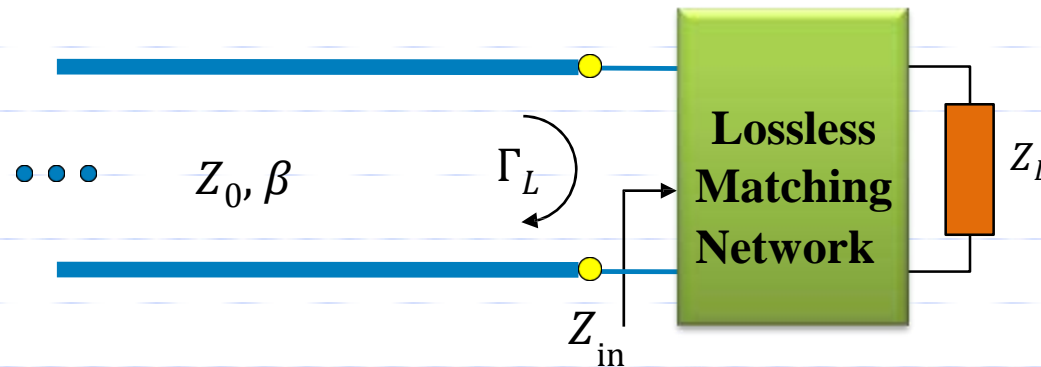- To match the load to the TL, we require $\Gamma_L = 0$.
- However, if $Z_L \neq Z_0$ **additional circuitry** must be placed between Z_L and Z_0 to bring the VSWR = 1, or least approximately so:




For $\Gamma_L = 0$, this implies $Z_{in} = Z_0$. In other words, $R_{in} = \Re[Z_0]$ and $X_{in} = 0$, if the TL is lossless.

Impedance Matching

- We will discuss **three methods** for impedance matching in this course:
 - Matching with **L-Sections** (lumped elements)
 - **Stub** tuners (T-line)
 - **Quarter wave** impedance transformers.
- **Factors** that influence the choice of a matching network include:
 - Physical complexity
 - Bandwidth
 - Adjustability (to match a variable load impedance) Implementation

Matching with L-Sections

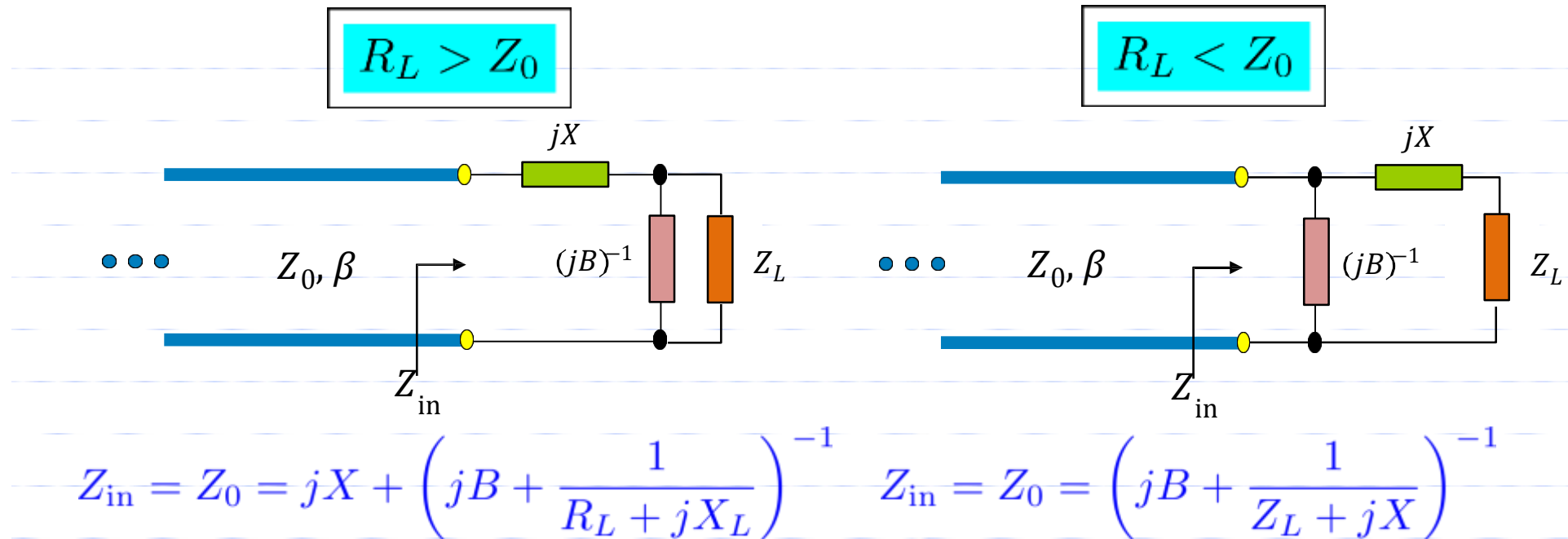- Since it uses lumped elements, it is applicable **only** if the frequency is low enough, or the circuit size is small enough
- This network topology gets its name from the fact that the series and shunt elements of the matching network form an **“L” shape**.
- Two possible L-Sections:




➡ where $Z_L = R_L + jX_L$.

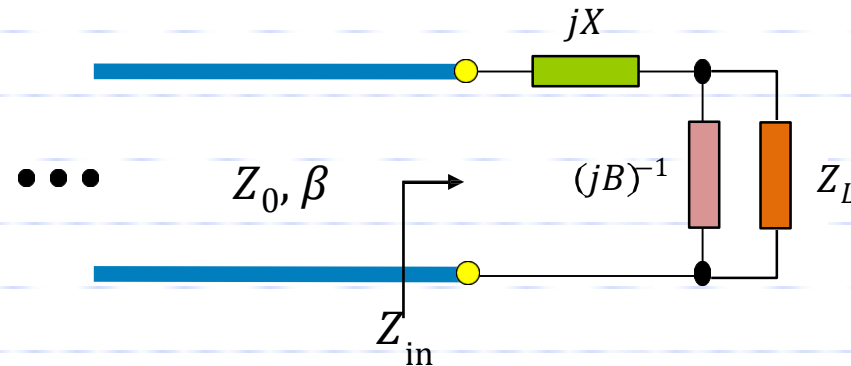Example

Design an L-section matching network to match a series RC load with an impedance $Z_L = 200 - j100 \Omega$ to a 100Ω line at a frequency of 500 MHz.

Since $R_L > Z_0$, we'll use the following circuit topology:




Normalization: $z_L = \frac{Z_L}{Z_0} = 2 - j1 \text{ p.u.}\Omega$

First solution

Rotated $1 + jx$ circle on admittance i.e., $y = 1 + jb$ chart

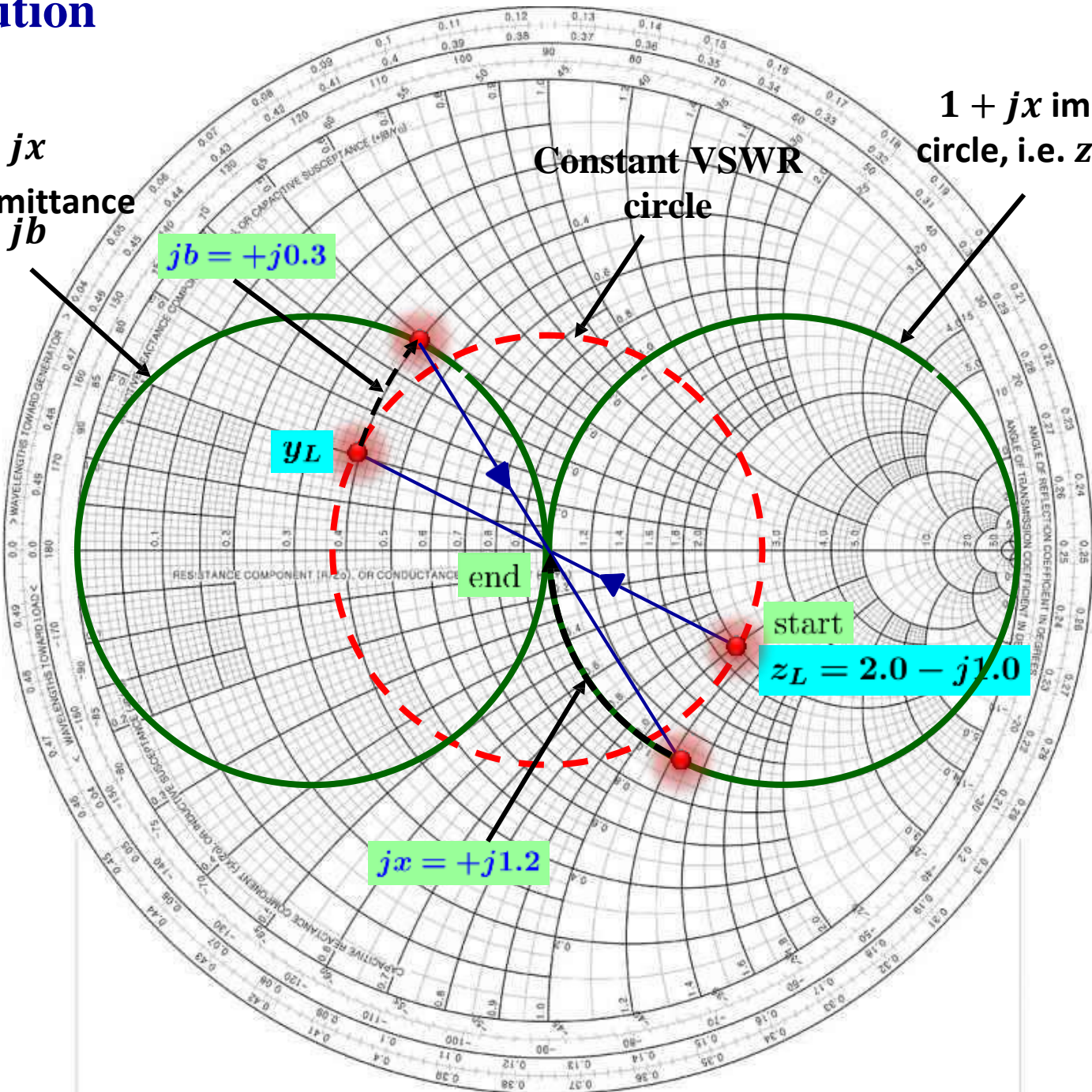$1 + jx$ impedance circle, i.e. $z = 1 + jx$



Solution

✍ Un-normalizing, we find that

$$jB = jb \cdot Y_0 = j0.3 \cdot \frac{1}{100} = j0.003 \text{ S}$$

$$jX = jx \cdot Z_0 = j1.2 \cdot 100 = j120 \ \Omega$$

✍ What are the L and C values of these elements?



➡ We can identify the type of element by the **sign of the reactance or susceptance:**

| | Inductor | Capacitor |
|-----|---|---|
| X | $Z_L = j\omega L$ | $Z_C = \frac{1}{j\omega C} = \frac{-j}{\omega C}$ |
| B | $Y_L = \frac{1}{j\omega L} = \frac{-j}{\omega L}$ | $Y_C = j\omega C$ |

Solution

Since $B > 0$, we identify this as a **capacitor**. Therefore,

$$jB = j\omega C = j0.003 \text{ S}$$


For operation at 500 MHz, we need $C = \frac{0.003}{2\pi f} = 0.95 \text{ pF}$

Since $X > 0$, we identify this as a **inductor**. Therefore,

$$jX = j\omega L = j120 \Omega$$

For operation at 500 MHz, we need $L = \frac{120}{2\pi f} = 38.8 \text{ nH}$

The final circuit is:

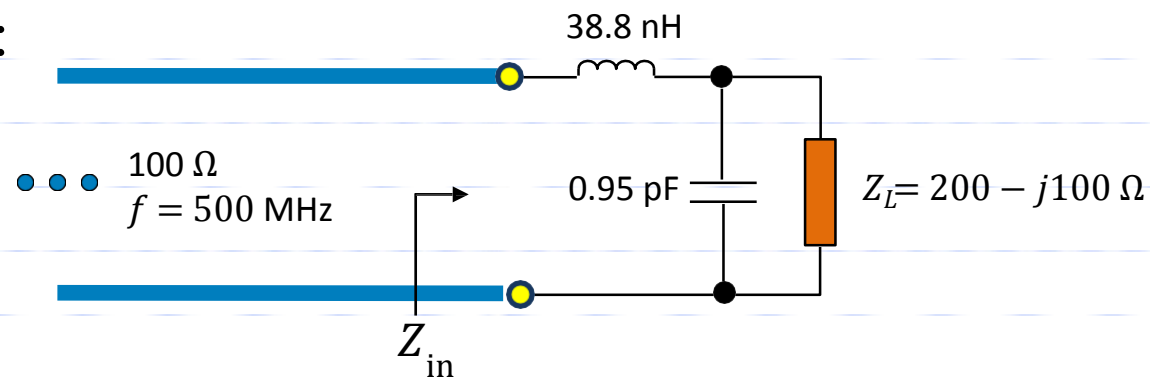


Let's check to see if we have really achieved a match at 500 MHz:

$$\begin{aligned} Z_{in} &= j2\pi fL + \left(j2\pi fC + \frac{1}{Z_L} \right)^{-1} \\ &= j120 + 100 - j120 = 100 + j0\Omega \end{aligned}$$

Second solution

Rotated $1 + jx$ circle
on admittance chart
i.e., $y = 1 + jb$

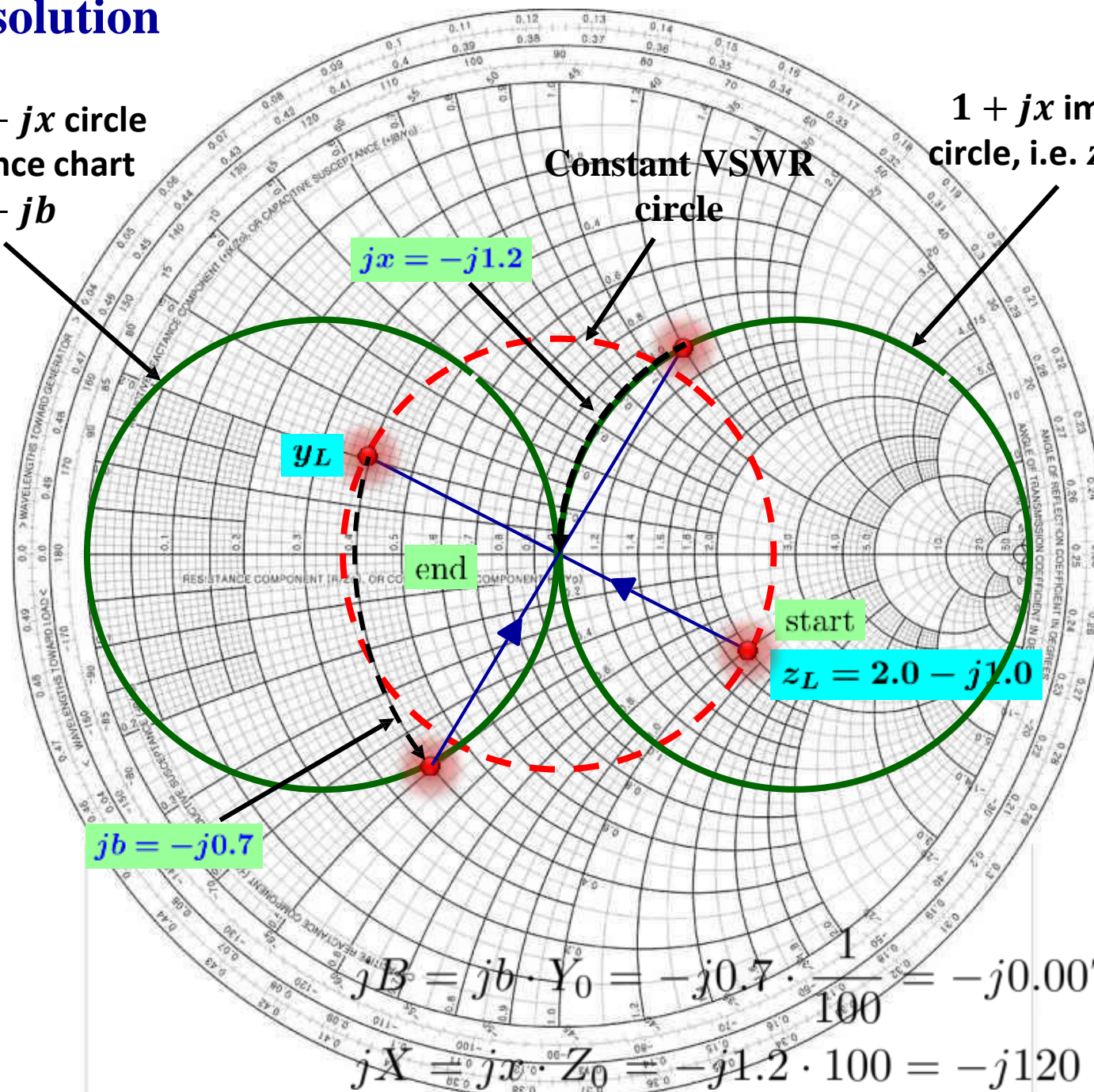$1 + jx$ impedance
circle, i.e. $z = 1 + jx$



$$jB = jb \cdot Y_0 = -j0.7 \cdot \frac{1}{100} = -j0.007 \text{ S}$$

$$jX = jx \cdot Z_0 = -j1.2 \cdot 100 = -j120 \text{ } \Omega$$

Solution

✍ Since $B < 0$, we identify this as a **inductor**. Therefore,

$$jB = \frac{-j}{\omega L} = -j0.007 \text{ S}$$

✍ For operation at 500 MHz, we need $L = \frac{1}{2\pi f B} = 45.47 \text{ nH}$


✍ Since $X < 0$, we identify this as a **capacitor**. Therefore,

$$jX = \frac{-j}{\omega C} = -j120 \text{ } \Omega$$

✍ For operation at 500 MHz, we need

$$C = \frac{1}{2\pi f X} = 2.65 \text{ pF}$$


✍ The final circuit is:

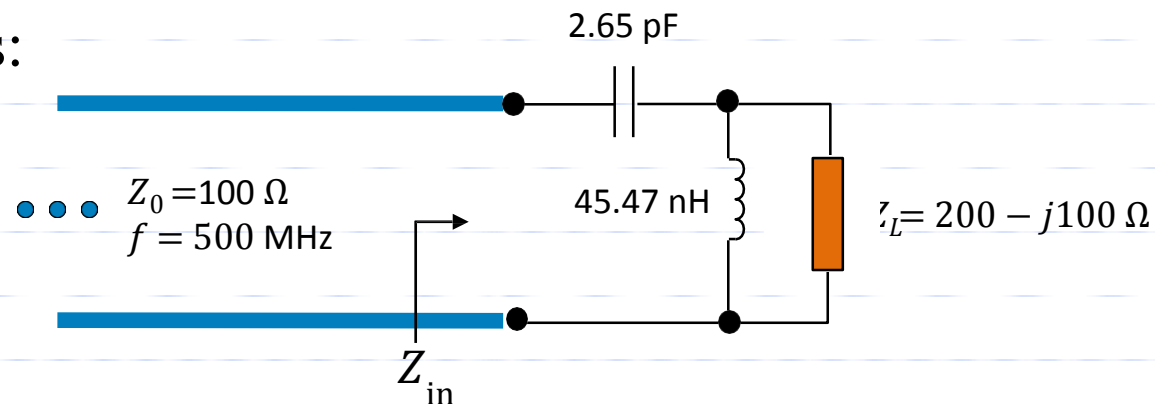

Single-Stub Tuner (SST) Matching

- The SST uses a shorted or open section of TL attached at some position along another TL.
- It does not require lumped elements.
- It can be used for extremely high frequencies.
- It uses segments of T-lines with the **same Z_0 (not necessary)** used for the feeding line.
- **Easy** to fabricate, the length can easily be made **adjustable** and little to **no power is dissipated** in the stub. (An open stub is sometimes easier to fabricate than a short.)
- It is very convenient for microstrip and stripline technologies.


Single-Stub Shunt Matching

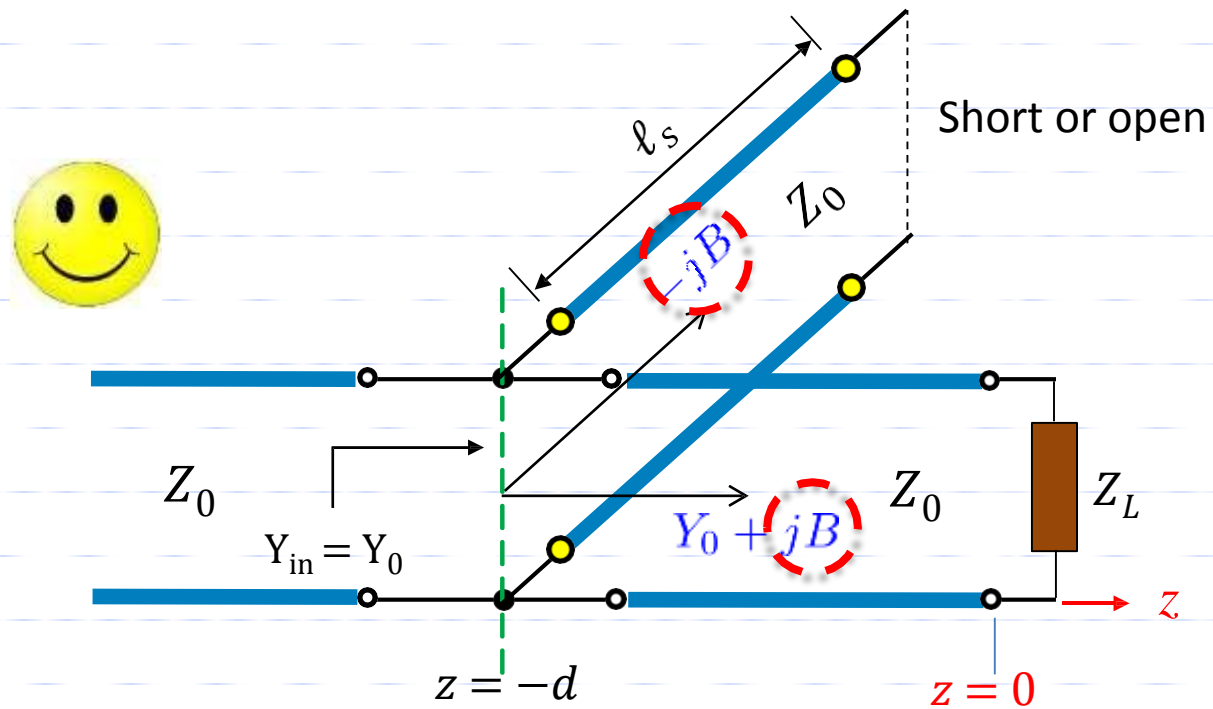

We only need to find d and l_s

- First TL converts $Y_L = 1/Z_L$ to an admittance $Y_0 + jB$
- Second TL converts a short or an open to an admittance $-jB$

Single-Stub Series Matching

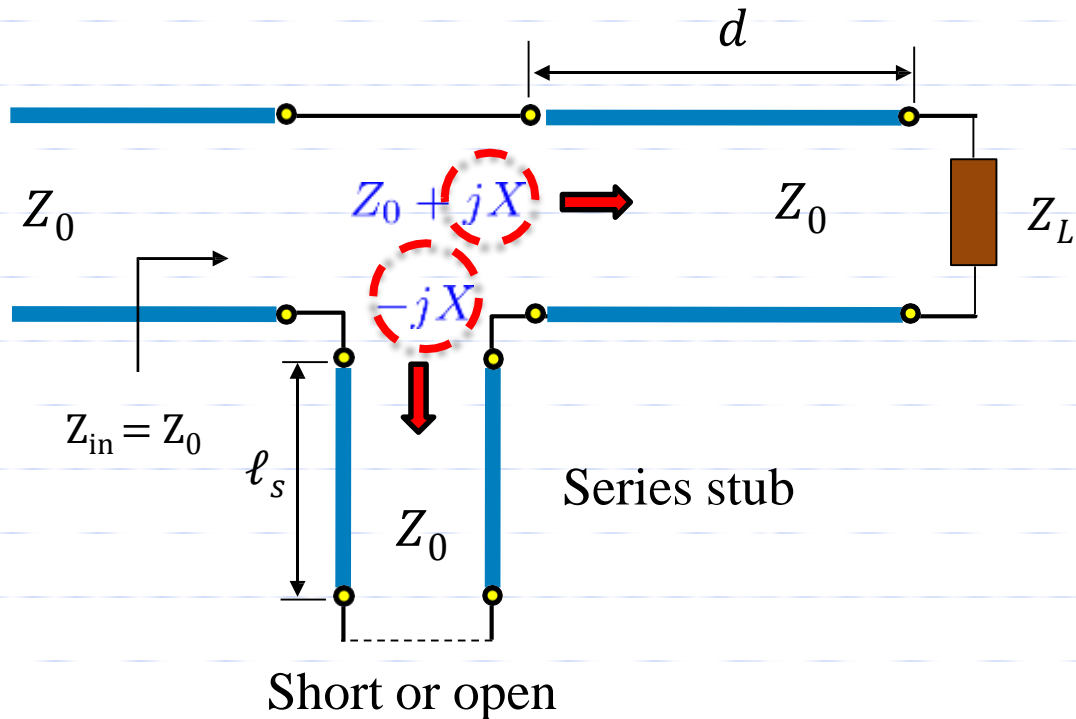

- **First** TL converts Z_L to an impedance $Z_0 + jX$
- **Second** TL converts a short or an open to an impedance $-jX$
- We only need to find d and ℓ_s

SST Using the Smith Chart


✦ In terms of quantities **normalized** to Z_0 or Y_0 , the geometry is

✦ Recall that the operation of the SST requires that

1. d is chosen such that y' has **real part = 1**, i.e., $y' = 1 \pm jb_s$.

2. The imaginary part of y' is **negated** by the stub susceptance after choosing the proper length ℓ_s .


✦ This produces the **matched state**

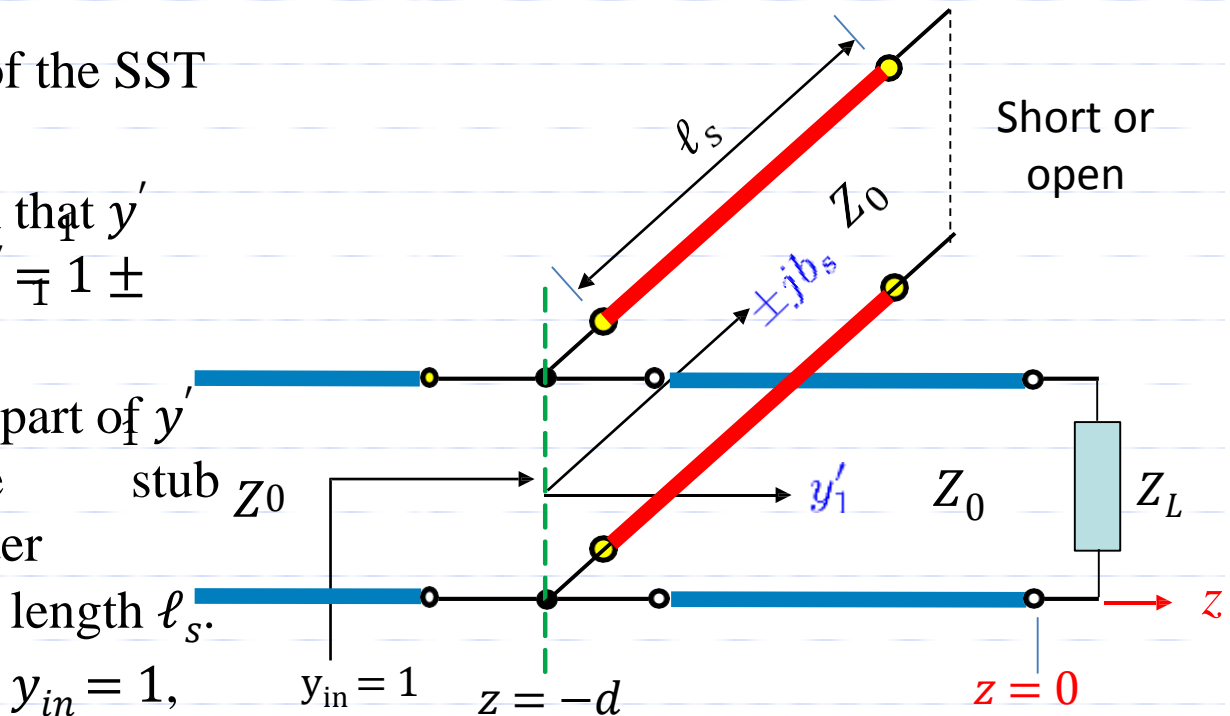


✦ **Example 5.2: Using the Smith chart, design a shorted shunt, single-stub tuner to match the load $Z_L = 60 - j80 \Omega$ to a TL with characteristic impedance $Z_0 = 50 \Omega$.**

✦ The normalized load impedance is: $z_L = 1.2 - j1.6$ p.u. Ω

First solution

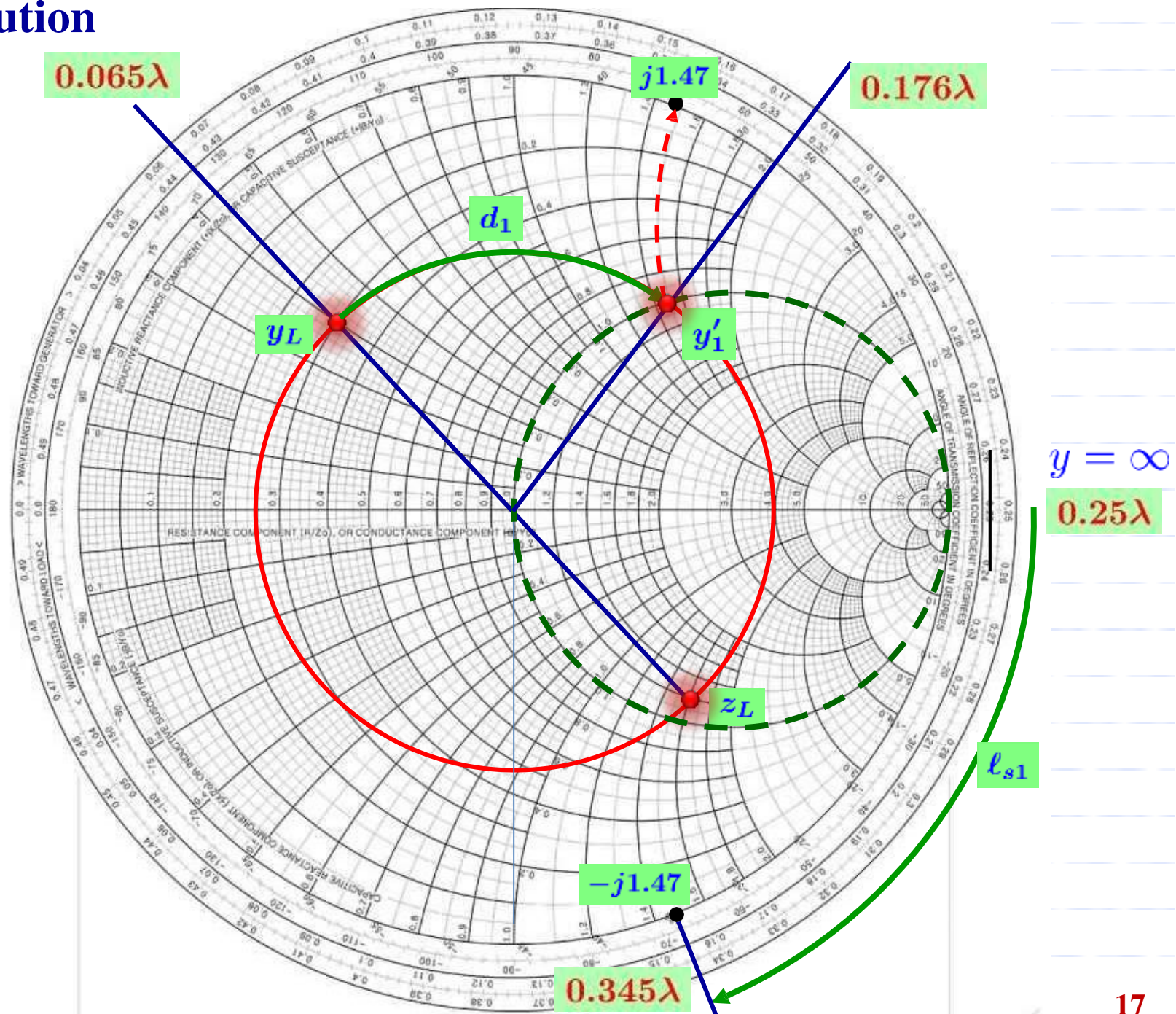

Second solution

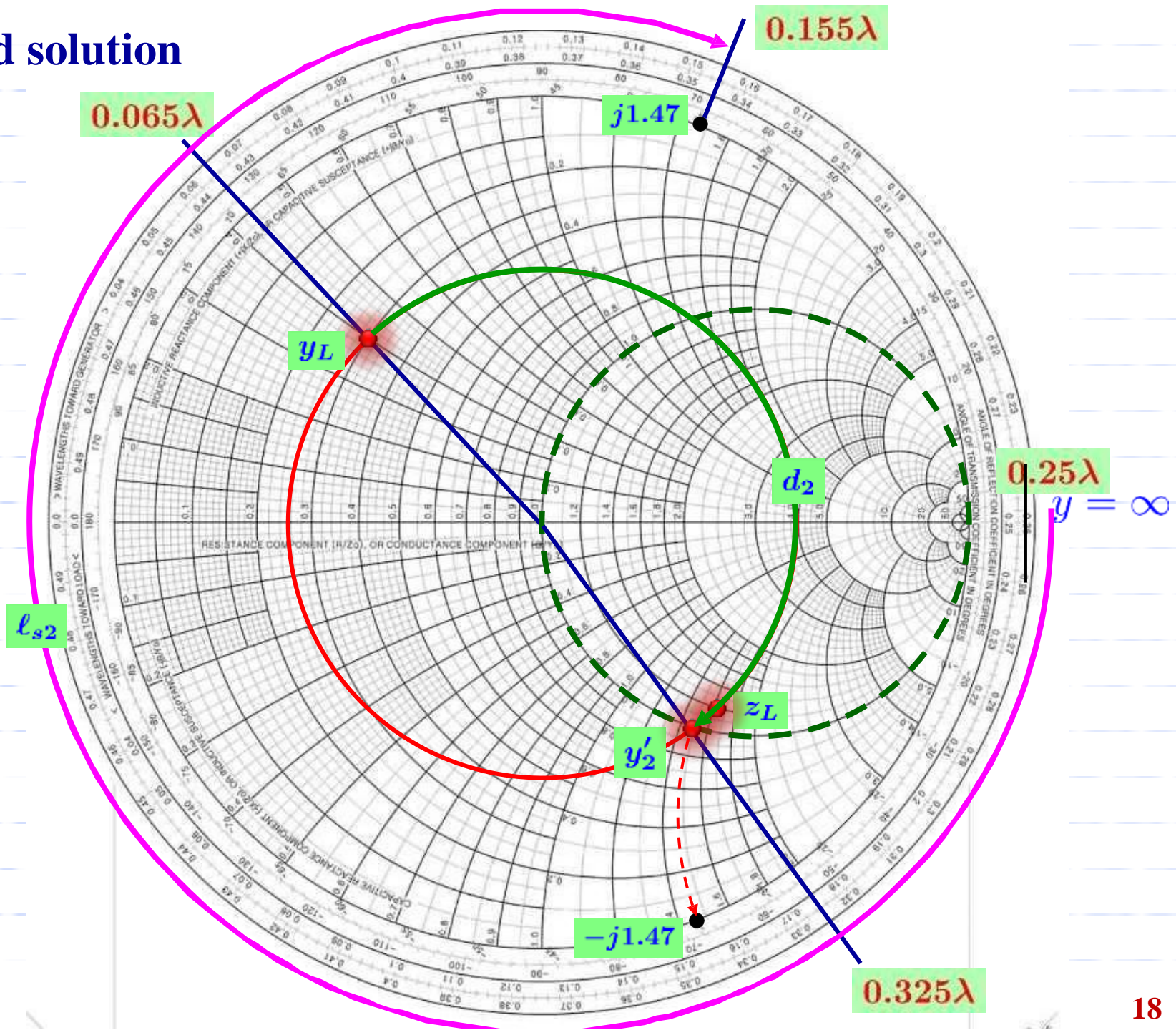

Solution: Smith

There will be **two solutions**. Both of these give $y = 1 \pm jb_1$.

For this example, we find from the Smith chart that

(I) $y'_1 = 1 + j1.47$

(II) $y'_2 = 1 - j1.47$

From these rotations we can compute d as

(I) $d_1 = 0.176\lambda - 0.065\lambda = 0.110\lambda$

(II) $d_2 = 0.325\lambda - 0.065\lambda = 0.260\lambda$

Next, find the stub lengths ℓ_s :


(I) want $b_{s1} = -1.47$

(II) want $b_{s2} = 1.47$

When either of these two susceptances is added to y'_1 , then $y_{in} = 1$.

Solution: Smith

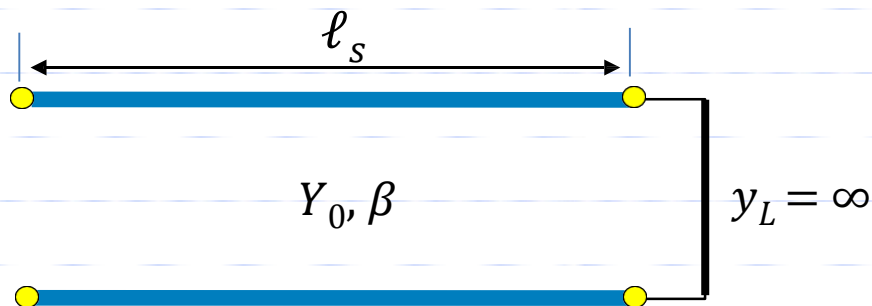✍ The stub lengths can be determined directly from the Smith chart.



✍ On the Smith admittance chart, $y_L = \infty$ is located at $\Re \{ \Gamma \} = 1$, $\Im \{ \Gamma \} = 0$. From there, rotate “wavelengths towards generator” to:

$$(I) \ b_s = -1.47 \Rightarrow \ell_{s1} = 0.345\lambda - 0.25\lambda = 0.095\lambda$$



$$(II) \ b_s = +1.47 \Rightarrow \ell_{s2} = 0.25\lambda + 0.155\lambda = 0.405\lambda$$


✍ The final two solutions are:

$$(I) \ d_1 = 0.110\lambda \text{ and } \ell_s = 0.095\lambda$$

$$(II) \ d_2 = 0.260\lambda \text{ and } \ell_s = 0.405\lambda$$

Solution: Smith

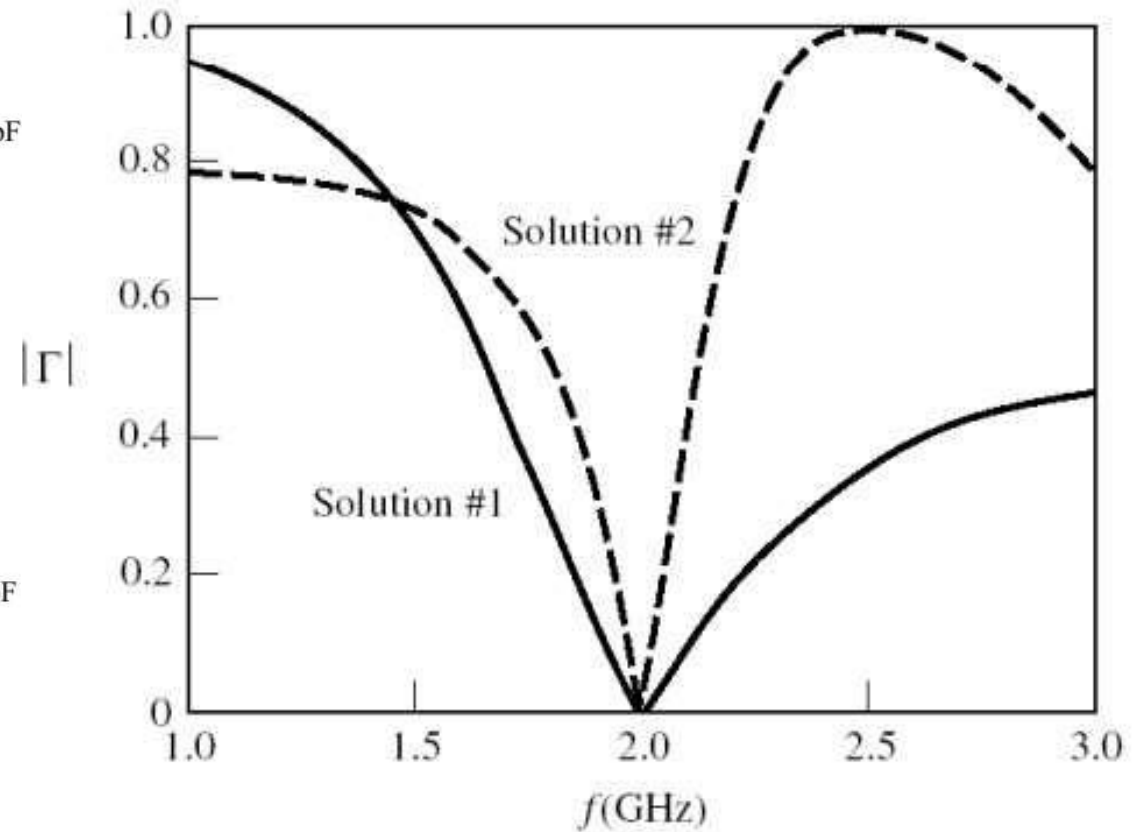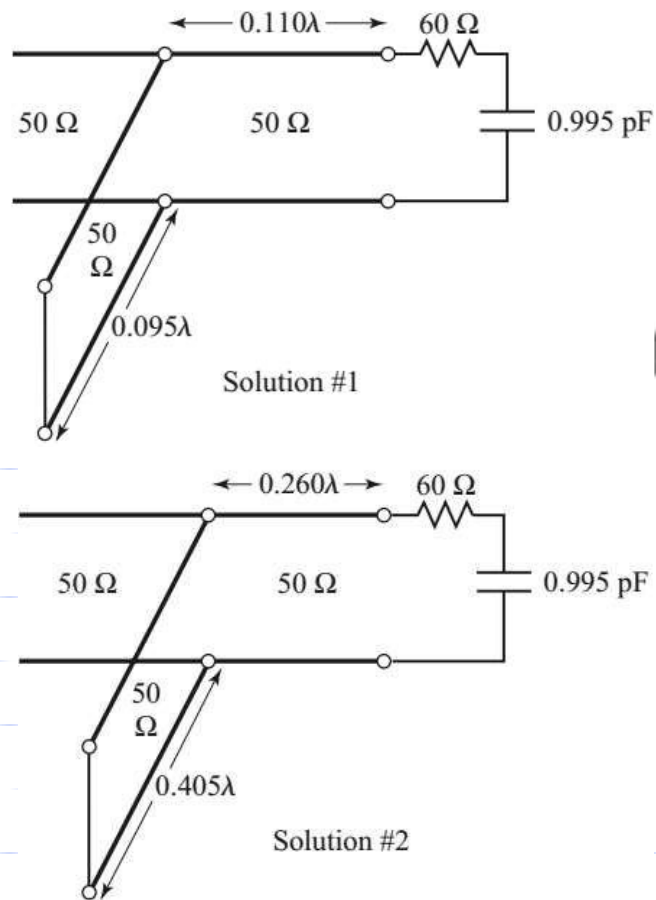


 **Solution 1** has a significantly better bandwidth than solution 2.

 Shorter stub produces wider bandwidth.

Quarter-Wave-Transformer Matching

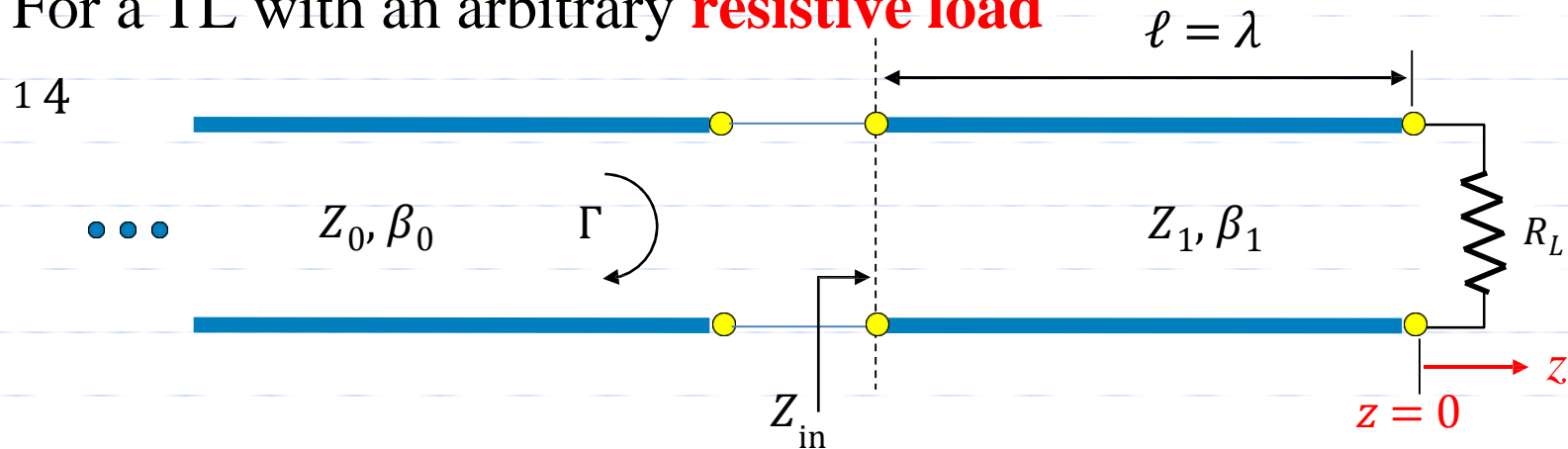For a TL with an arbitrary **resistive load**



the input impedance of the right-hand TL is given

as

$$Z_{in} = Z_1 \frac{R_L + jZ_1 \tan(\beta_1 l)}{Z_1 + jR_L \tan(\beta_1 l)} \quad (1)$$

At $l = \lambda_1/4$ $\beta_1 l = \frac{2\pi}{\lambda_1} \frac{\lambda_1}{4} = \frac{\pi}{4}$ **electrical length**

Since $\tan \beta_1 l \rightarrow \infty$. Using this result in (1) gives

$$Z_{in} = \frac{Z_1^2}{R_L} \quad (2)$$

Quarter-Wave-Transformer Matching

- ✦ This result is an interesting characteristic of TLs that are exactly $\lambda/4$ long.
- ✦ We can harness this characteristic to **design a matching network** using a $\lambda/4$ -length section of TL.

$$Z_1 = \sqrt{Z_0 R_L} \quad (3)$$

- ✦ Note that we can adjust Z_1 in (2) so that $Z_{\text{in}} = Z_0$. In particular, from (2) with $Z_{\text{in}} = Z_0$ we find
- ✦ In other words, a $\lambda/4$ section of TL with this particular characteristic impedance will present a perfect match ($\Gamma = 0$) to the feedline (the left-hand TL).

This type of matching network is called a **quarter-wave transformer (QWT)**.

Disadvantages of QWTs



1. A TL must be **placed** between the load and the feedline.
1. A very **special characteristic impedance** (i.e., Z_1) for the QWT is required, which depends both on the load resistance, R_L , and the characteristic impedance of the feedline, Z_0 .
1. QWTs work perfectly only for **one load at one frequency**. (Actually, it produces some bandwidth of “acceptable” VSWR on the TL, as do all real-life matching networks.)

Thank you Very Much !!!